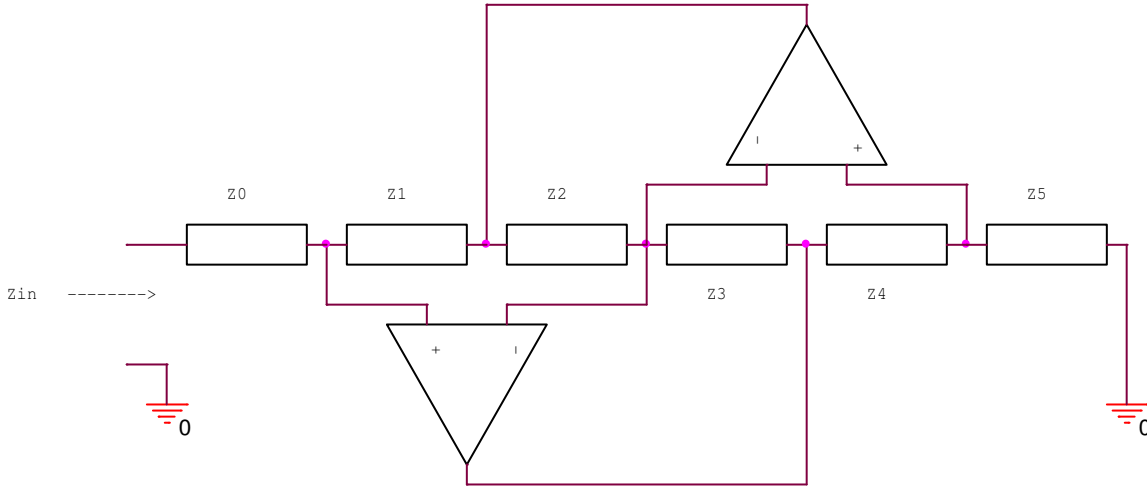


ENEE 417 Experiments Week 7 Spring 2011
 Week starting 03/07/11; active circuits (C=>L, R=>-R)

- The following circuit is called a GIC (=General Impedance Converter). When the op-amps are ideal, it is known that (where all Z's are impedances)

$$Z_{in}(s) = Z_0(s) + (Z_1(s) \cdot Z_3(s) \cdot Z_5(s)) / (Z_2(s) \cdot Z_4(s))$$



- Verify the above formula for $Z_{in}(s)$
 - Choose $Z_0=0$, $Z_1(s)=Z_2(s)=Z_3(s)=Z_5(s)=R$, $Z_4(s)=1/(Cs)$. In this case loading by a capacitor makes $Z_{in}(s)$ look like an inductor. Construct the circuit using the 1458 op-amps and various values of R and C (start with $R=2K\Omega$ and $C=1\mu F$).
 - Devise means to test if an inductor is really seen, one means being via a time constant evaluation and another via an LC resonance.
 - Repeat when $Z_0=0$, $Z_1=Z_3=Z_5=R$, $Z_2(s)=Z_4(s)=1/(Cs)$.
- In the above circuit add Z_6 on the top op-amp as feedback from the output to the + input. Choose $Z_0=0$, $Z_1=Z_2=Z_3=Z_4=R$, $Z_6=R/2$.
 It is surmised that $Z_{in}(s) = -Z_5(s)$.
 Check this analytically and devise an experiment to check your calculations.

- Catch up on all previous projects so that you can start your base paper experiments next time.