

ENEE 417 -Spring 2011
Weeks #5 & 6 starting M 02/21/11
Designs #2: Astable Multivibrator and Ring Oscillator Designs; VLSI & Spice Extraction

In this experiment a good reference is Sedra and Smith (pages 1026-1027 of the 5th edition)
For the active devices use the 4007 CMOS transistor package.

1. Construct the astable circuit of Figure 11-15 (a) of the above reference and make measurement to verify Figure 11.15(b) using various resistors and capacitors.
2. Construct both a three stage and a five stage ring oscillator and record via the GPIB the oscillations. Check the results of Figure 11.16 of the above reference.
- 3 Insert various capacitors at the outputs of the stages and see the effects. Among the capacitor values use one of the super-capacitors (whose values are on the order of Farads). Check also the effect of using an even number of stages.
4. In Spice use MOSIS 1.6u level 4 CMOS model parameters, available in the bicmos12.lib files, to design a three stage inverter (for this adjust the W and L so that a symmetric bias yields zero output voltage for zero input voltage; make sure that both W and L are bigger than 7microns). Based on your Spice design make a vlsi layout of your three stage ring oscillator. Using the layout obtain a Spice extraction. Insert the models used for your original Spice design and check that your layout gives comparable results to your original design.