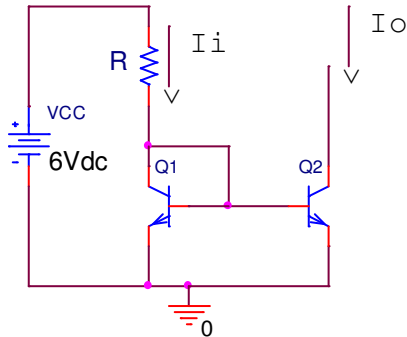



ENEE 303 Midterm Exam, Spring 2012

100 points, 75 minutes, open book, open notes, open calculators [but not open computers]. If stuck go on to the next problem. Good luck and have a good spring break!

1. (35 points, 20 minutes) Assuming identical transistors with their base-emitter diode governed by the base emitter saturation current, $I_s = 6E-16$, and having the forward beta, $B_f=100$, give the resistance, R , needed to give an output current of 6 milliAmps.



2. (30 points, 20 minutes) For the following inverter assume that M_p and M_n are fully complementary with Spice parameters $K_P=4E-5$, $|V_{TO}|=1$, $LAMBDA=0.1$, $C_{gs}=C_{gd}=10pFd$, and $W=L=10uM$. Find symbolically and numerically the small signal gain, $V_o/V_i(s)$ when loaded with the capacitor $C=20pFd$. Give also its zeros and poles.

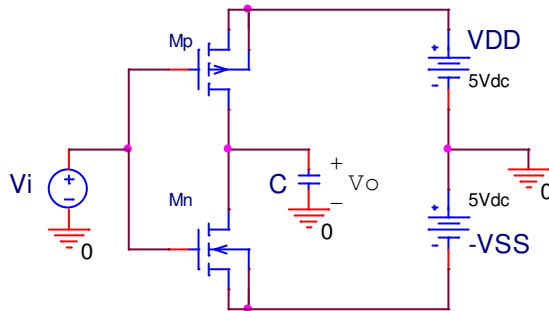

3. (35 points, 20 minutes) For the following circuit assume the open circuit transfer function is $V_1/V_o(s) = 1/[C_1C_2LRs^3 + C_2Ls^2 + (C_1+C_2)Rs + 1]$.

Assume also that $R_1=R_i$ are very large and $K=R_f/R_1$.

- Give the transfer function $V_o/V_i(s)$ as a ratio of two polynomials.
- Give the conditions for sinusoidal oscillations and the oscillation frequency as well as the poles of the transfer function V_o/V_i .

