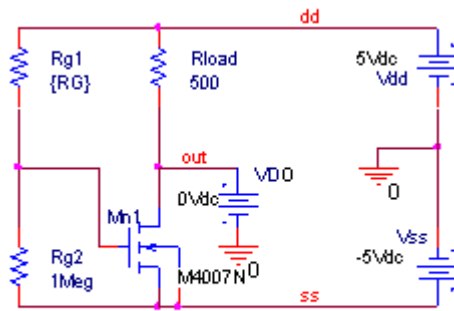


File: f:/coursesS12/303/303S12hmwk2.doc RWN 02/10/12b  
 303 Spring 2012– Homework 2 Due M 02/13/12 in class  
 In the following all the transistors are 4007s.

1. (50 points, CMOS biasing)

a) For the following circuit run curves to show the possible Q points for choices of  $R_{g1}$  {use  $100K \leq R_G \leq 10Meg$  with 1 point per log step; plot  $I_D$  and current in  $R_{load}$  on the same curves).

b) For  $R_{g1}=1Meg$  Ohm give the small signal  $g_m$ , (use  $I_D$  from a non-parametric run of PSpice) and calculate with it the corresponding voltage gain,  $-g_m R_{load}$ . Check by hand calculation of the  $I_D$  using the PSpice model parameters.




PARAMETERS:  
 $R_G = 1Meg$

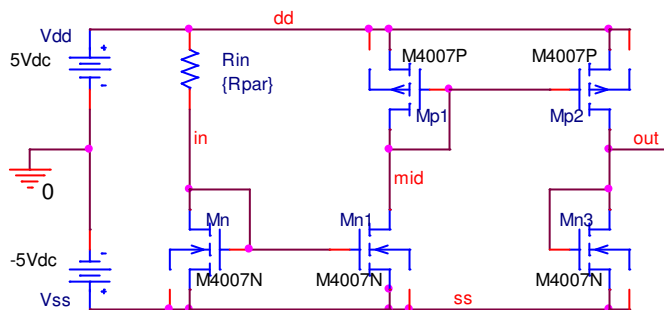2. (50 points, Current Mirrors)

The following circuit illustrates two types of current mirrors. Use PSpice DC runs varying  $V_{dd}$  near 5V to obtain the desired results.

- With parameterized  $R_{in}$  for  $100 \leq R_{par} \leq 100K$  in logarithmic steps, 1 curve per step, determine the resulting currents into  $M_n$ , and  $M_{n2}$  as well as  $M_{p1}$  and  $M_{p2}$  (Show the  $I_{Dn}$ 's in one plot and the  $I_{Dp}$ 's in another)
- Over the same range of  $R_{in}$  determine the voltages at in, mid, and out
- Since the currents are supposed to be equal, explain why they are not.



PARAMETERS:  
 $R_{par} = 1K$