

1. (50 points, BJT npn and pnp amplifiers)

Design an npn amplifier (using a 2N3904) for $|I_C|=5.2\text{mA}$, $R_L=R_C=1\text{Kohm}$ and $R_E=100\text{Ohm}$. Repeat for a pnp one (using a 2N3906). Give the voltage gains, VCE and the range of values of the single battery VCC needed. For the base bias resistors choose one at a minimum of 1MegOhm. Run Spice to check your designs.

2. (50 points, NMOS and PMOS amplifiers)

Replace the transistors in the circuits of problem 1 above by 4007 CMOS ones and calculate the new gains. Also run Spice to check your results.

3. (50 points; RC phase shift amplifier)

For the RC phase shift amplifier of Figure 17.7, p. 1345, assume the amplifier is realized by an Op-amp inverter of the type used in Homework 1, Problem 2 with $R_2=10\text{Meg}$.

- a) In terms of R and C find R1 needed for oscillations and give the oscillation frequency in Herz.
- b) Do a Spice run for $R=10\text{KOhm}$ and $C=20\text{nFd}$ and check against your calculations of part a). Submit your plots of amplifier output versus time.