

To look at

Diodes Chap. 3, p. 150 F. 3.13 & eq. (3.40)

Chap. 4 pp. 174-175

load line p. 180, F. 4.11

small signal p. 184, F. 4.13  $g_d$  eq. (4.17-18)

BJT Chap. 6 p. 374, F. 6.18



p. 375, F. 6.19

MOS Chap. 5 p. 249, table 5.1 (curves & eq.)

p. 255 F. 5.17 (Early effect)

hybrid- $\pi$ , p. 711, F. 9.2

Load line & small signals

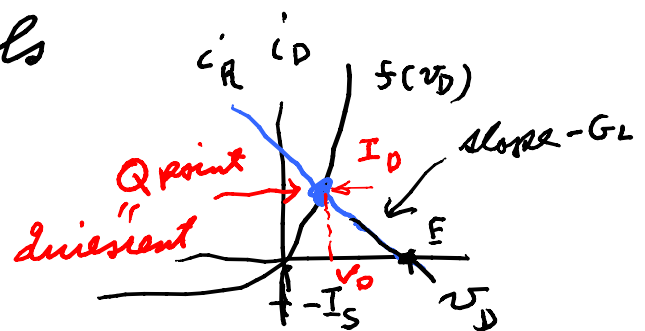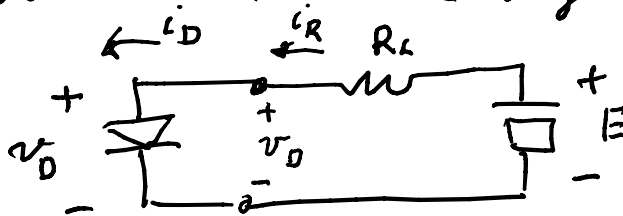

$$f(v_D) = i_D = I_S (e^{+v_D/V_T} - 1) \quad , \quad V_T = \text{thermal voltage} = kT/q$$

$$f(v_D) = i_D = i_R = (E - v_D)/R_L = G_L(E - v_D)$$

Desire to know the Q point


$$I_S (e^{v_D/V_T} - 1) = G_L E - G_L v_D \Rightarrow \text{solve for } v_D$$

For small changes, expand in a series expansion around the Q point

$$i_R = G_L E - G_L v_D = f(v_D) = f(v_D) + \left. \frac{\partial f}{\partial v_D} \right|_{v_D=v_D} (v_D - v_D) + \frac{1}{2} \left. \frac{\partial^2 f}{\partial v_D^2} \right|_{v_D=v_D} (v_D - v_D)^2 + \dots$$

$$v_D = V_D + v_d \Rightarrow G_L E - G_L (V_D + v_d) = f(V_D) + \left. \frac{\partial f}{\partial v_D} \right|_{V_D} v_d \quad \leftarrow (\text{ignore?})$$

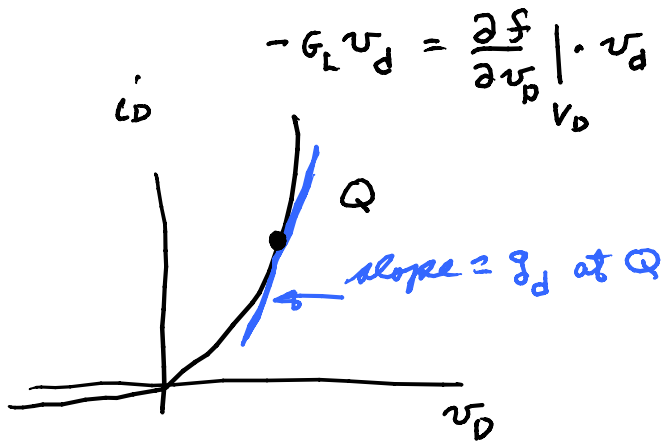" total bias
" signal
" bias
" signal
"  $I_D$ 
"  $v_D$




$$f(v_D) = I_S (e^{v_D/V_T} - 1)$$

$$\left. \frac{\partial I_D}{\partial v_D} \right|_{V_D} = \left. \frac{\partial f}{\partial v_D} \right|_{V_D} = \frac{I_S \cdot e^{v_D/V_T}}{V_T} \Big|_{V_D} = \frac{I_D}{V_T} = g_d$$

= conductance of the diode at Q

bias:  $G_L E - G_L V_D = I_D = I_S (e^{V_D/V_T} - 1) \approx I_S e^{V_D/V_T}$  if in forward region

redraw: bias

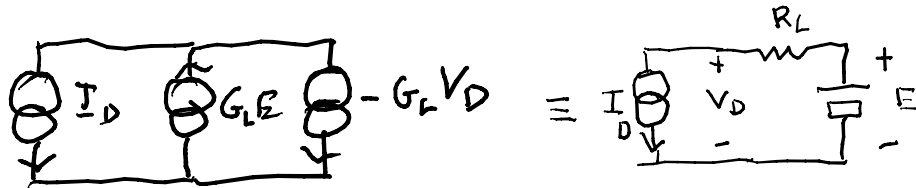

(small) signal

