
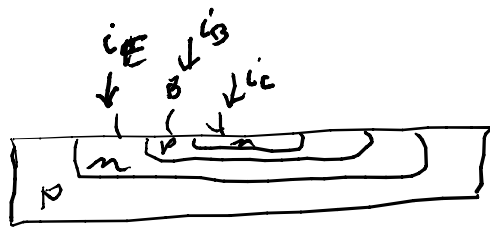
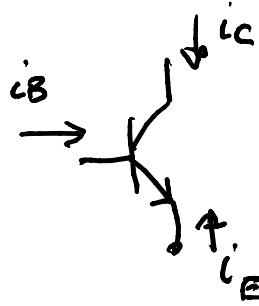
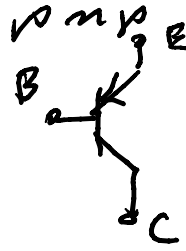


BJT = bipolar junction transistor

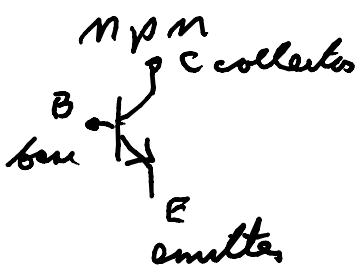

KCL $i_C + i_B + i_E = 0$

$i_C = -\alpha i_E$




by a small base $\alpha < 1$

$i_C + i_B - \frac{1}{\alpha} i_C = 0 \Rightarrow (1 - \frac{1}{\alpha}) i_C = -i_B$

$i_C = \frac{-\alpha}{\alpha - 1} i_B = \frac{\alpha}{1 - \alpha} i_B$

$= \beta i_B$

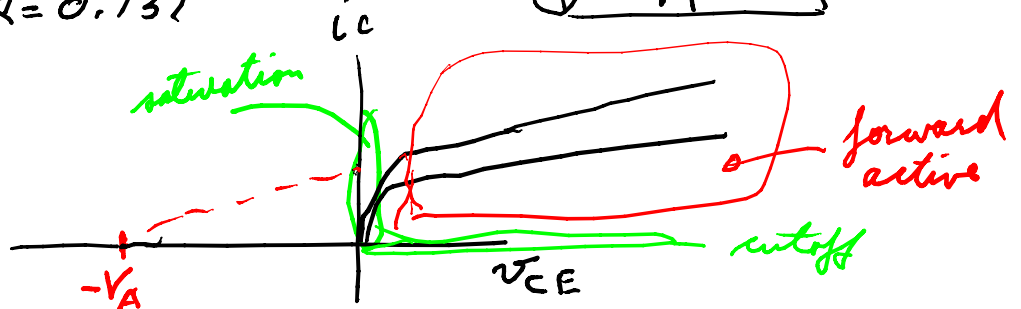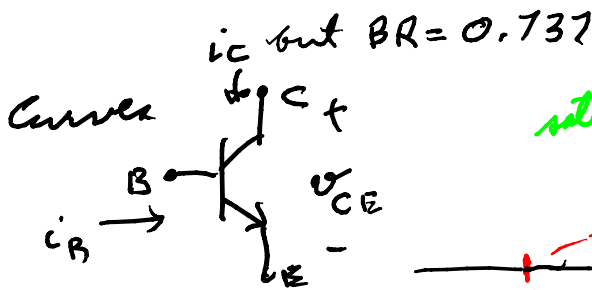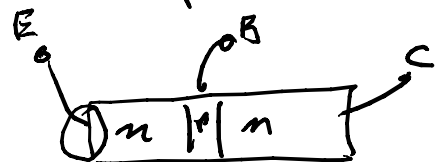for 2N3904, $\beta = 416.4$ in spec
 $= \beta_F$





$V_A =$ Early Voltage

$V_{AF} = 74.03$

(18.7 for PNP 2N3906)

Normally: forward bias BE junction

back bias BC junction

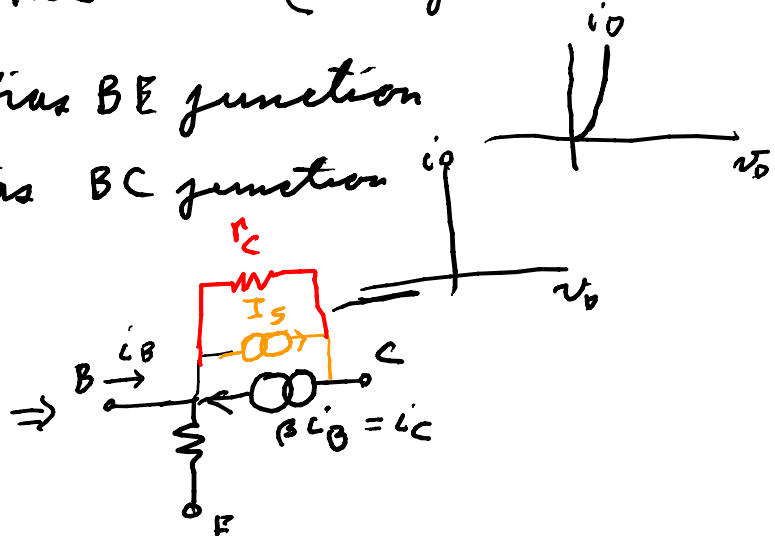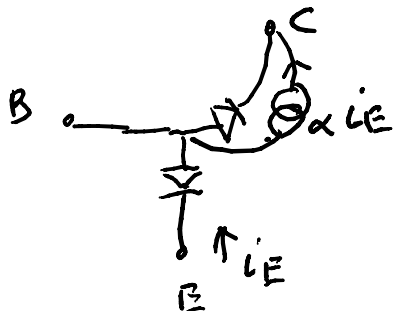

for small signals do a Taylor series expansion

$$i_c(v_{CE}, i_B) = I_C + \frac{\partial I_C}{\partial v_{CE}} (v_{CE} - V_{CE}) + \frac{\partial I_C}{\partial i_B} (i_B - I_B) + \dots$$


$$i_r = i_c - I_C, \quad v_{r,r} = v_{CE} - V_{CE}$$

$$i_b = i_B - I_B$$


$$i_r = \frac{\partial I_C}{\partial v_{CE}} \cdot v_{r,r} + \beta \cdot i_b$$

$$\quad \quad \quad \parallel$$

$$\quad \quad \quad g_r$$


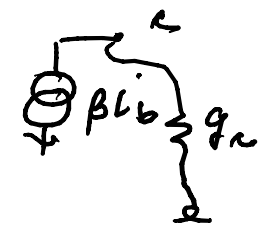


to get g_r

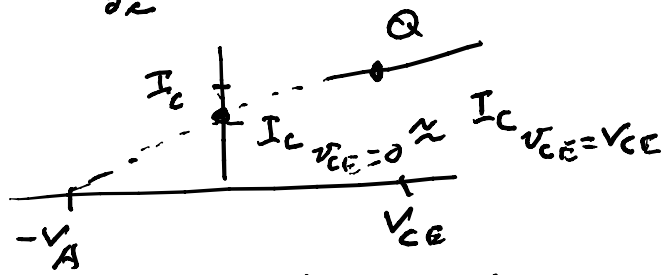

$$g_r = \text{slope of this curve} \approx \frac{I_C}{V_A}$$

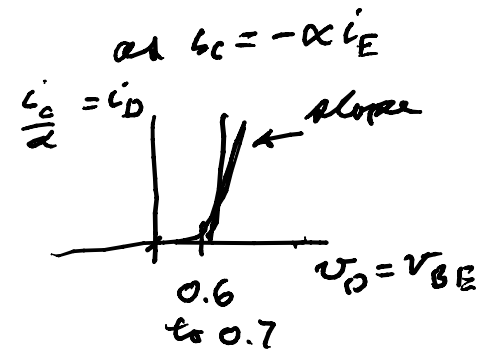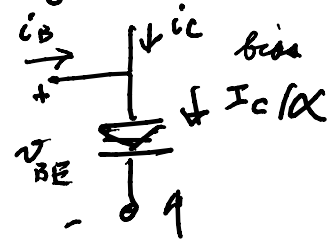look at the emitter in the forward active region




(forward bias BE junction)

$$i_D = I_{SE} (e^{v_{BE}/V_T} - 1)$$

$$g_E = \frac{\partial i_D}{\partial v_{BE}} \Big|_Q = \frac{I_{SE}}{V_T} \cdot e^{v_{BE}/V_T} = \frac{-I_E}{V_T} = \frac{I_C}{\alpha V_T} = \text{diode conductance}$$


$g_r = \text{conductance}$

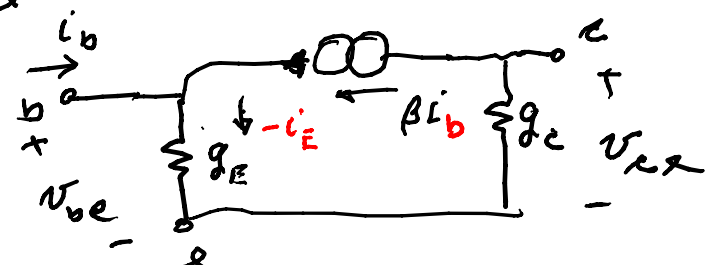

Normal equivalent circuit uses voltage controls & here is a current controlled source, βi_b

(see p. 421 for Y matrix form)
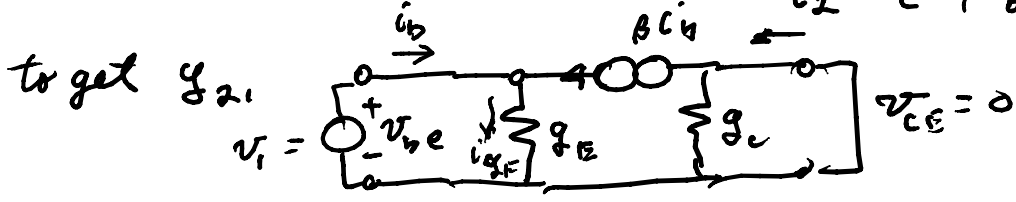
$$\begin{bmatrix} i_b \\ i_c \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_{be} \\ v_{ce} \end{bmatrix} \quad \text{note } y_{21} \Rightarrow i_c = y_{21} \cdot v_{be} \text{ if } v_{ce} = 0$$



$$g_E v_{be} = i_{g_E}; \quad i_b' = g_E v_{be} - \beta i_b \Rightarrow (1+\beta) i_b = g_E v_{be}$$

$$\beta i_b = \frac{\beta}{1+\beta} \cdot g_E \cdot v_{be} \Rightarrow y_{21} = \frac{\beta}{1+\beta} \cdot g_E = \frac{\beta}{1+\beta} \cdot \frac{I_C}{\alpha V_T} = \frac{I_C}{V_T}$$


since $\frac{\beta}{1+\beta} = \alpha$

at $\beta = \frac{\alpha}{1-\alpha} \Rightarrow \beta - \beta\alpha = \alpha = \beta = \beta\alpha + \alpha = (1+\beta)\alpha \Rightarrow \alpha = \beta/(1+\beta)$

for $y_{12} = \frac{i_b}{v_{ce}} \Big|_{v_{be}=0} = 0$ as i_b is independent of v_{ce} if $v_{be}=0$

$y_{22} = \frac{i_c}{v_{ce}} \Big|_{v_{be}=0} = \frac{\text{current in } g_C}{v_{ce}} = g_C$ (if $y_{12}=0$)
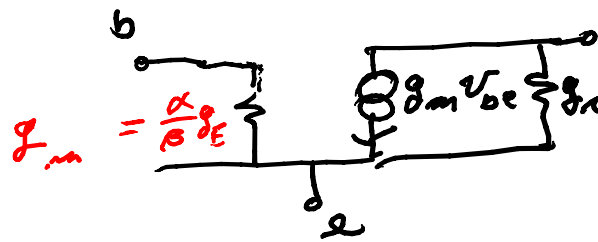
$$\Rightarrow Y = \begin{bmatrix} \frac{I_C}{\beta V_T} & 0 \\ \frac{I_C}{V_T} & \frac{I_C}{V_A} \end{bmatrix}$$



$$g_m \approx g_{21} = \frac{I_C}{V_T}$$

$$y_{11} = \frac{\text{current } i_b}{v \text{ on the diode}}$$

$$= \frac{-\alpha/\beta I_E}{v_{be}} = \frac{\alpha}{\beta} \cdot g_E = \frac{I_C}{\beta V_T} = \frac{g_m}{\beta}$$

$$i_b = \frac{i_c}{\beta}$$

$$\Rightarrow Y = I_C \begin{bmatrix} 1/\beta V_T & 0 \\ 1/V_T & 1/V_A \end{bmatrix} = \begin{bmatrix} g_m/\beta & 0 \\ g_m & g_m \frac{V_T}{V_A} \end{bmatrix} = g_m \begin{bmatrix} 1/\beta & 0 \\ 1 & V_T/V_A \end{bmatrix}$$