
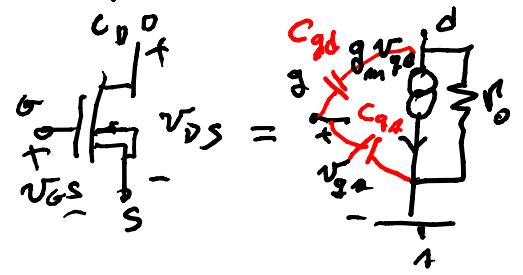


MOS

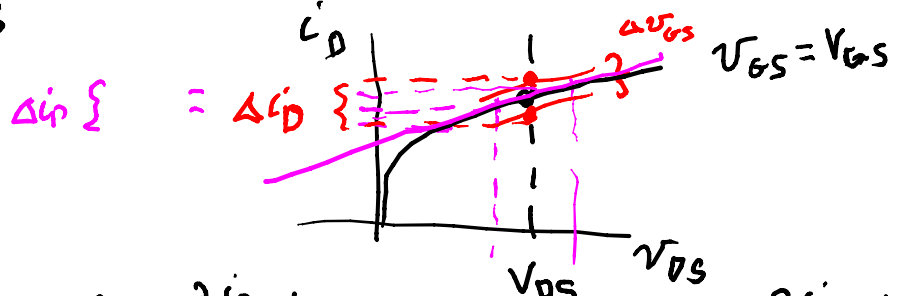




$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{DS}=V_{DS}, Q} \quad g_o = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{GS}=V_{GS}, Q} \quad r_o = \frac{1}{g_o}$$

in saturation

$$i_D = \frac{K_P}{2} \cdot \frac{W}{L} (v_{GS} - V_{th})^2 (1 + \lambda v_{DS})$$

$$\frac{\partial i_D}{\partial v_{GS}} = 2 \left(\frac{K_P W}{2 L} \right) \frac{(v_{GS} - V_{th})^2 (1 + \lambda v_{DS})}{(v_{GS} - V_{th})} \Big|_Q = \frac{2 I_D}{(v_{GS} - V_{th})} = \frac{2 I_D}{V_{ov}}$$

$$\frac{\partial i_D}{\partial v_{DS}} = \frac{K_P W}{2 L} (v_{GS} - V_{th})^2 \lambda \Big|_Q = \frac{I_D \times \lambda}{1 + \lambda v_{DS}} \approx \lambda I_D$$

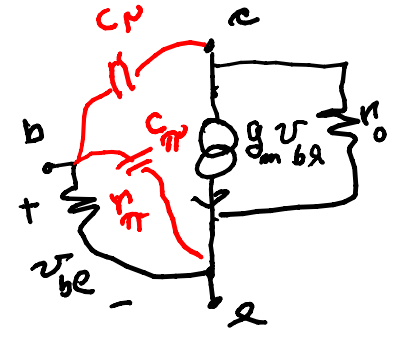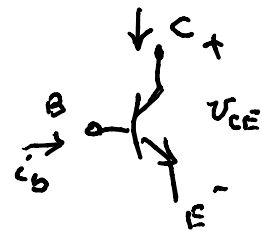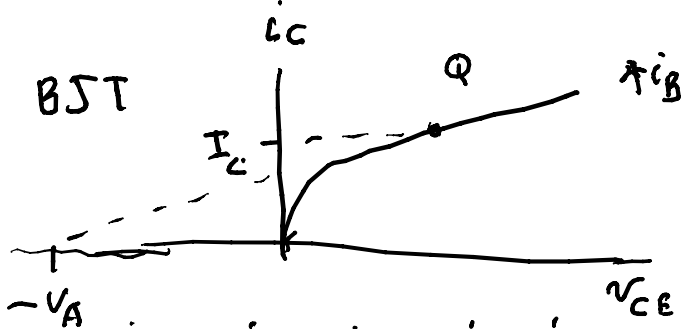

Equivalent circuit

$$i_C = \beta i_B, \quad i_E = -i_C - i_B = -(1 + \beta) i_B$$

BE diode; $i_{diode} = I_{SE} (e^{v_{BE}/V_T} - 1) \approx I_{SE} e^{v_{BE}/V_T}$ in forward active region

$$\frac{\partial(-i_E)}{\partial v_{BE}} = \frac{\partial i_{diode}}{\partial v_{BE}} \Big|_Q = \frac{i_{diode}}{V_T} \Big|_Q = \frac{-i_E}{V_T} = \frac{(1 + \beta) I_B}{V_T} \approx \frac{I_C}{V_T}; \quad \frac{\partial i_C}{\partial v_{BE}} = \frac{I_C}{\beta V_T} = g_{m\pi}$$

and $g_m = \frac{I_C}{V_T}, \quad g_o = \frac{I_C}{V_A}, \quad V_T = \frac{kT}{|q|} \approx 26mV @ room T$
 $V_A = \text{Early voltage}$

$$g_{m\pi} = \frac{\partial i_b}{\partial v_{be}} = \frac{g_m}{\beta} = \frac{I_C}{\beta V_T}$$



$$Y(s) = \begin{bmatrix} g_m + sC_{gs} + sC_{gd} & 0 - sC_{gd} \\ g_m - sC_{gd} & g_o + sC_{gd} \end{bmatrix}$$

BJT

$$Y(s) = \begin{bmatrix} s(C_{gs} + C_{gd}) & -sC_{gd} \\ g_m - sC_{gd} & g_o + sC_{gd} \end{bmatrix}$$

MOS

Bias

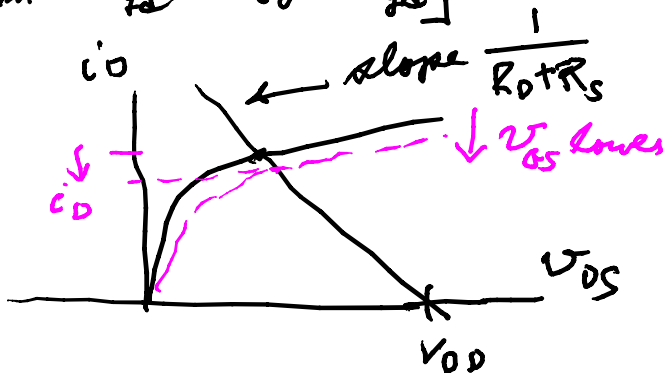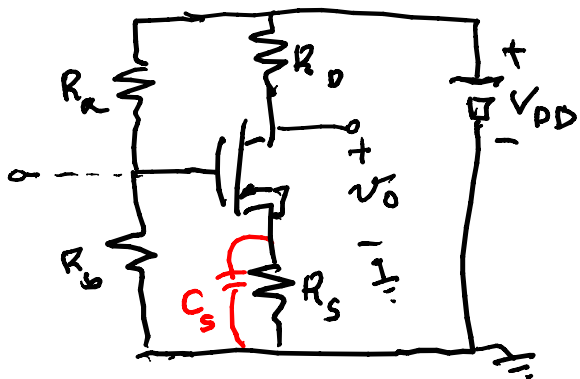

R_s stabilizes thermal behavior



for signal choose C_s large so R_s is shorted.

@ DC C_s is open so does not affect bias.

Effective input voltage, $V_{gs} = \frac{R_b}{R_a + R_b} V_{DD} = \frac{1}{1 + \frac{R_a}{R_b}} V_{DD}$

input $R_{in} = \frac{R_a R_b}{R_a + R_b} = \frac{R_a}{1 + R_a/R_b}$ to keep large choose R_a large (10 Meg Ω)


Biasing the BJT

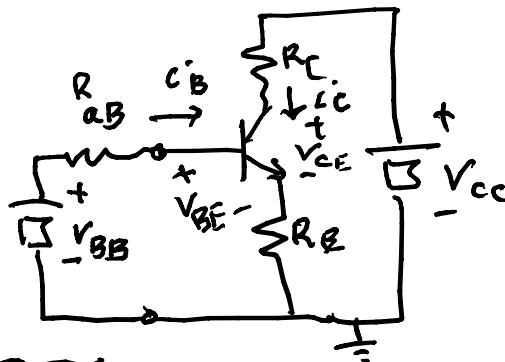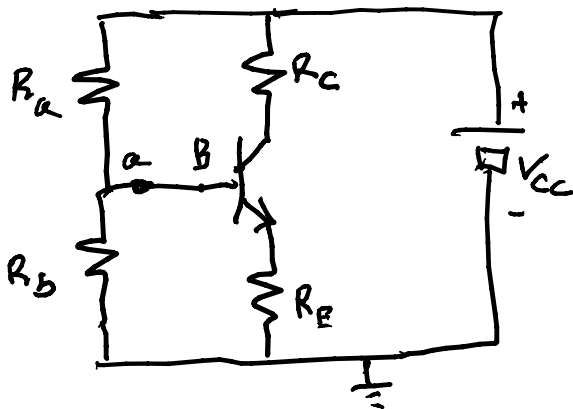

Thevenin's equivalent

$$V_{oc} = \frac{R_b}{R_a + R_b} V_{CC} \Rightarrow Z_{th} = R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{R_a R_b}{R_a + R_b}$$

$$I_{sc} = V_{CC} / R_a$$

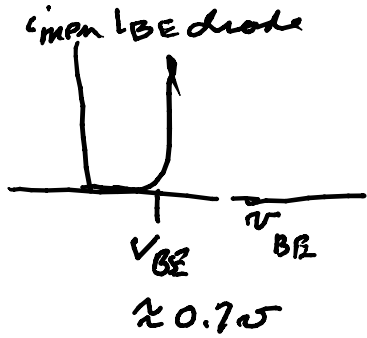

if choose V_{BE} then can find I_B from KVL around the BE loop

$$-V_{BB} + R_{\alpha B} I_B + V_{BE} + R_E (-I_E)$$

" I_C/α

usually choose R_E



gives again 1 eq in 2 unknowns, R_a & R_b

choose one, say R_b in Meg Ω 's then have 1 eq. 1 unknown

(need $R_a > 0$)

gain $\frac{v_o}{v_i} = -g_m R_{Load} = -\frac{I_C}{V_T} R_C$ if bypass R_S

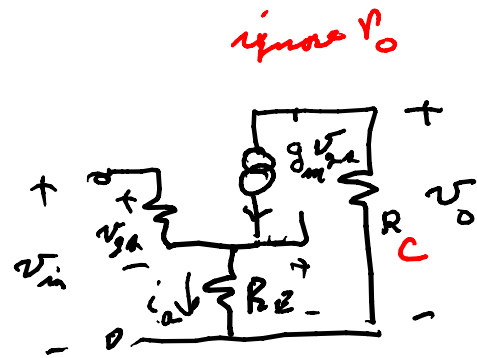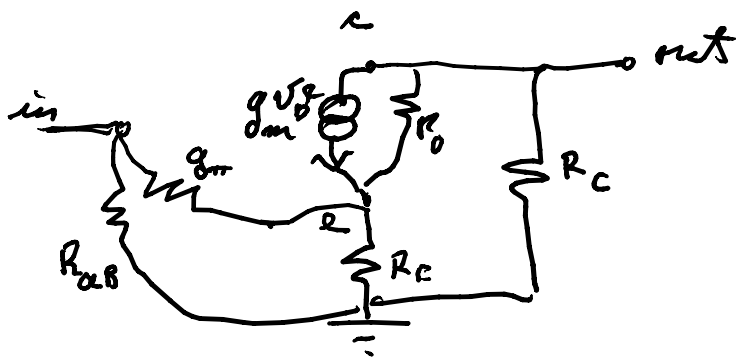look at equivalent circuit with R_S present



$$R_E i_a = v_{in} - v_{g_e}$$

$$R_E G_E = (g_m v_{g_a} + g_m v_{g_e}) R_E$$

$$\hat{=} (g_m R_E) v_{g_a}$$

$$\Rightarrow v_{in} = (1 + g_m R_E) v_{g_a}$$

$$v_o = -g_m R_C v_{g_e} = \frac{-g_m R_C v_{in}}{1 + g_m R_E}$$

$$\frac{v_o}{v_{in}} = -g_m \frac{R_C}{1 + g_m R_E} \quad \} \text{ feedback factor}$$