
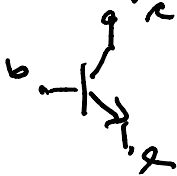


BJT high frequency

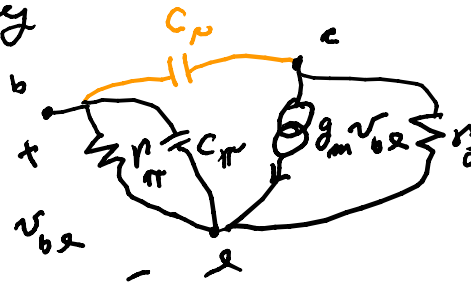

small signal
 fwd bias BE
 back bias BC




A.711

$$g_{\pi} = \frac{I_C}{\beta_0 V_T}, \quad g_m = \frac{I_C}{V_T}$$

$$= \frac{g_m}{\beta_0}, \quad g_o = \frac{I_C}{V_A}$$

$$\frac{i_c}{i_b} \Big|_{\text{short } R_L}$$

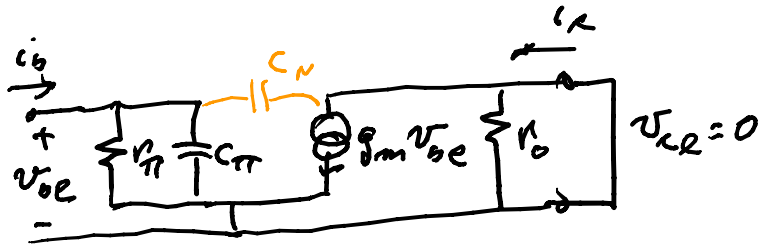

$$i_b = \frac{v_{be}}{g_{\pi}} = (g_{\pi} + sC_{\pi}) v_{be}$$

$$i_c = g_m v_{be} - sC_{\mu} v_{be}$$

$$= g_m \cdot \frac{1}{g_{\pi} + sC_{\pi}} \cdot i_b$$


$$\Rightarrow \frac{i_c}{i_b} = \beta(s) = \frac{g_m}{g_{\pi} + sC_{\pi}} = \frac{g_m/g_{\pi}}{1 + s(C_{\pi}/g_{\pi})} = \frac{\beta_0}{1 + s(C_{\pi}/g_{\pi})}$$

$$\beta_0 = \beta(0) = \beta \Big|_{@ DC}; \quad \beta(s) = |\beta(s)| e^{j\Delta\phi(s)} = \frac{\beta_0}{1 + j\omega(C_{\pi}/g_{\pi})}$$

stops working $|\beta(s)|$ drops to 1;

$$|\beta(s)| = \frac{\beta_0}{\sqrt{1 + \omega^2(C_{\pi}/g_{\pi})^2}} \Rightarrow 1 = \frac{\beta_0^2}{1 + \omega_T^2(C_{\pi}/g_{\pi})^2} = \beta_0^2$$



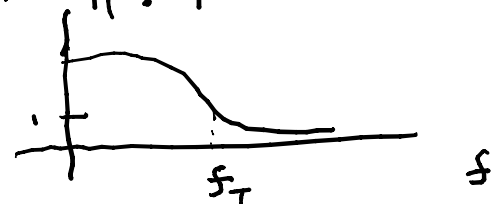
$$\Rightarrow \omega_T^2 = \frac{\beta_0^2}{(C_{\pi}/g_{\pi})^2} \Rightarrow f_T = \frac{1}{2\pi} \frac{\beta_0}{(C_{\pi}/g_{\pi})}$$



practical f_T is in Meg Hz.

" transition frequency

Current mirror p.533

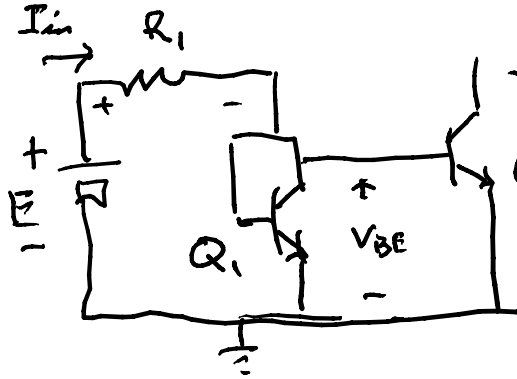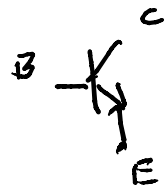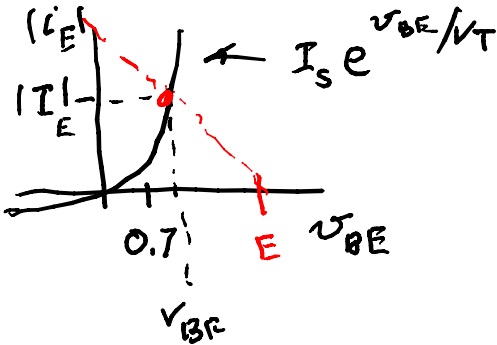


$I_0 = I_{in}$ if $\beta_1 = \beta_2$
 back bias CB

(current sink)
 uses n-p-n


(current source)
 uses p-n-p

$v_{BE} \approx 0.7V$ $I_{in} = G_1 (E - v_{BE}) \Rightarrow G_1 = \frac{1}{R_1} = \frac{I_{in}}{E - 0.7}$

Current source that sources current

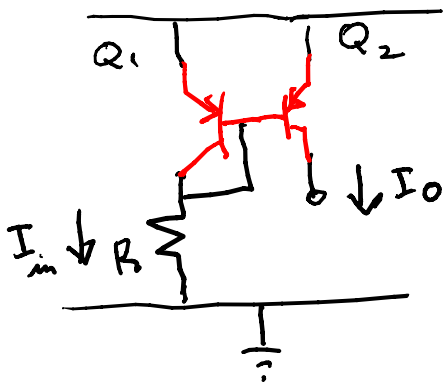

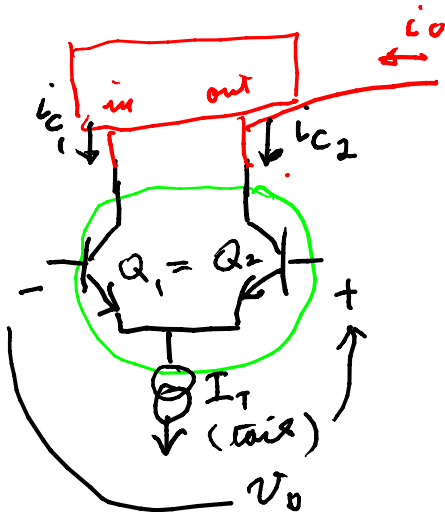Differential pair, BJT p.613, eq. 616, active load p.645



if i_{B1} & i_{B2} are small

KCL: $i_{c1} + i_{c2} = I_T$

$i_{c1} = \alpha |i_{E1}|$, $i_{c2} = \alpha |i_{E2}|$

$v_o = v_{BE2} - v_{BE1}$

$|i_E| = I_s e^{v_{BE}/V_T}$ if forward bias BE

$$i_{c1} = \alpha I_S e^{v_{BE1}/V_T} \quad i_{c2} = \alpha I_S e^{v_{BE2}/V_T}$$


$$\frac{i_{c2}}{i_{c1}} = \frac{e^{v_{BE2}/V_T}}{e^{v_{BE1}/V_T}} = e^{(v_D/V_T)} \Rightarrow I_T = \left(1 + \frac{i_{c2}}{i_{c1}}\right) \cdot i_{c1}$$

$$\Rightarrow i_{c1} = \frac{I_T}{1 + e^{v_D/V_T}} ; i_{c2} = \frac{I_T \cdot e^{v_D/V_T}}{1 + e^{v_D/V_T}}$$


$$i_o = i_{c2} - i_{c1} = \left(\frac{i_{c2}}{i_{c1}} - 1\right) i_{c1} = (e^{v_D/V_T} - 1) \cdot i_{c1} ; \tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{e^{2x} - 1}{e^{2x} + 1}$$

$$\frac{i_o}{I_T} = \frac{e^{v_D/V_T} - 1}{1 + e^{v_D/V_T}} \cdot \frac{i_{c1}}{i_{c1}} = \tanh\left(\frac{v_D}{2V_T}\right)$$
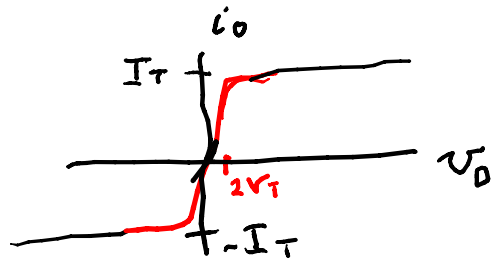
$$i_o = I_T \tanh\left(\frac{v_D}{2V_T}\right)$$




02/24/12

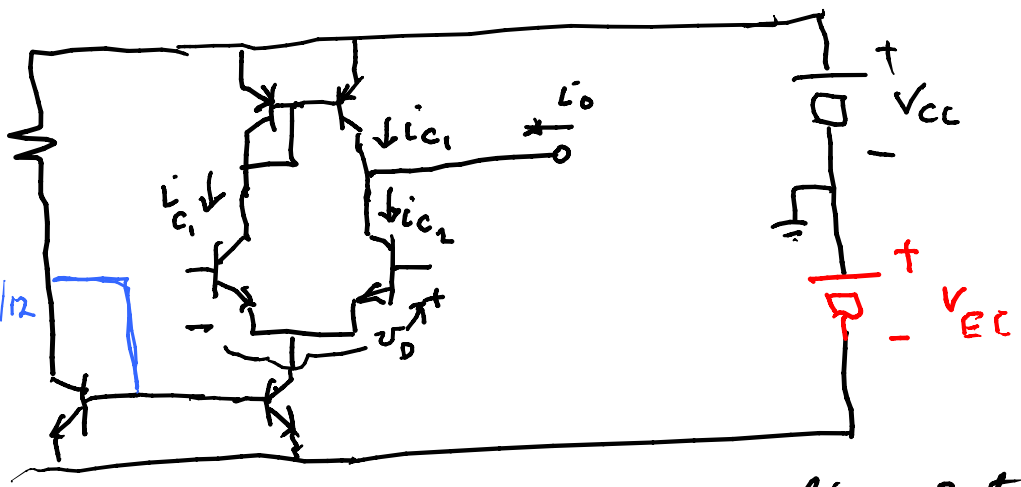

this is an OTA = operational transconductance amplifier

$$i_o = I_T \tanh\left(\frac{v_D}{2V_T}\right)$$

To get a good multiplier

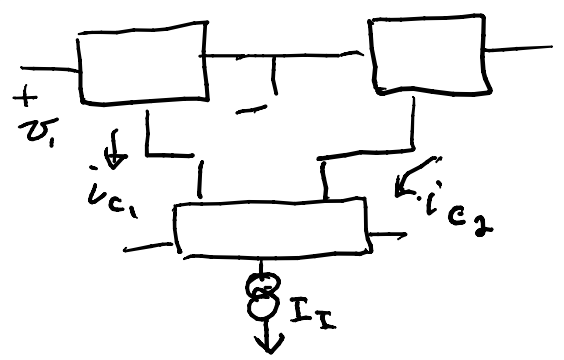

can get
$$i_o = I_T \tanh\left(\frac{v_{D1}}{2V_T}\right) \tanh\left(\frac{v_{D2}}{2V_T}\right)$$

