


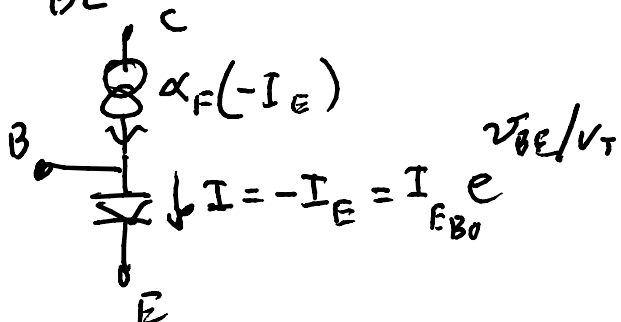


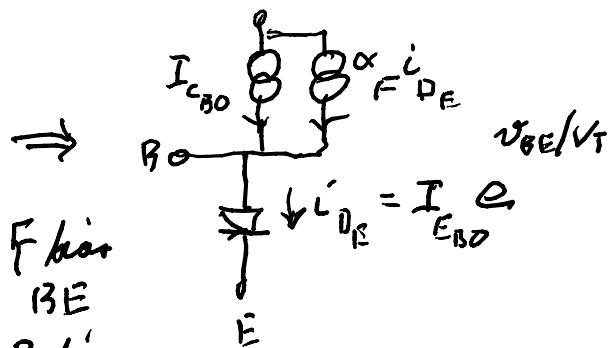

Ebers-Mell

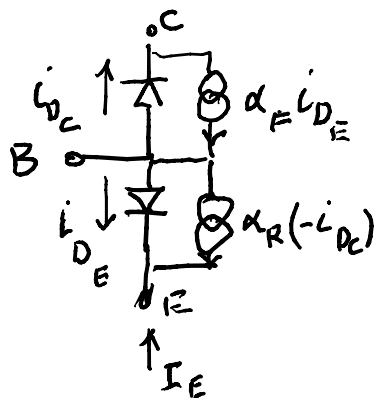

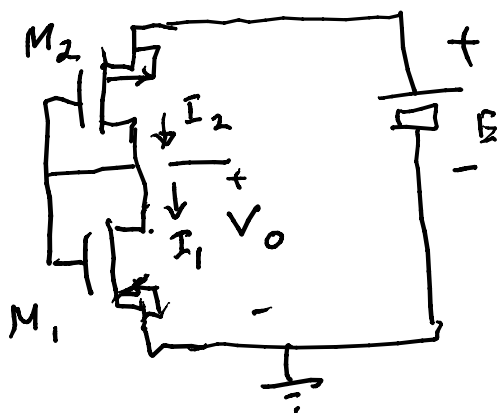Use of CMOS for creating currents & voltages



to see transistors are in saturation (for enhancement mode devices)
 $V_{GS} - V_{TO} \leq V_{DS}$

for M_1 : $V_{GS} = V_0 = V_{GS}$

$V_{GS} - V_{TO} = V_0 - V_{TO} < V_{DS}$

for M_2 : $E - V_0 = V_{SD} = V_{SG}$

$V_{SG} - V_{TOp} > V_{SD}$ but $V_{TOp} < 0$

$$I_1 = \frac{K_{Pm}}{2} \left(\frac{W}{L}\right)_m (V_0 - V_{TOm})^2$$

$$K_{Ch} = I_2 = \frac{K_{Po}}{2} \left(\frac{W}{L}\right)_p (E - V_0 - |V_{TOp}|)^2 \Rightarrow \text{yields } V_0$$

$$\beta = \frac{K_P W}{2 L}$$

$$\sqrt{\beta_m} \cdot (V_0 - V_{TOm}) = \sqrt{\beta_p} (E - V_0 - |V_{TOp}|)$$

$$V_0 - V_{TOm} = \sqrt{\frac{\beta_p}{\beta_m}} (E - |V_{TOp}|) - \sqrt{\frac{\beta_p}{\beta_m}} \cdot V_0$$


$$(1 + \sqrt{\beta_p/\beta_n}) V_0 = V_{TO_n} - \sqrt{\beta_p/\beta_n} |V_{TO_p}| + \sqrt{\beta_p/\beta_n} E$$

$$V_0 = \frac{1}{1 + \sqrt{\beta_p/\beta_n}} \cdot E + \left(\frac{V_{TO_n} - \sqrt{\beta_p/\beta_n} |V_{TO_p}|}{1 + \sqrt{\beta_p/\beta_n}} \right)$$


if given V_0 can design the transistors by adjusting the W/L's

$$\frac{\beta_n}{\beta_p} = \frac{(E - V_0 - |V_{TO_p}|)^2}{(V_0 - V_{TO_n})^2}$$


To make a current source



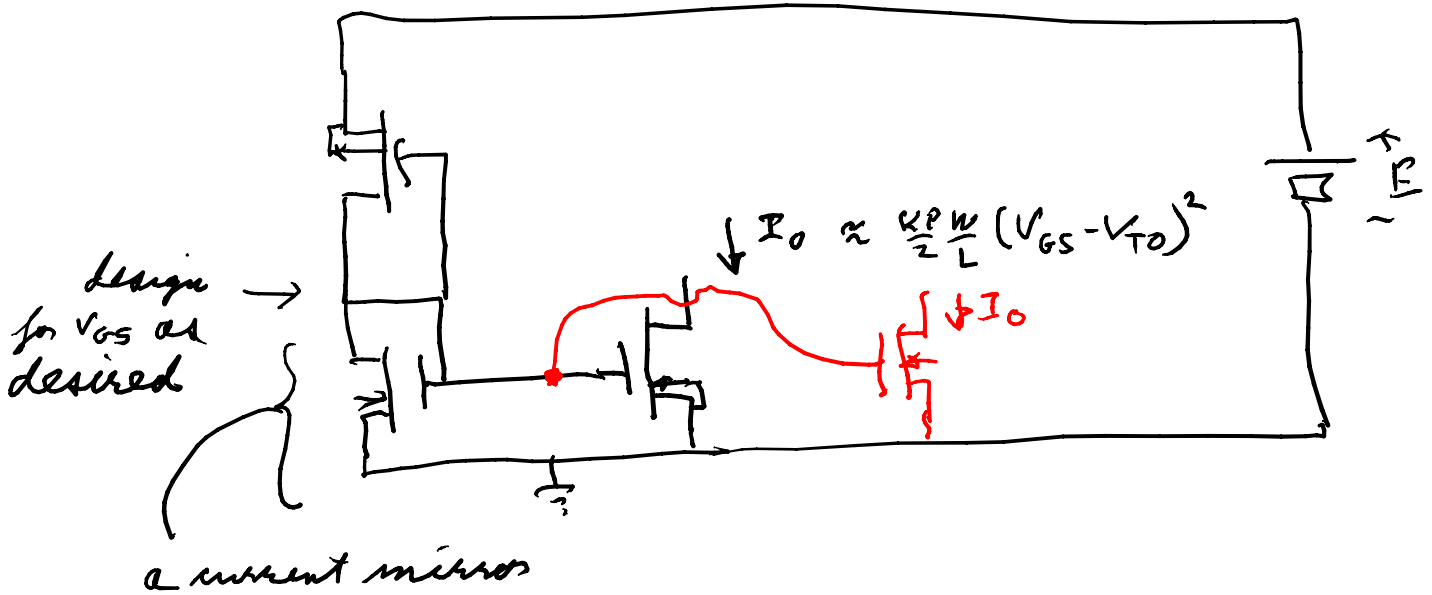


Look at the CMOS inverters

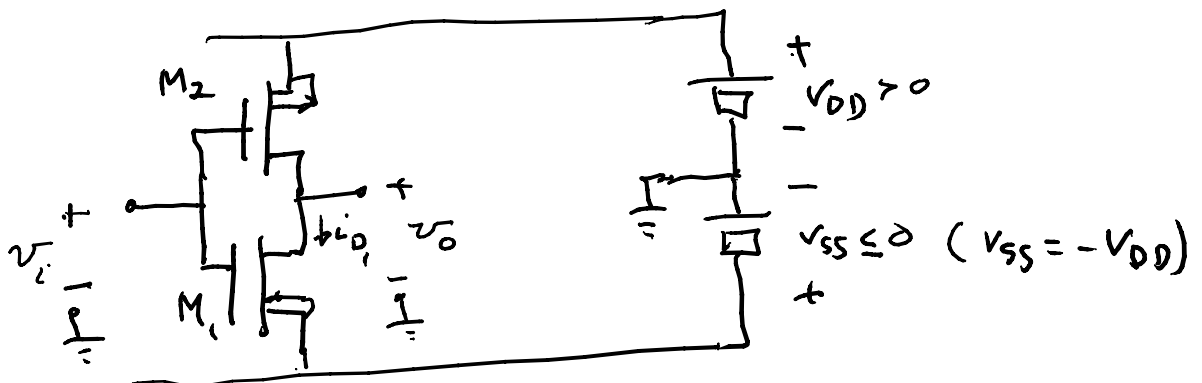

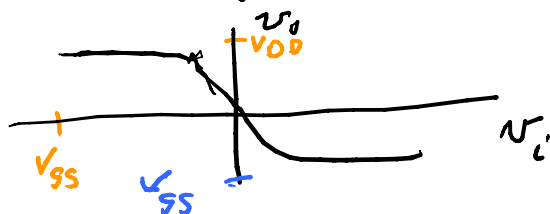
Design for $v_o = 0$ if $v_i = 0$ (by choice of W/L's)



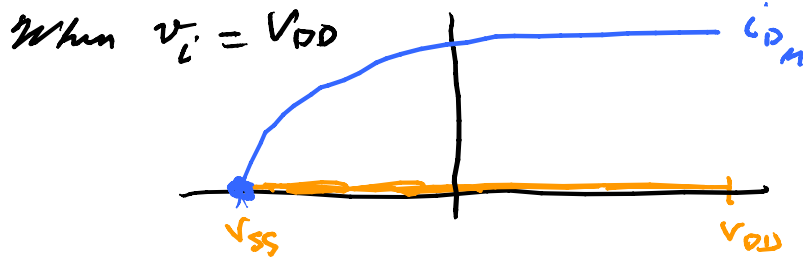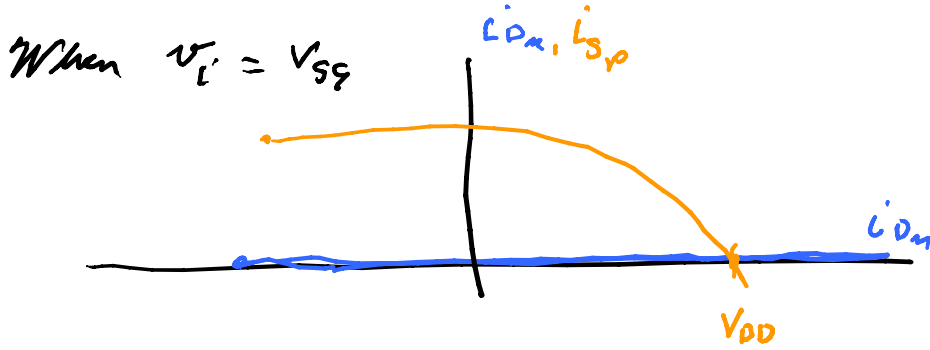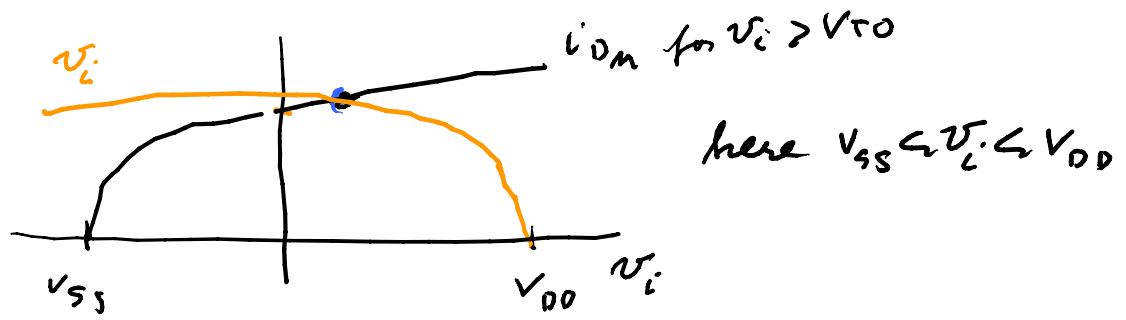


In the two rest points of v_{SS} & v_{DD} no current flows as one of M_1 or M_2 is turned off.

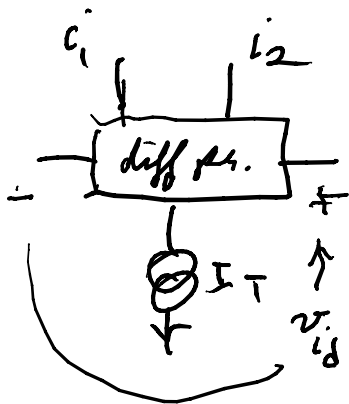
Multiplicities from the differential pair



B3T: $i_2 - i_1 = I_T \tanh(v_{id}/2V_T)$

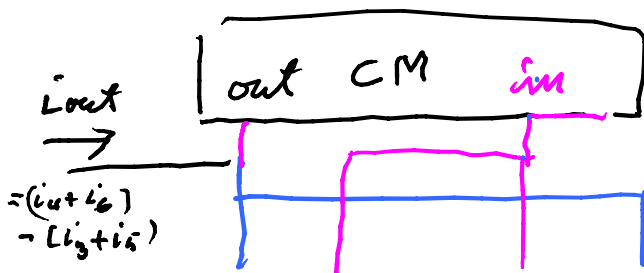(gives a 2 quadrant multiplier if vary I_T)



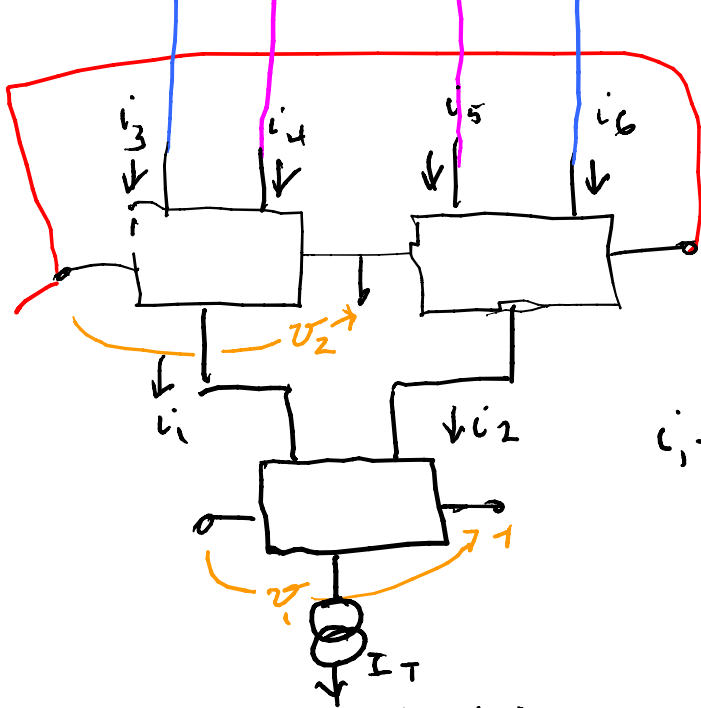

$$i_4 - i_3 = i_1 \tanh(v_2 / 2V_T)$$

$$i_5 - i_6 = i_2 \tanh(v_2 / 2V_T)$$

diff

$$i_1 - i_2 = I_T \tanh(v_1 / 2V_T)$$

$$\underbrace{(i_4 - i_3) - (i_5 - i_6)}_{\text{net KCL}} = (i_1 - i_2) \tanh(v_2 / 2V_T) = I_T \tanh(v_1 / 2V_T) \tanh(v_2 / 2V_T) = i_0$$

for small $i_0 \approx I_T \cdot \frac{v_1}{2V_T} \cdot \frac{v_2}{2V_T}$

