

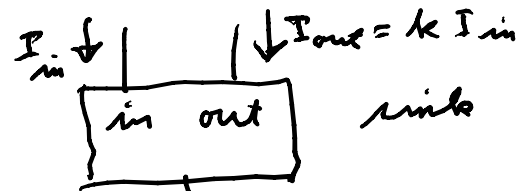
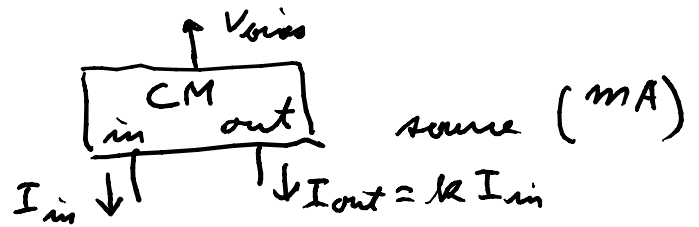
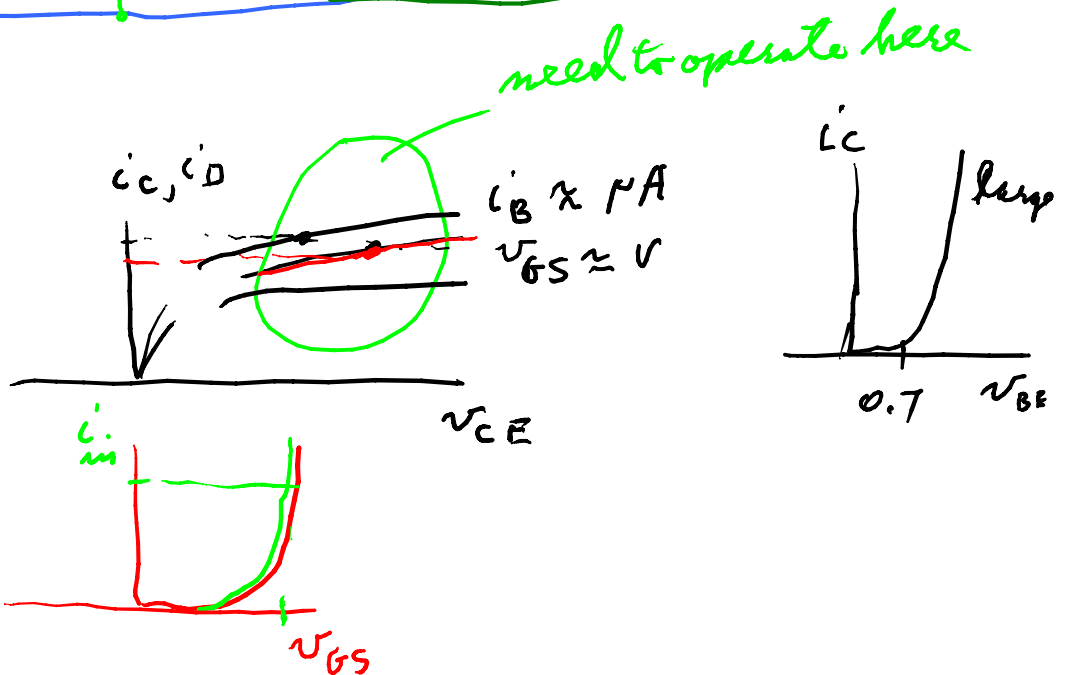



Homework due on W.  
Current mirror CM

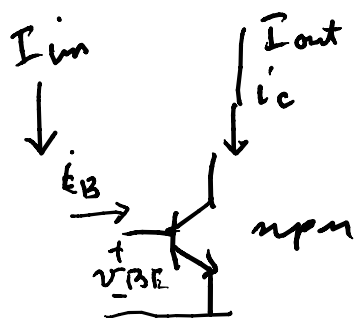

for MOS  
sink  
NMOS

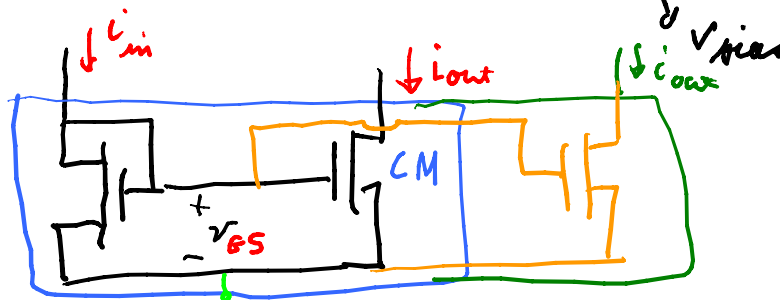

BJT  
sink

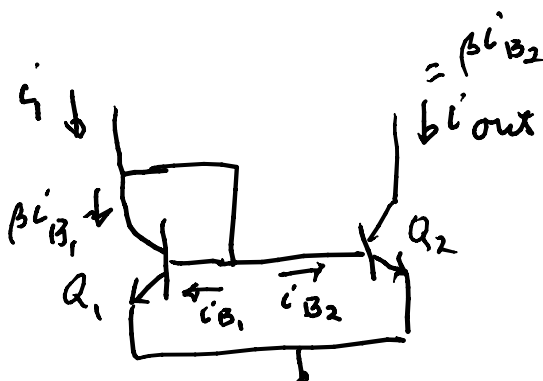


$$i_{in} = i_i = \beta i_{B1} + i_{B1} + i_{B2}$$



if  $Q_2 = Q_1$ ,  $i_{B2} = i_{B1}$ ,  $\beta_1 = \beta_2 = \beta$

$$\left. \begin{aligned} i_{in} &= (2 + \beta) i_{B2} \\ i_{out} &= \beta i_{B2} \end{aligned} \right\} \frac{i_{out}}{i_{in}} = \frac{\beta}{2 + \beta}$$


BJT current "source"

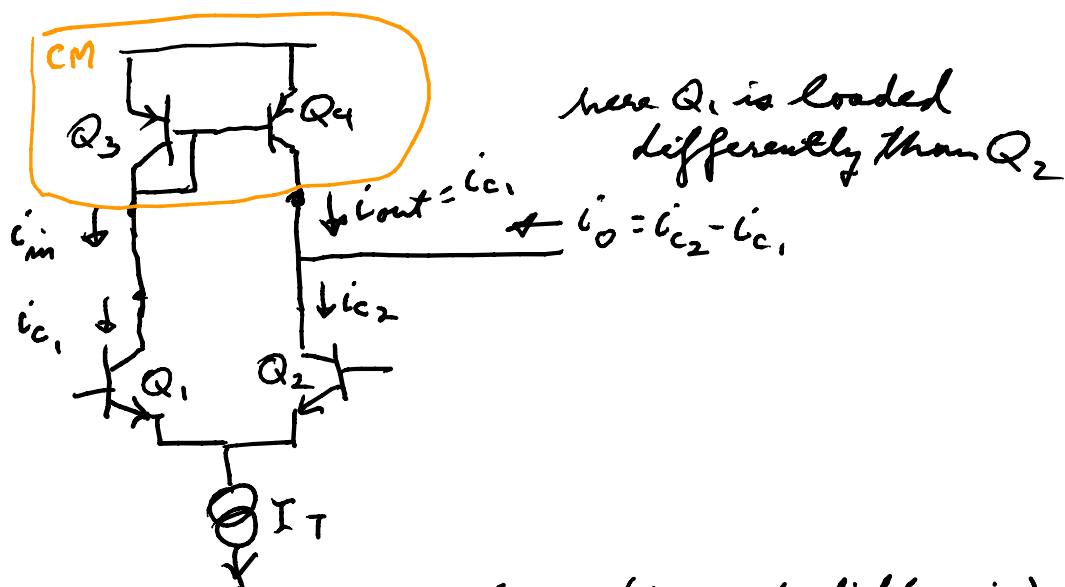

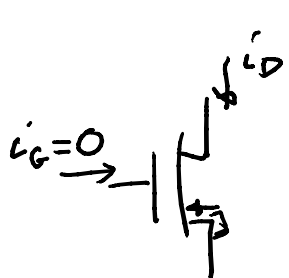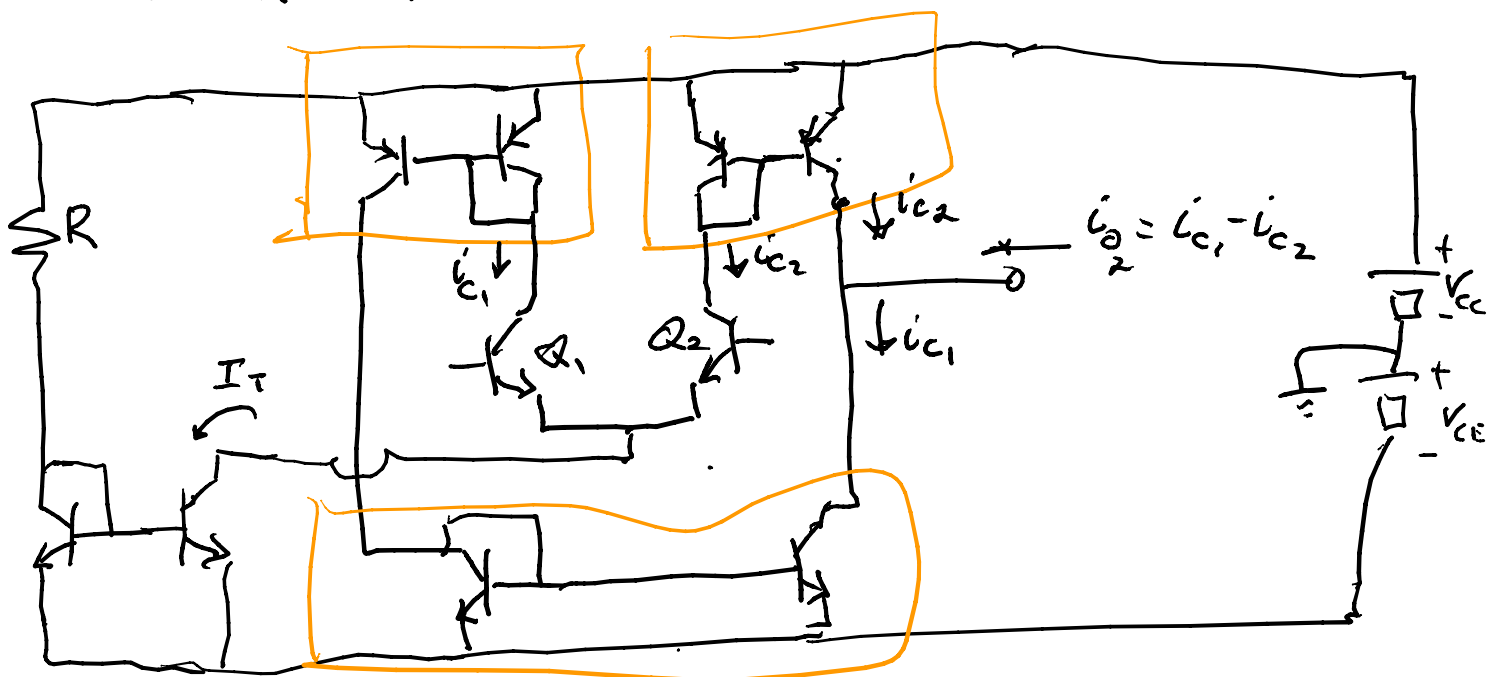∴ make  $Q_1$  &  $Q_2$  see the same load (ie on the diff. pair)



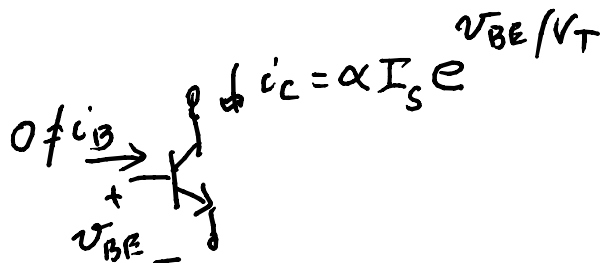subthreshold  
 $i_G = 0$  @ DC  
 $(V_{GS} - V_{T0})/V_T$   
 $i_D = \frac{K_P W}{2 L} e$   
 $V_{GS} > V_{T0}$   
 $V_{GS} - V_{T0} < V_{DS}$



means an OTA operating in subthreshold  
 $(I_T \sim 10^{-12} A)$  has  $i_o = I_T \tanh(V_D/2V_T)$

For small signals  $\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} \approx \frac{(1+x) - (1-x)}{(1+x) + (1-x)} = \frac{2x}{2} = x$


acts as a resistor

$i_o \sim I_T \cdot v_d / 2V_T = \frac{I_T}{2V_T} \cdot v_d \approx G_m \sim 10^{-10}$

small signal

Oscillators:

Feedback: via signal graph

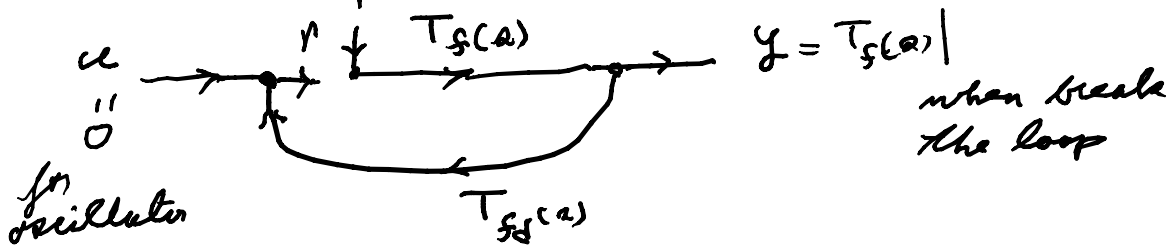


$\rho = \text{return ratio} = T_{Sd} \cdot T_S(s) = \text{loop gain}$

close the loop and then  $1 = \rho = T_{Sd} \cdot T_S(s)$


$\therefore$  desire  $1 - \text{loop gain} = 0 = 1 - T_{Sd}(s) \cdot T_S(s)$

we want those  $s$  which satisfy this

look at the RC phase shift oscillator

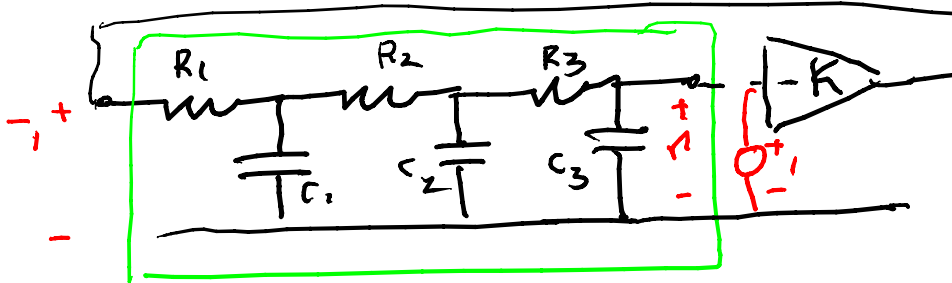

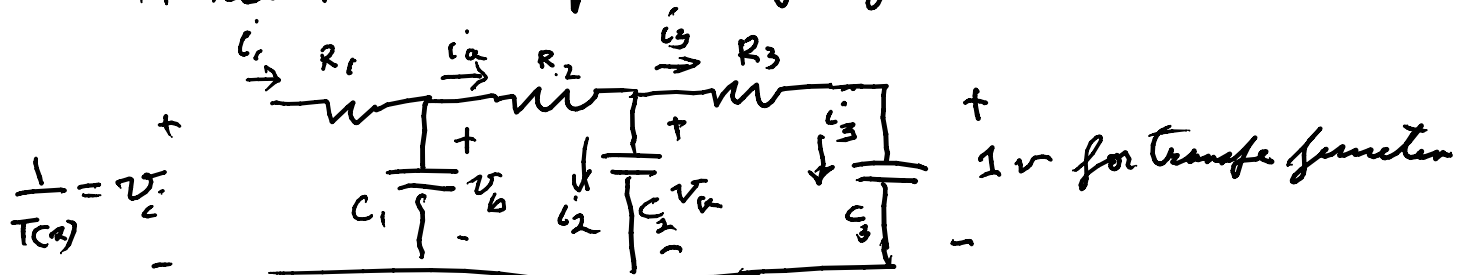$\therefore$  want the voltage transfer function of the ladder



$i_3 = \Delta C_3$

$v_a = R_3 i_3 + 1 = \Delta R_3 C_3 + 1$

$i_2 = \Delta C_2 v_a = \Delta^2 R_3 C_3 C_2 + \Delta C_2$

$$i_a = i_2 + i_3 = a^2 R_3 C_3 C_2 + a C_2 + a C_3$$

$$V_b = R_1 i_a + V_a = a^2 R_3 C_3 R_2 C_2 + a R_2 C_2 + a R_2 C_3 + a R_3 C_3 + 1$$

$$i_1 = i_a + a C_1, V_b = a^2 R_3 C_3 C_2 + a(C_2 + C_3) + a^3 R_3 C_3 R_2 C_2 C_1 \\ + a^2 R_2 C_2 C_1 + a^2 R_2 C_3 C_1 + a^2 R_3 C_3 C_1 + a C_1$$

$$V_{in} = R_1 i_1 + V_b = a^2 R_1 R_3 C_3 C_2 + a(C_2 R_1 + C_3 R_1) + a^3 R_3 C_3 R_2 C_2 R_1 C_1 \\ + a^2 R_2 C_2 R_1 C_1 + a^2 R_2 C_3 R_1 C_1 + a^2 R_3 C_3 R_1 C_1 + a C_1 R_1 \\ + a^2 R_3 C_3 R_2 C_2 + a R_2 C_2 + a R_2 C_3 + a R_3 C_3 + 1$$

$$V_{in}(s) = \frac{1}{T(s)} = (R_1 C_1 R_2 C_2 R_3 C_3) a^3 + (R_1 C_2 R_3 C_3 + R_1 C_1 R_2 C_2 + R_1 C_1 R_2 C_3 + R_1 C_1 R_3 C_3 \\ + R_2 C_2 R_3 C_3) a^2 \\ + (R_1 C_2 + R_1 C_3 + R_1 C_1 + R_2 C_2 + R_2 C_3 + R_3 C_3) a + 1$$

= -K for oscillations (when close the loop)