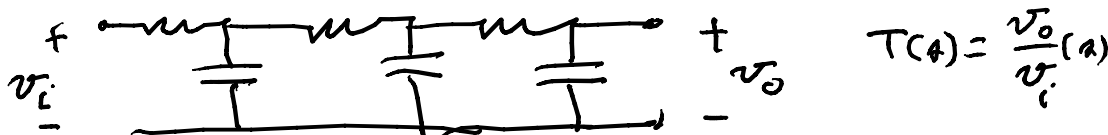


$$V_{in}(s) = \frac{1}{T(s)} = (R_1 C_1 R_2 C_2 R_3 C_3) s^3 + (R_1 C_2 R_3 C_3 + R_1 C_1 R_2 C_2 + R_1 C_1 R_2 C_3 + R_1 C_1 R_3 C_3 + R_2 C_2 R_3 C_3) s^2 + (R_1 C_2 + R_1 C_3 + R_1 C_1 + R_2 C_2 + R_2 C_3 + R_3 C_3) s + 1$$

= -K for oscillations (when close the loop)



$$T(s) = \frac{v_o(s)}{v_i(s)}$$

as $s \rightarrow \infty$



$v_o \rightarrow 0$ as 3rd power of s


$$T(s) \sim \frac{ks}{s^3} \Rightarrow \text{low pass}$$

if $C_1 = C_2 = C_3 = C$
if $R_1 = R_2 = R_3 = R$

$$T(s) = \frac{1}{R^3 C^3 s^3 + 5R^2 C^2 s^2 + 6RCs + 1}$$

here $k = 1/R^3 C^3$

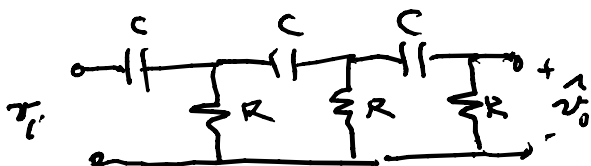
if $R \rightarrow \frac{1}{CA}, C \rightarrow \frac{1}{R}$




$$\hat{T}(s) = \frac{\hat{v}_o}{\hat{v}_i} = \frac{1}{(\frac{1}{CA})^3 (\frac{1}{R})^3 + 5(\frac{1}{CA})^2 (\frac{1}{R})^2 + 6\frac{1}{CA} \frac{1}{R} + 1} = \frac{1}{C^3 R^3 s^3 + 5C^2 R^2 s^2 + 6C R s + 1}$$

here as $s \rightarrow \infty$ we get $\frac{1}{C^3 R^3}$

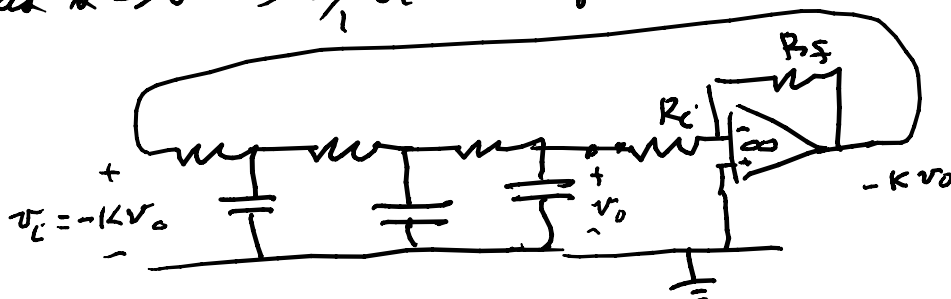as $s \rightarrow 0 \rightarrow 0^3$ or a 3rd zero at DC \Rightarrow high pass



need $R_i \rightarrow \infty$

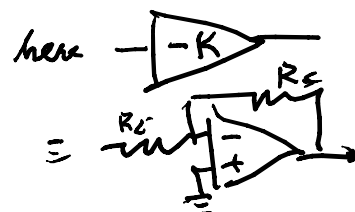

$$\frac{v_o}{v_i} = -R_f/R_i = -K$$

$$T(s) = \frac{v_o}{v_i} = \frac{v_o}{-Kv_o} = -\frac{1}{K} \Rightarrow \text{for behavior } \frac{1}{T(s)} = -K$$

$$1 + 6RCs + 5R^2C^2s^2 + R^3C^3s^3 = -K$$

For sinusoids, a sine wave oscillator, $s = j\omega$

$$1 + j6RC\omega - 5R^2C^2\omega^2 - jR^3C^3\omega^3 = -K$$

$$\text{Re: } 1 + K - 5R^2C^2\omega^2 = 0$$


$$\text{Im: } 6RC\omega - R^3C^3\omega^3 = 0 \Rightarrow \text{if } \omega \neq 0 \text{ \& } RC \neq 0 \Rightarrow 6 - R^2C^2\omega^2 = 0$$

$$\omega_0^2 = \frac{6}{R^2C^2} ; \quad 1 + K = 5R^2C^2 \times \frac{6}{R^2C^2} = 30 \Rightarrow K = 29$$

we can design for a given $\omega \Rightarrow s^2 + \omega_0^2$ is a factor of the degree three polynomial $\frac{1}{T(s)} + K = P(s)$

$$P(s) = K + \frac{1}{T(s)} = (s^2 + \omega_0^2)(s + \sigma_0)K_0$$

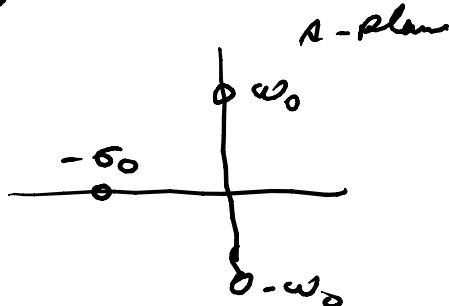$s + \sigma_0$ found by long division of $s^2 + \omega_0^2$ into $P(s)$



This is for low pass ladder

For high pass one

$$-K = \frac{1}{\hat{T}(s)} = \frac{1 + 5\hat{C}\hat{R}s + 6\hat{C}^2\hat{R}^2s^2 + \hat{R}^3\hat{C}^3s^3}{\hat{R}^3\hat{C}^3s^3} \Rightarrow$$

$$\left(K\hat{C}^3\hat{R}^3s^3 + \hat{R}^3\hat{C}^3s^3 + 5\hat{C}\hat{R}s \right) + (1 + 6\hat{C}^2\hat{R}^2s^2) = \hat{P}(s)$$

$$\text{desire } \hat{P}(s) = 0 ; \quad \hat{P}(s) = \hat{P}(s) + \sum \hat{P}(s)$$

$$s = j\omega \quad \text{or: } j\omega(-\omega^2(K+1)\hat{C}^3\hat{R}^3 + 5\hat{C}\hat{R}) = 0$$

$$\text{or: } 1 - 6\hat{C}^2\hat{R}^2\omega^2 = 0$$

$$\hat{\omega}_0^2 = \frac{1}{6\hat{R}^2\hat{C}^2}$$

$$; \quad -\omega^2(K+1)\hat{C}^3\hat{R}^3 + 5\hat{C}\hat{R} = 0$$

$$\equiv -(K+1)\frac{\hat{C}\hat{R}}{6} + 5\hat{C}\hat{R} = 0 \Rightarrow K+1 = 30$$

$$K = 29$$

$$\hat{P}(s) = (s^2 + \hat{\omega}_0^2)(s + \hat{\sigma}_0)\hat{K}_0$$


$$\text{Ex: } R = 20K\Omega, \quad C = 10nF \Rightarrow RC = 2 \times 10^4 \times 10 \times 10^{-9} \\ = 2 \times 10^{-4} \Rightarrow 4 \times 10^{-8} = RC^2$$

$$\hat{\omega}_0^2 = \frac{1}{6 \times 4 \times 10^{-8}}$$

$$\hat{\omega}_0 = \frac{1}{2\sqrt{6}} \times 10^4$$

$$\hat{f}_0 = \frac{1}{2\pi} \times \frac{1}{2\sqrt{6}} \times 10^4 = \frac{10,000}{31} \approx 325 \text{ Hz}$$


To make a negative resistor

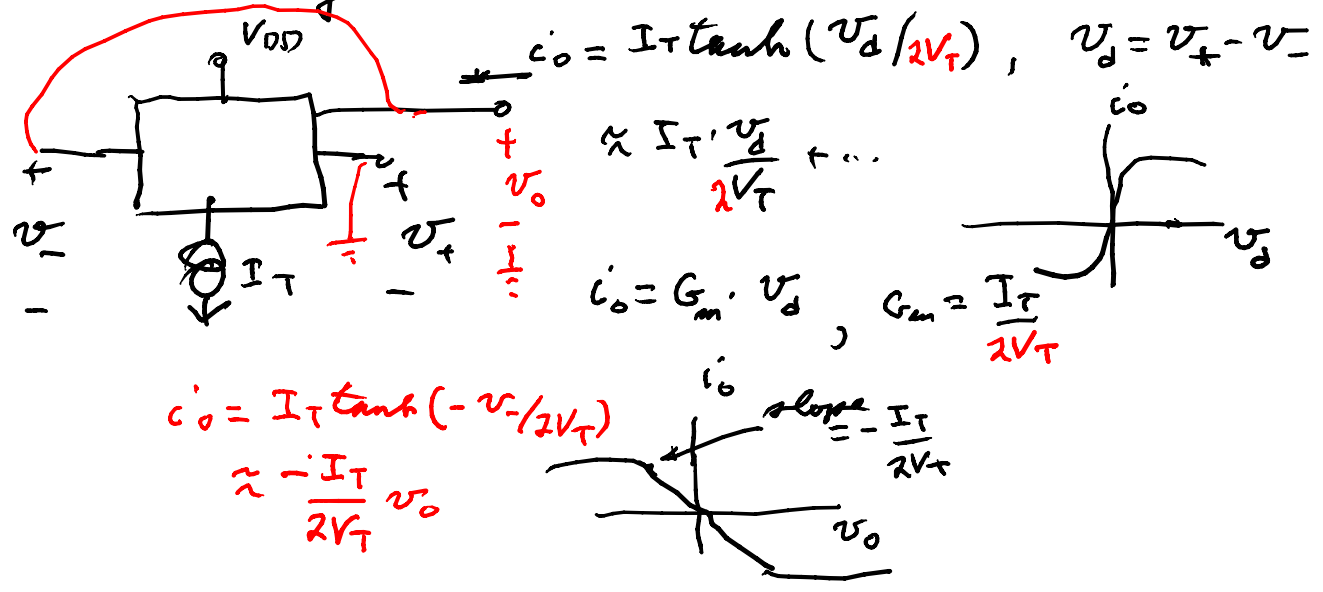

⇒ a negative resistor
 $i = g v$, $g < 0$

(result ⇒ "any" linear circuit can be made with OTA's and capacitors)


pass transistors p. 1153

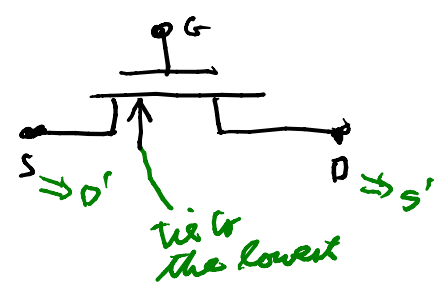

off if $v_{GS} < V_{th}$, ⇒ v_G small ⇒ $D \rightarrow S = \text{open}$

if $v_G = \text{large}$ ⇒ $D \rightarrow S$ like a short & current flows

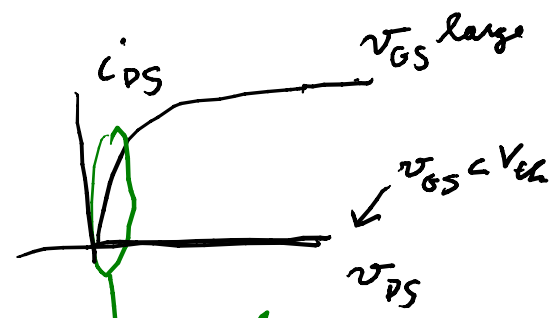stops signal from S to D if G is a binary 0



desire to operate here as then the voltage difference from S to D is small

then passes signal from S to D if G is a binary 1

