

Exam next period open book, open notes

pages in book summer, p. 66

phase shift oscillator, p. 1345

MOS inverter, p. 1070

& CMOS region

CMOS inverter, p. 1089-1098


+ related topics as
CMOS eqs.

diode, p. 175,

BJT, p. 367, Table 6.2

Hybrid- π , BJT, p. 708

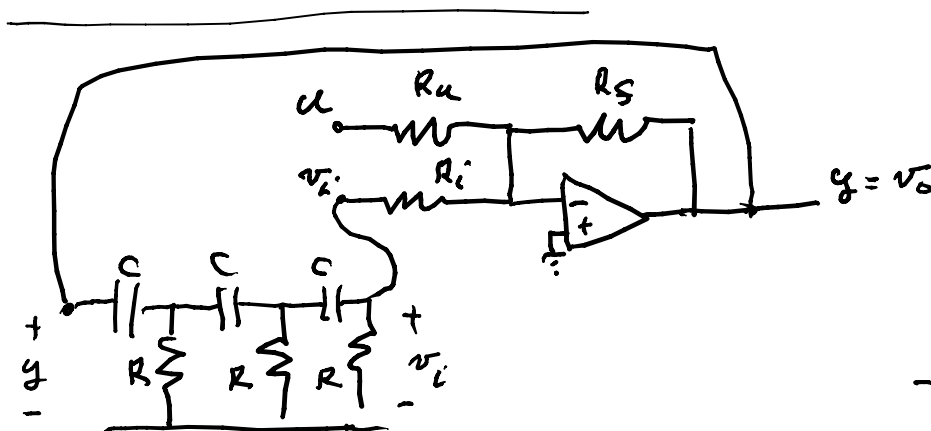MOS, p. 290, Table 7.A.3 = p. 558
Table 5.3



$$+ \frac{1}{-j} C \quad i = C \frac{dv}{dt} = CA \cdot v$$

$$y = -\frac{R_S}{R_u} u - \frac{R_S}{R_i} v_i$$

$$-\frac{R_S}{R_u} = -K_u \quad -K = -R_S/R_i$$

$$y = -\frac{R_S}{R_u} u - \frac{R_S}{R_i} T(\omega) \cdot y \Rightarrow (1 + K T(\omega)) y = -K_u \cdot u$$

$$\frac{y}{u} = \frac{-K_u}{1 + K T(\omega)} \quad ; \quad T(\omega) = \frac{(CRA)^3}{(CRA)^3 + 6(CRA)^2 + 5(CRA) + 1}$$

$$p = CRA \quad \frac{y}{u} = \frac{-K_u}{1 + \frac{p^3 K}{p^3 + 6p^2 + 5p + 1}} = \frac{-K_u (p^3 + 6p^2 + 5p + 1)}{(1+K) p^3 + 6p^2 + 5p + 1}$$

$$((1+K)p^3 + 6p^2 + 5p + 1) y = -K_u (p^3 + 6p^2 + 5p + 1) u$$

oscillator has $u=0$ need $y(0), y'(0), y''(0)$

define $P(p) = (1+k)p^3 + 6p^2 + 5p + 1$, to satisfy $P(p) = 0$ so
 $P(p) \neq 0$

define $p_0 = j\omega_0$

$$-j\omega^3(1+k) - 6\omega^2 + 5j\omega + 1 = 0 \Rightarrow \begin{cases} -6\omega^2 + 1 = 0 \\ \& -\omega^2(1+k) + 5 = 0 \end{cases}$$


$$\omega_0^2 = 1/6, \quad \frac{1}{6}(1+k) = 5 \cong 30 = 1+k \Rightarrow k = 29$$

$$y(t) = C_1 e^{j\sqrt{1/6}t} + C_1^* e^{-j\sqrt{1/6}t} + C_2 e^{-6_0 t}$$

$$P(p) = (30p^3 + 6p^2 + 5p + 1) = (p^2 + 1/6)(p + 6_0) \cdot 30$$

$$= 29p^3 + \dots + \frac{6_0}{6} 30 \Rightarrow 1 = \frac{6_0}{6} \times 30 \Rightarrow 6_0 = 1/5$$

Inverters: CMOS

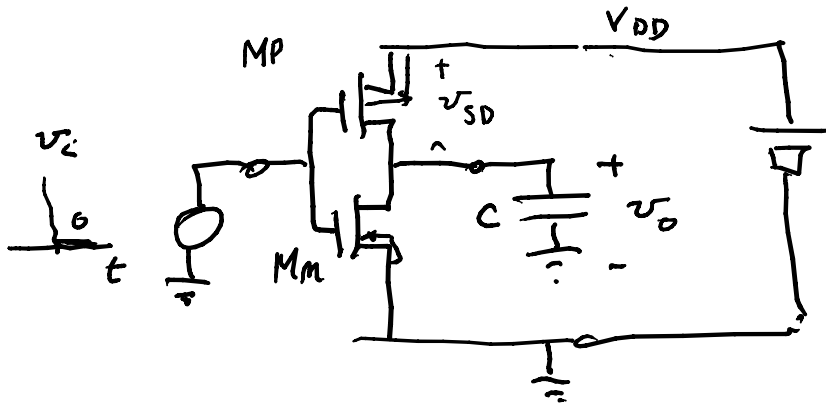

$$v_o(0) = 0$$

$$v_{SG_p}(0) = V_{DD} \rightarrow \text{on all the way}$$

$$v_{GS_n}(0) = 0 \Rightarrow \text{off}$$

$$v_{SD_p}(0) = V_{DD}$$

check state of M_p (M_n is off) at $t=0$

$$v_{SD} \text{ vs } v_{SG} - |V_{th_p}| \quad \text{starts out in saturation}$$

$$\begin{matrix} v_{SD} \\ \parallel \\ v_{DD} \end{matrix} \quad \begin{matrix} v_{SG} \\ \parallel \\ v_{DD} \end{matrix} \quad i_D = C \frac{dv_o}{dt} = \frac{K P_p W}{2 L} (V_{DD} - V_{th})^2 \quad (\text{gives a linear in } t \text{ charge})$$

after awhile, eventually $v_{SD}(t) = v_o(t) < v_{SG} - V_{th} = V_{DD} - V_{th}$


then goes into ohmic range


$$i_D = C \frac{dv_o}{dt} = \frac{K P_p W}{2 L} (2(V_{DD} - V_{th})v_o - v_o^2)$$

a Riccati equation

\therefore a very nonlinear system

look at small signal behavior of this inverter



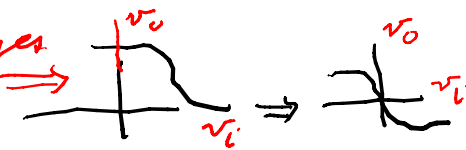
shift apts. by bias voltages \Rightarrow 

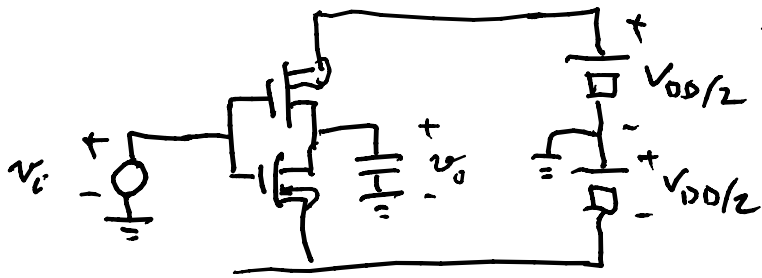

biases the transistors at $V_{GS_n} = -V_{GS_p} = V_{DD}/2$

for small signals replace transistors by their linear equivalent circuits

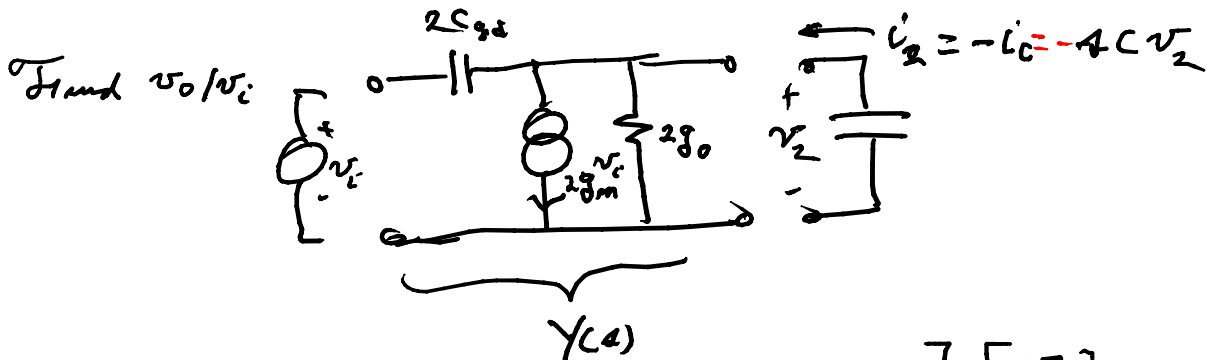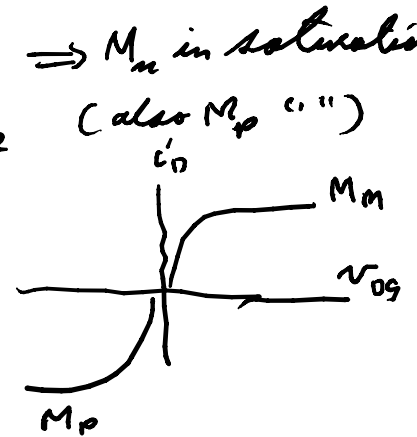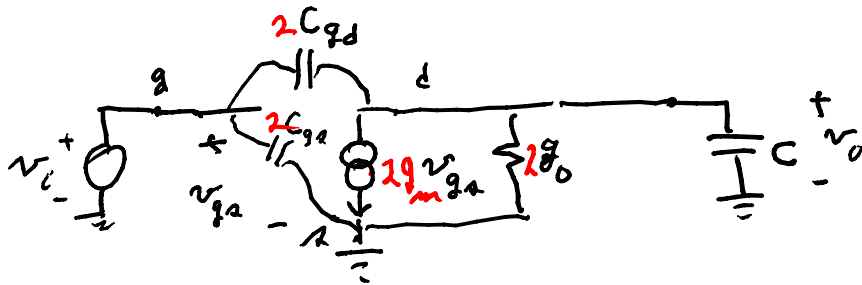
here at the bias point $V_{GS} - V_{th} < V_{DS} \Rightarrow M_n$ in saturation (also M_p)



$$Y(s) = \begin{bmatrix} 2sC_{gd} & -2C_{gd}s \\ g_m - 2sC_{gd} & 2g_o + 2sC_{gd} \end{bmatrix} \begin{bmatrix} v_i \\ v_2 \end{bmatrix}$$

$$i_2 = (g_m - 2sC_{gd}) v_i + (2g_o + 2sC_{gd}) v_2 = -4C v_2$$


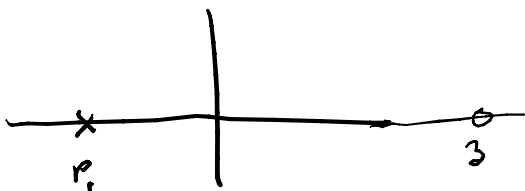
$$\Rightarrow \frac{v_2}{v_i} = \frac{(g_m - 2sC_{gd})}{-4(2C_{gd} + C - 2g_o)} = - \frac{(g_m - 2sC_{gd})}{2g_o + 4(2C_{gd} + C)}$$



$$pole = p_1 = - \frac{2g_o}{2C_{gd} + C}$$

$$zero = z_1 = + \frac{g_m}{2C_{gd}}$$

Biasing for a current source, npn or pnp

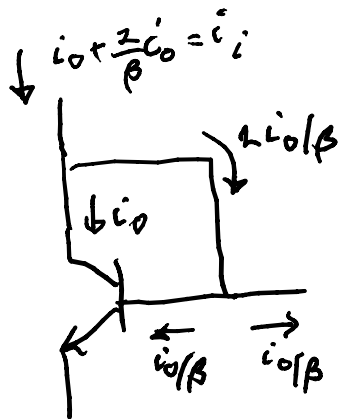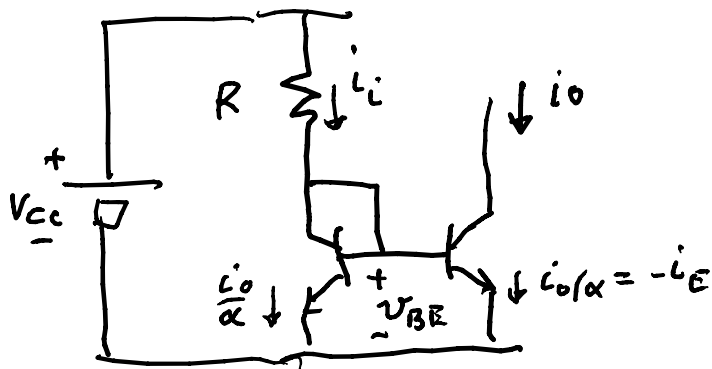

$$iR = V_{CC} - v_{BE}$$

$$\frac{i_C}{\alpha} \approx I_S \left(e^{v_{BE}/V_T} - 1 \right) \approx I_S e^{v_{BE}/V_T}$$

ignore if $i_C > 0$

$$v_{BE} = V_T \ln \left(\frac{i_C/\alpha}{I_S} \right) \approx V_T \ln \left(\frac{i_C}{I_S} \right)$$

for Q 2N3904, $I_S = 650.5 \times 10^{-18}$

if $i_C = 6.5 \text{ mA}$ then $\frac{i_C}{I_S} = \frac{6.5 \times 10^{-3}}{6.5 \times 10^{-16}} = 10^{+13}$

$$v_{BE} = 26 \times 10^{-3} \times \ln 10^{13} = 26 \times 10^{-3} \times (6 \times \ln 100 + \ln 10)$$