

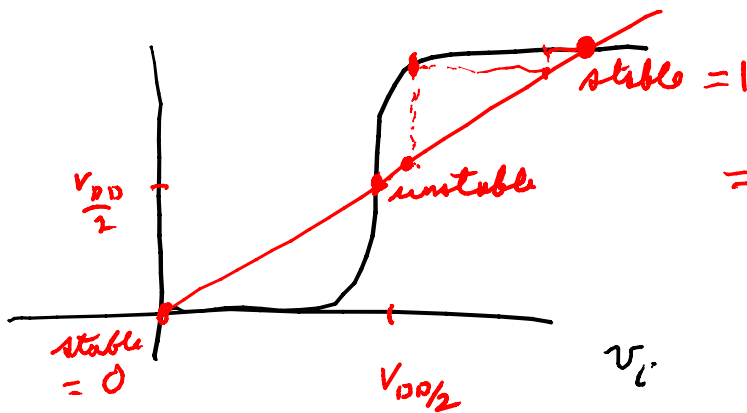
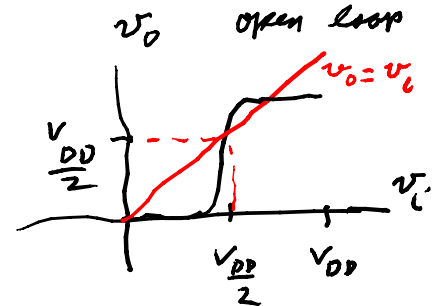
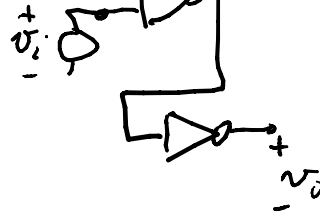


P. 1205 latch

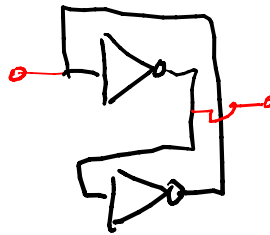

⇒ SRAM p. 1218

Van der Pol oscillator

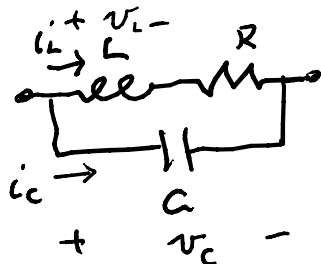

$$i_c = C \frac{dv_c}{dt} = -i_L \quad \text{KCL}$$

$$v_L = L \frac{di_L}{dt} = v_c - Ri_L \quad \text{KVL}$$

laws of components laws of connection

$$C \frac{dv_c}{dt} = -i_L$$

$$L \frac{di_L}{dt} = v_c - Ri_L$$

→

$$C \frac{d^2 v_c}{dt^2} = -\frac{di_L}{dt} = -\frac{1}{L} v_c + \frac{R}{L} (-C \frac{dv_c}{dt})$$

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0 \Rightarrow \left(a^2 + \frac{R}{L} a + \frac{1}{LC} \right) v_c = 0$$

to get $v_c(t) = v_c e^{at}$

$$\pm v_c a^2 e^{at} + \frac{R}{L} v_c e^{at} + \frac{1}{LC} v_c e^{at} = 0 \Rightarrow \left(v_c a^2 + \frac{R}{L} v_c + \frac{1}{LC} v_c \right) e^{at} = 0$$

if $v_c \neq 0$, e^{at} never zero $\Rightarrow a^2 + \frac{R}{L} a + \frac{1}{LC} = 0$

$$= a^2 + \frac{\omega_0}{Q} a + \omega_0^2 = 0, \quad Q \approx \frac{1}{R}$$

$$P(s) = s^2 + \frac{R}{L}s + \frac{1}{LC}$$


$\underbrace{\frac{1}{LC}}_{\omega_0^2}$

if $R=0 \Rightarrow s^2 + \omega_0^2 = 0$


$$s = \pm j\omega_0$$

if $R \neq 0 \Rightarrow s_{1,2} = \frac{-R}{2L} \pm \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 - 4/LC}$
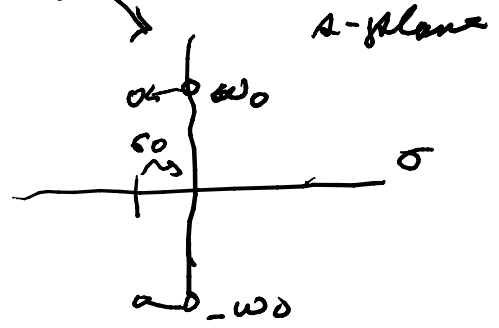
$$= \sigma_0 \pm j(\omega_0 - \epsilon)$$



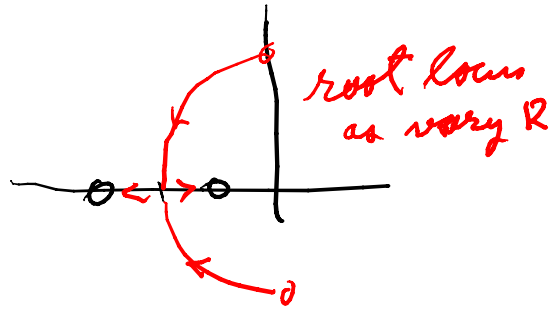If R is large $s_{1,2} = \sigma_0 \pm \sigma_0'$



$$A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



$$\ddot{y} + \epsilon(y^2 - 1)\dot{y} + \omega_0^2 y = 0$$

$$\frac{d}{dt}(\dot{y} + \epsilon f(y)) = \dot{y} + \epsilon \frac{df(y)}{dy} \dot{y}$$

Van der Pol oscillator
nonlinear with a
limit cycle
structurally stable


$$x = \dot{y}$$

$$\dot{x} = \ddot{y} = -\epsilon(y^2 - 1)x - \omega_0^2 y$$


$$\dot{y} = x$$

$$\dot{x} = -\epsilon(y^2 - 1)x - \omega_0^2 y$$


} state variable equation

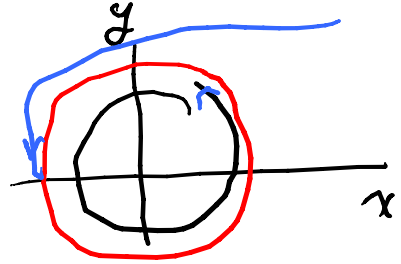



We can make with OTA's & C's

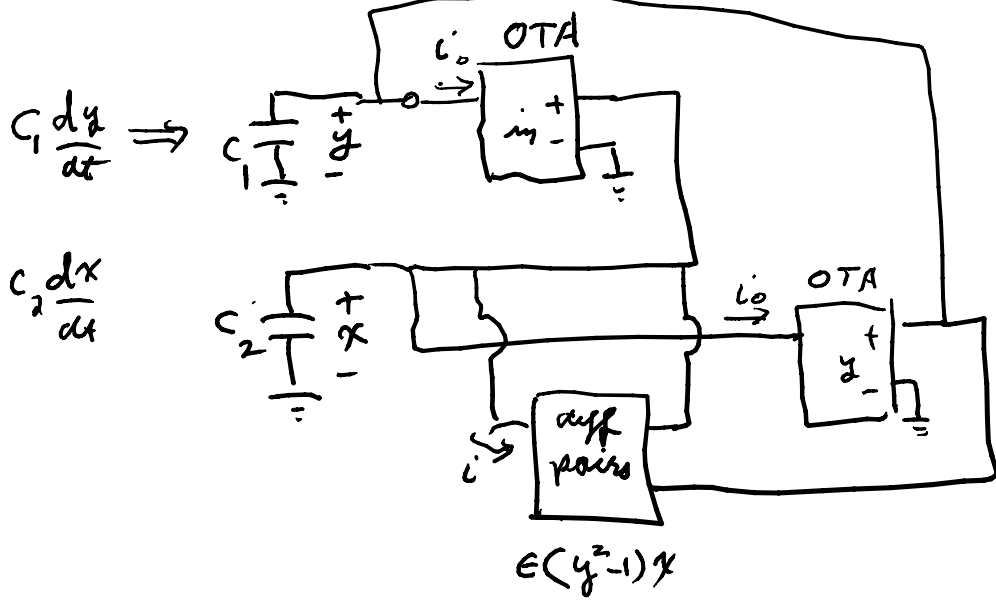

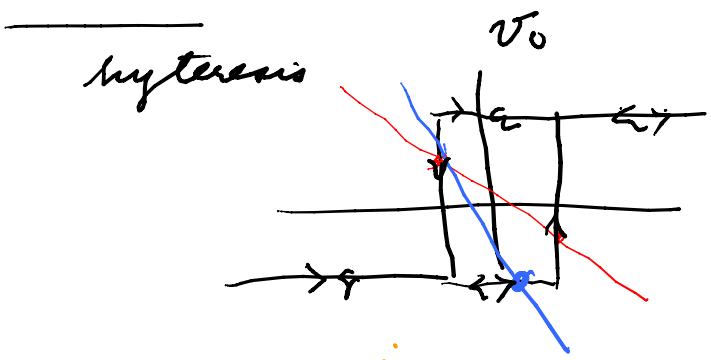In Spice G components are voltage in current out & beautifully there is the G value which allows to type in function.



Schmitttrigger
S. 1358

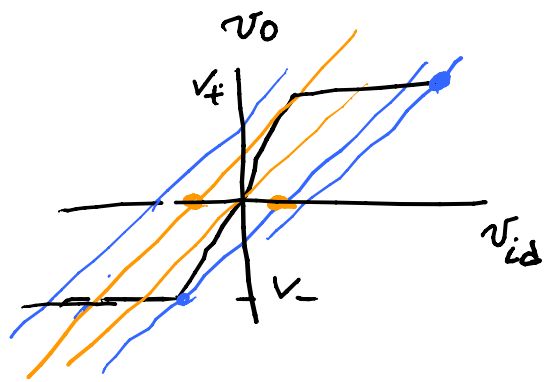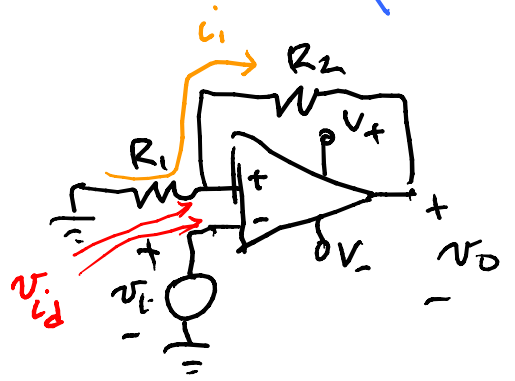

$$v_o = f(v_{id})$$

$$0 = R_1 i_1 + v_{i1} + v_i \quad (1)$$

$$0 = -v_i - v_{id} + R_2 i_1 + v_o \quad (2)$$


add

$$0 = R_1 i_1 + R_2 i_1 + v_o \quad (3)$$



$$\Rightarrow i_1 = -\frac{v_o}{R_1 + R_2} \quad (3')$$

$$(3') \Rightarrow (1) \Rightarrow 0 = -v_o \times \frac{R_1}{R_1 + R_2} + v_{id} + v_i$$
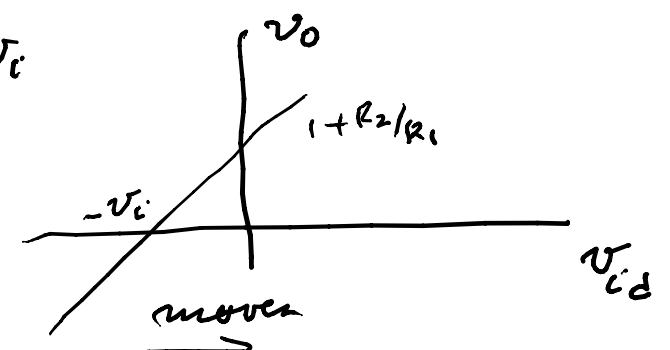
$$v_o = \left(1 + \frac{R_2}{R_1}\right)(v_{id} + v_i)$$



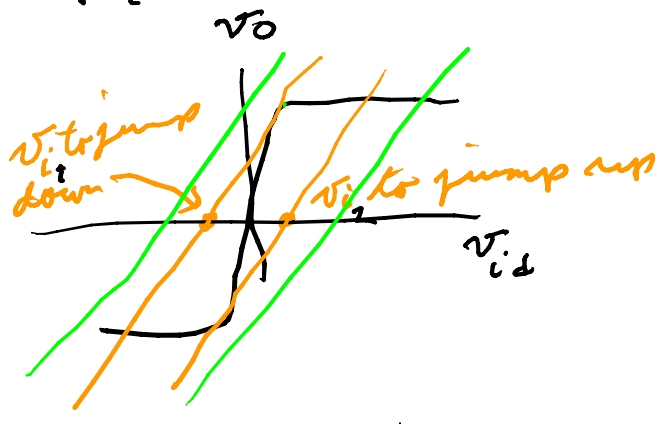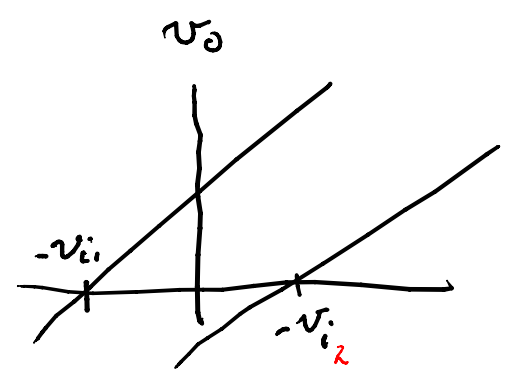moves
 \leftarrow if $v_i > 0$ \rightarrow if $v_i < 0$



\Rightarrow



won't converge as a DC
 run in Spice (as multiple
 Q points)
 \therefore do a transient analysis
 with slowly varying
 triangle waves.