

$$\#1. \quad V_{CC} = R I_L + V_{BE}, \quad I_L = I_0 + \frac{1}{\beta} I_0 = \left(\frac{\beta+1}{\beta}\right) I_0 = \frac{101}{100} \times 6 \times 10^{-3} \\ = 6.12 \times 10^{-3}$$

$$V_{BE} \Rightarrow |I_E| = I_S e^{V_{BE}/V_T}$$

$$\Rightarrow V_{BE} = V_T \ln\left(\frac{|I_E|}{I_S}\right) = V_T \ln\left(\frac{I_0 \times \left(\frac{\beta+1}{\beta}\right)}{I_S}\right)$$

$$= 26 \times 10^{-3} \ln\left(\frac{6 \times 10^{-3} \times \frac{101}{100}}{6 \times 10^{-16}}\right)$$

$$= 26 \times 10^{-3} \times (\ln 10^3 + 1.01) = 26 \times 10^{-3} \ln(10^{6.2} \times 1.01)$$

$$= 26 \times 10^{-3} (6 \ln 10 + \ln 10 + 1.01)$$

$$= 26 \times 10^{-3} (27.63 + 2.30 + 1.01)$$

$$= 26 \times (29.93 + 0.01) \times 10^{-3}$$

$$= 0.778 + 0.0003$$

$$= 0.778$$

$$R = \frac{V_{CC} - V_{BE}}{I_L} = \frac{6 - 0.778}{6.12 \times 10^{-3}}$$

$$= 0.853 \times 10^3$$

$$= 853 \text{ ohm}$$

#2. @ zero input bias, M_p & M_n are in saturation as $|V_{GS}| = |V_{DS}| = 5 \gg |V_{GS}| - |V_{TO}|$

$$\Rightarrow I_{Dn} = -I_{Dp} = \frac{K_p}{2} \frac{W}{L} (|V_{GS}| - |V_{TO}|)^2 (1 + 0.1|V_{DS}|) = 4 \times 10^{-5} (5-1)^2 (1 + 0.1 \times 5) / 2$$


$$\frac{4 \times 16 \times 1.5 \times 10^{-5}}{2} = \frac{96 \times 10^{-5}}{2} = 0.48 \text{ mA}$$

$$g_m = \frac{2I_{Dn}}{|V_{GS}| - |V_{TO}|}$$


$$= \frac{4 \times 16 \times 1.5 \times 10^{-5}}{4} = 16 \times 1.5 \times 10^{-5} \quad , \quad g_o = \lambda I_{Dn} = 0.048 \times 10^{-3} \text{ mho}$$

$$= 0.24 \times 10^{-3} \text{ mho}$$

Equivalent circuit (admittances double)

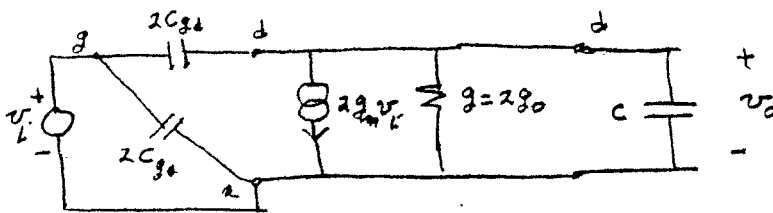

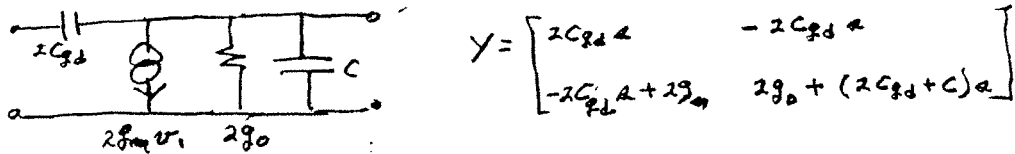To find v_o/v_i consider the Y matrix for




and set $I_2 = 0 \Rightarrow -y_{21} v_1 = y_{22} v_2 \Rightarrow$

$$\frac{v_2}{v_1} = -\frac{y_{21}}{y_{22}} = \frac{-(2g_m - 2C_{gd} a)}{2g_o + (2C_{gd} + C) a} = \frac{-g_m}{g_o} \left(\frac{1 - (C_{gd}/g_m) a}{1 + \frac{(2C_{gd} + C) a}{2g_o}} \right)$$

$$= -\frac{0.24 \times 10^{-3}}{0.048 \times 10^{-3}} \left(\frac{1 - \left(\frac{10^{-11}}{0.24 \times 10^{-3}} \right) a}{1 + \left(\frac{40 \times 10^{-12}}{0.096 \times 10^{-3}} \right) a} \right) = -5 \times \left(\frac{1 - 4.167 \times 10^{-8} a}{1 + 41.67 \times 10^{-6} a} \right)$$

$$= +0.5 \left(\frac{a - 24 \times 10^6}{a + 214 \times 10^6} \right)$$

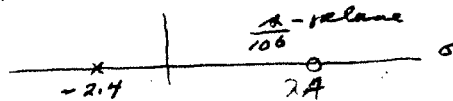Zero @ $a = 24 \times 10^6$
 pole @ $a = 214 \times 10^6$



#3.

$$v_0 = -\frac{R_2}{R_1} v_i - \frac{R_2}{R_1} v_i = -\frac{R_2}{R_1} v_i - \frac{R_2}{R_1} T(s) v_0 \Rightarrow (1 + K \cdot T(s)) v_0 = -K v_i$$

$$\Rightarrow \frac{v_0}{v_i} = \frac{-(R_2/R_1)}{1 + (R_2/R_1) \cdot T(s)} \quad \text{where } T(s) = V/V_0 = \frac{1}{C_1 C_2 L R s^3 + C_2 L s^2 + (C_1 + C_2) R s + 1}$$

$$= \frac{-(K) [C_1 C_2 L R s^3 + C_2 L s^2 + (C_1 + C_2) R s + 1]}{C_1 C_2 L R s^3 + C_2 L s^2 + (C_1 + C_2) R s + (1 + K)}$$

For oscillations, $s = j\omega_0$ & denominator = 0

$$\Rightarrow -j\omega_0^3 C_1 C_2 L R + j\omega_0 C_2 L (C_1 + C_2) R - C_2 L \omega_0^2 + (1 + K) = 0$$

$$\text{Imaginary} = 0 \Rightarrow \omega_0^2 = \frac{C_1 + C_2}{C_1 C_2 L}$$

$$\text{Real} = 0 \Rightarrow (1 + R_2/R_1) + C_2 L \omega_0^2 = 1 + \frac{C_2}{C_1} \Rightarrow \frac{R_2}{R_1} = \frac{C_2}{C_1} = K$$

Poles are zeros of denominator, two from $s^2 + \omega_0^2$

$$\Rightarrow s_{1,2} = \pm j\omega_0 = \pm j \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

The other is from $s + \sigma_0$ found by long division

$$\frac{s^2 + \omega_0^2}{C_1 C_2 L R s^3 + C_2 L R s^2 + (C_1 + C_2) R s + C_2 L \omega_0^2} \Rightarrow \frac{C_1 C_2 L R s + C_2 L}{C_1 C_2 L R s^3 + C_2 L R s^2 + (C_1 + C_2) R s + C_2 L \omega_0^2} = \frac{C_1 C_2 L R s + C_2 L}{C_1 C_2 L R s^3 + C_2 L R s^2 + C_1 C_2 L R \omega_0^2 s + C_2 L \omega_0^2}$$

$$\Rightarrow \sigma_0 = \frac{1}{C_1 R}$$

$$\Rightarrow C_1 C_2 L R s^3 + C_2 L s^2 + (C_1 + C_2) R s + (1 + R_2/R_1) = C_2 L R (s^2 + \omega_0^2) (s + \sigma_0)$$

$$\Rightarrow \text{poles: } s_{1,2} = \pm j \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}, \quad s_0 = -\sigma_0 = -\frac{1}{C_1 R}$$

$$\text{Note } C_{\text{series}} = \frac{C_1 C_2}{C_1 + C_2} \Rightarrow \omega_0^2 = \frac{1}{C_s \cdot L} \Rightarrow \omega_0 \text{ from } L \& C_s \text{ is reasonable as } L \& C_s \text{ are in parallel}$$