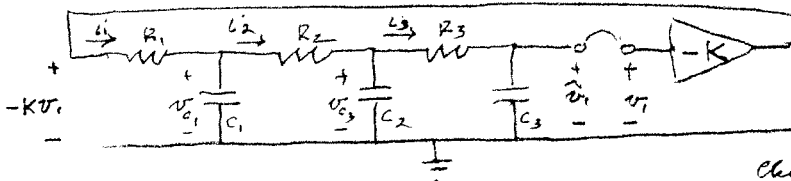


analysis of RC phase shift oscillator

02/21/12
RWN



Derive $\hat{v}_1 = v_1$ for natural response
& for $v = V e^{j\omega_0 t} + V^* e^{-j\omega_0 t}$

Choose input to $-K$ of $R_{in} \rightarrow \infty$ so all of R_3 current is through C_3 [else add R_{in}]

1a), b), c) $i_1 = \frac{1}{R_1} (-Kv_1 - v_2) = \alpha C_1 v_2 + i_2 \Rightarrow -Kv_1 = (1 + \alpha R_1 C_1) v_2 + R_1 i_2$

2a), b), c) $i_2 = \frac{1}{R_2} (v_2 - v_3) = \alpha C_2 v_3 + i_3 \Rightarrow v_2 = (1 + \alpha R_2 C_2) v_3 + R_2 i_3$

3a), b), c) $i_3 = \frac{1}{R_3} (v_3 - \hat{v}_1) = \alpha C_3 \hat{v}_1 \Rightarrow v_3 = (1 + \alpha R_3 C_3) \hat{v}_1$

3b) & 3c) \rightarrow 2c)

4a), b), c) $v_2 = (1 + \alpha R_2 C_2) v_3 + \alpha R_2 C_3 \hat{v}_1 = (1 + \alpha R_2 C_2)(1 + \alpha R_3 C_3) \hat{v}_1 + \alpha R_2 C_3 \hat{v}_1$

4c) & 3a) \rightarrow 2a)

5a) $i_2 = \frac{1}{R_2} \left([(1 + \alpha R_2 C_2)(1 + \alpha R_3 C_3) + \alpha R_2 C_3] - [1 + \alpha R_3 C_3] \right) \hat{v}_1$

5b) $= \frac{1}{R_2} \left(\alpha R_2 C_2 (1 + \alpha R_3 C_3) + \alpha R_2 C_3 \right) \hat{v}_1$

5b) & 4c) \Rightarrow 1c)

6a) $-Kv_1 = (1 + \alpha R_1 C_1) \left\{ (1 + \alpha R_2 C_2)(1 + \alpha R_3 C_3) + \alpha R_2 C_3 \right\} \hat{v}_1 + \frac{R_1}{R_2} \left(\alpha R_2 C_2 (1 + \alpha R_3 C_3) + \alpha R_2 C_3 \right) \hat{v}_1$

setting $v_1 = \hat{v}_1 \neq 0 \Rightarrow$

6b) $0 = (1 + \alpha R_1 C_1) (1 + \alpha R_2 C_2) (1 + \alpha R_3 C_3) + (\alpha R_2 C_3) (1 + \alpha R_1 C_1) + \alpha R_1 C_2 (1 + \alpha R_3 C_3) + \alpha R_1 C_3 + K$

6c) $0 = [1 + (R_1 C_1 + R_2 C_2) \alpha + R_1 C_1 R_2 C_2 \alpha^2] (1 + \alpha R_3 C_3) + R_2 C_3 \alpha + R_1 C_1 R_2 C_3 \alpha^2 + R_1 C_2 \alpha + R_1 C_2 R_3 C_3 \alpha^2 + R_1 C_3 \alpha + K$

6d) $= 1 + [(R_1 C_1 + R_2 C_2) + R_3 C_3] \alpha + [R_1 C_1 R_2 C_2 + (R_1 C_1 + R_2 C_2) R_3 C_3] \alpha^2 + (R_1 C_1 R_2 C_2 R_3 C_3) \alpha^3 + (R_2 C_3 + R_1 C_2 + R_1 C_3) \alpha + (R_1 C_1 R_2 C_3 + R_1 C_2 R_3 C_3) \alpha^2 + K$

6e) $= (R_1 C_1 R_2 C_2 R_3 C_3) \alpha^3 + \{ R_1 C_1 + R_2 C_2 + R_3 C_3 + R_2 C_3 + R_1 C_2 + R_1 C_3 \} \alpha^2 + \{ R_1 C_1 R_2 C_2 + R_1 C_1 R_3 C_3 + R_2 C_2 R_3 C_3 + R_1 C_1 R_2 C_3 + R_1 C_2 R_3 C_3 \} \alpha + (1 + K)$

set $\alpha = j\omega_0$ in 6e) & equate real and imaginary parts both = 0

7a) $0 = j\omega_0 \{ -R_1 C_1 R_2 C_2 R_3 C_3 \omega_0^2 + [R_1 C_1 + R_2 C_2 + R_3 C_3 + R_2 C_3 + R_1 C_2 + R_1 C_3] \}$

7b) $0 = -\omega_0^2 \{ R_1 C_1 R_2 C_2 + R_1 C_1 R_3 C_3 + R_2 C_2 R_3 C_3 + R_1 C_1 R_2 C_3 + R_1 C_2 R_3 C_3 \} + (1 + K)$

set $R_1 = R_2 = R_3 = R, C_1 = C_2 = C_3 = C, \omega_0 \neq 0$

8a) $0 = -R^3 C^3 \omega_0^2 + 6RC \Rightarrow \omega_0^2 = 6/R^2 C^2$

8b) $0 = -\omega_0^2 \cdot 5R^2 C^2 + (K+1) \Rightarrow K = -1 + 5R^2 C^2 \omega_0^2 = -1 + 30 = 29$

If $R = 10k\Omega, C = 18mF \Rightarrow \omega_0 = \frac{\sqrt{6}}{10^4 \times 18 \times 10^{-6}} \Rightarrow f_0 = \frac{1}{2\pi} \times \frac{\sqrt{6}}{18} \times 10^5 \text{ Hz} = 2.17 \text{ kHz}$

Note if $C_1 = 0$ then 7a) requires a negative R or C