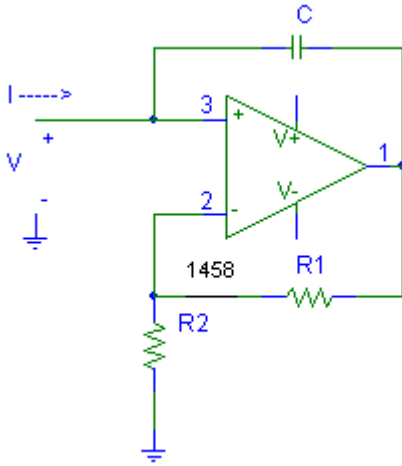


## ENEE 417 -Spring 2012


Week #7 starting M 03/12/12

## Negative Y &amp; Crystal equivalent circuit, Oscillator Designs; VLSI &amp; Spice Extraction

1. Construct the following circuit to make a negative capacitor (first replace the capacitor by a resistor and check if you see a negative resistor at the input). Note that  $I = -(R1/R2)y(s).V$  where  $y(s)$  is the admittance of a two-terminal device placed where the capacitor is;  $y(s) = sC$  for the capacitor.



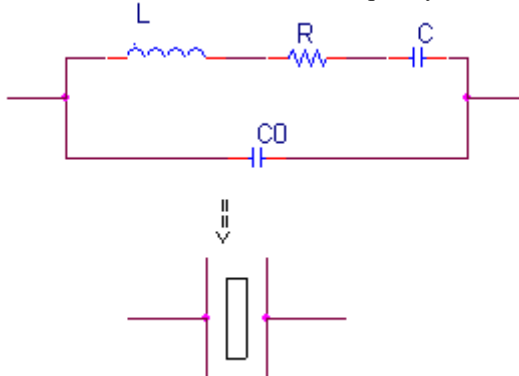2. Use the S663 quartz crystal (ECS inc. part ECS-3X8X) **[note that the crystal will shatter when too high a voltage is applied]**
- a) Find the values of the components in its following equivalent circuit. For that use the circuit of part 1 above to cancel out the parallel  $C_0$  (of  $C_0 = 1.6\text{pF}$  given in the ECS data sheet) and then check the resonant frequency ( $f_0 = 32.768\text{KHz}$  of the ECS data sheet).



- b) Construct the Recommended Oscillation Circuit of the ECS data sheet and check its oscillation.