
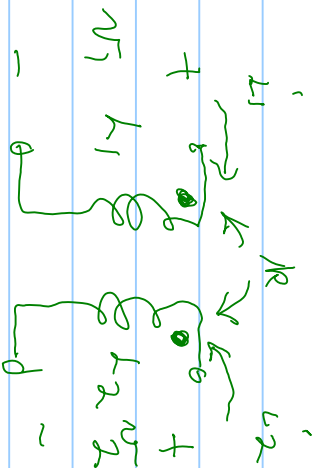
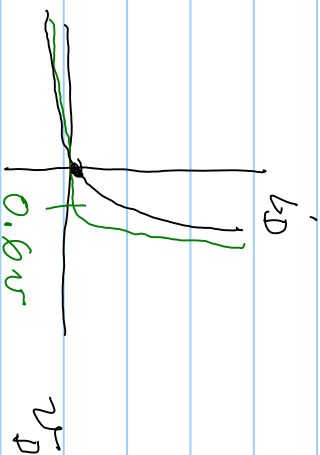


EE 307

02/03/16

actual diode

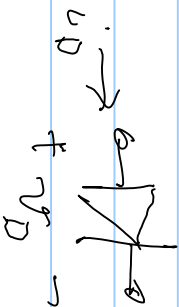

$$Z(\omega) = R L = \begin{bmatrix} L_1 & R\sqrt{L_1 L_2} \\ R\sqrt{L_1 L_2} & L_2 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Z(\omega) \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


$$|R| \leq 1$$

$$\det L = L_1 h_2 - R^2 h_1 h_2 = h_1 h_2 (1 - R^2)$$

$$y(s) = z^{-1}(s) = \frac{1}{\det h} \begin{bmatrix} L_2 & -R\sqrt{L_1 L_2} \\ -R\sqrt{L_1 L_2} & L_1 \end{bmatrix}$$

This has trouble
if $|R| = 1$
not pass criteria

ideal transformer

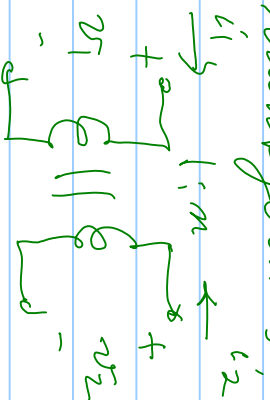

$$v_2 = n v_1 \Rightarrow v_2 v_1 \Rightarrow E$$

$$i_2' = -n i_1' \Rightarrow C C C S \Rightarrow F$$

$$P_{in} = -P_{out} \Rightarrow P_{in} = v_1 i_1', \quad P_{out} = v_2 i_2'$$

$$\begin{cases} n v_1 i_1' + v_2 i_2' = 0 \Rightarrow v_2 = -n v_1 \\ n v_1 i_1' + n v_1 i_2' = 0 \Rightarrow i_2' = -n i_1' \end{cases}$$

To relate to coupled coils set $i_2 = 0$ & measure $v_1 = n v_2$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = k \begin{bmatrix} L_1 \\ k\sqrt{L_1 L_2} \end{bmatrix} \quad k\sqrt{L_1 L_2} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow v_2 = z(i_1, i_2)$$

if $i_2 = 0 \Rightarrow v_2 = n v_1$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = k \begin{bmatrix} L_1 \\ k\sqrt{L_1 L_2} \end{bmatrix} \begin{bmatrix} i_1 \\ 0 \end{bmatrix}$$

$$\frac{v_1}{v_2} = \frac{k L_1 i_1}{k\sqrt{L_1 L_2} i_1} = \frac{L_1}{k\sqrt{L_1 L_2}} = \frac{1}{k} \sqrt{\frac{L_1}{L_2}}$$

$$v_2 = k \sqrt{\frac{L_2}{L_1}} \cdot v_1 \quad n = k \sqrt{\frac{L_2}{L_1}}$$

for $n = 0.9999$
for iron cores

$$n \approx \sqrt{\frac{L_2}{L_1}}$$

also derive $i_1 = -n i_2$ let's set $v_2 = 0$


$$0 = k\sqrt{L_1 L_2} i_1 + L_2 i_2 \Rightarrow i_1 = -\frac{L_2}{k\sqrt{L_1 L_2}} i_2 \Rightarrow -n = -\frac{\sqrt{L_2 L_1}}{k} \quad n = \sqrt{\frac{L_2}{L_1}}$$

K in series gives the coupling coeff $k=1$

$$\left[\begin{matrix} \bullet \\ h_1 \end{matrix} \right] \left[\begin{matrix} \bullet \\ L_2 \end{matrix} \right] \text{ choose } \sqrt{\frac{L_2}{L_1}} = n$$


$$L_2 = n^2 L_1$$


choose h_1 or 100Hg

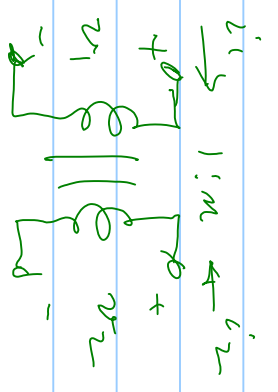

$$v_2 = n v_1, \quad i_1 = -n i_2$$

$$\text{gain} = n$$

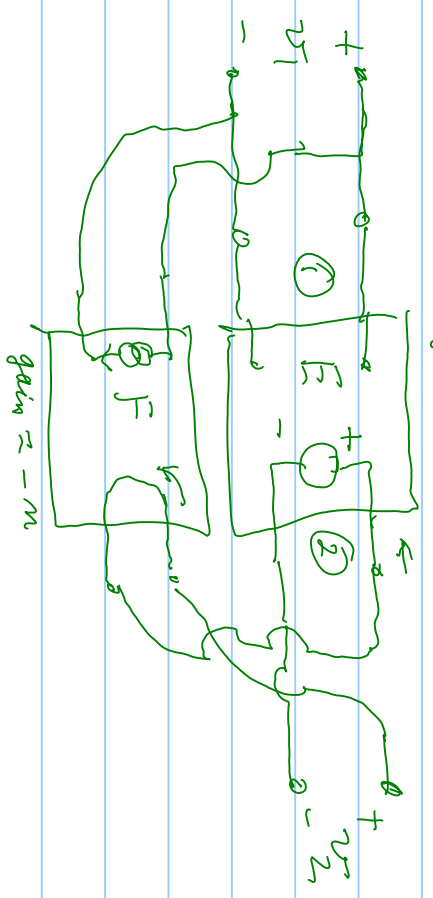

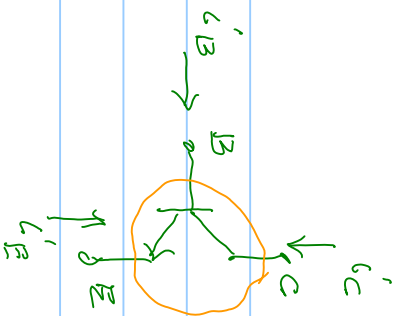

MPN
BJT

$$KCL \Rightarrow 0 = i_B + i_E + i_C \Rightarrow i_E = -(i_B + i_C)$$

$$\text{if } i_C = \beta i_B \quad i_E = -(\beta + 1)i_B$$