

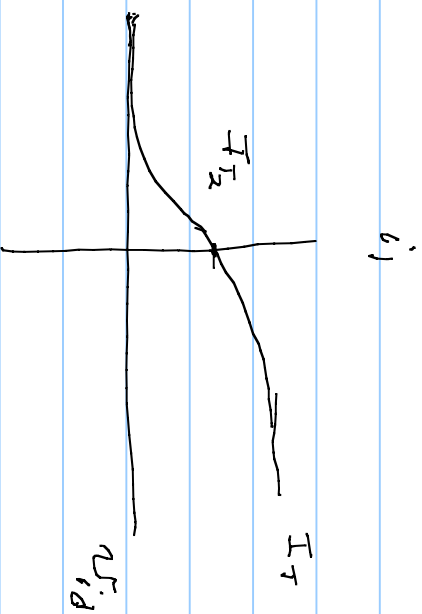


EE 307

03/30/16

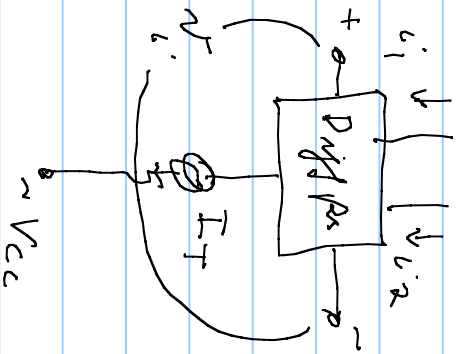


$V_{cc}$

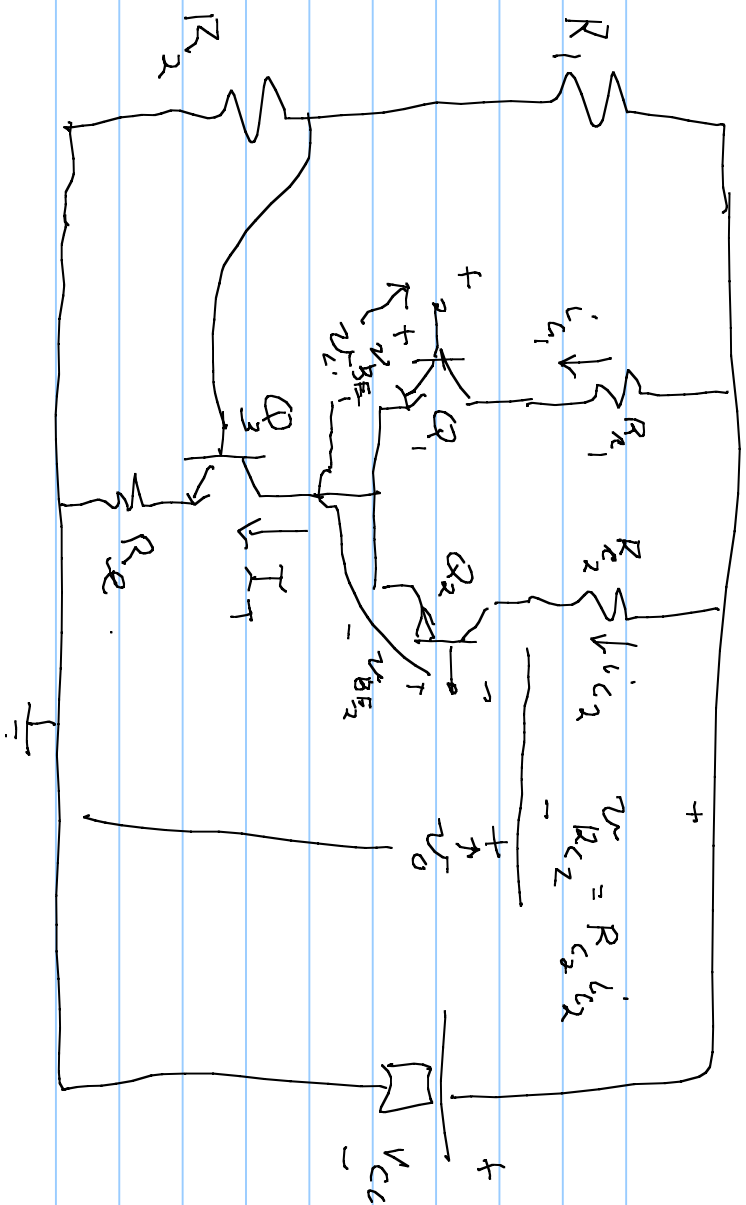

$$V_1 \approx V_{BE1} - V_{BE2}$$


$$\begin{aligned}
 I_T &= (-I'_{C1}) + (-I'_{C2}) && \text{by KCL} \\
 &= \frac{I'_{C1} + I'_{C2}}{\alpha} \approx \frac{I_S e^{V_{BE1}/V_T} + I_S e^{V_{BE2}/V_T}}{\alpha} = \frac{I_S}{\alpha} e^{V_{BE2}/V_T} (e^{V_1/V_T} + 1) \\
 I'_{C1} - I'_{C2} &= I_{out} \approx I_S e^{V_{BE1}/V_T} - I_S e^{V_{BE2}/V_T} = I_S \cdot e^{V_{BE2}/V_T} (e^{V_1/V_T} - 1)
 \end{aligned}$$
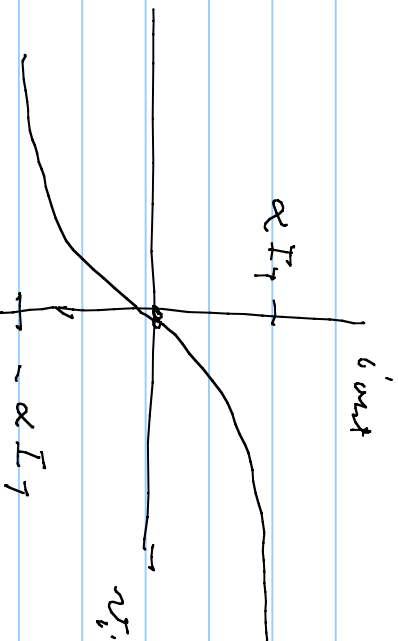
$$\begin{aligned}
 i_{out} &= I_S e^{v_{BE}/V_T} (e^{v_i/V_T} - 1) = \alpha I_T \frac{e^{v_i/V_T}}{e^{v_i/2V_T} + 1} \times (e^{v_i/2V_T} - 1) \\
 &= \alpha I_T \left( \frac{e^{v_i/2V_T}}{e^{v_i/2V_T} + e^{-v_i/2V_T}} \right) \left( \frac{e^{v_i/2V_T} - e^{-v_i/2V_T}}{e^{v_i/2V_T} + e^{-v_i/2V_T}} \right) = \alpha I_T \cdot \tanh\left(\frac{v_i}{2V_T}\right)
 \end{aligned}$$



if output is a current difference

$$\begin{aligned}
 q_m &= \frac{d i_{out}}{d v_i} \Big|_{v_i=0} = \alpha I_T \cdot \frac{1}{2V_T} \left( 1 - \tanh^2\left(\frac{v_i}{2V_T}\right) \right) \Big|_{v_i=0} \\
 &= \alpha \cdot \frac{I_T}{2V_T}
 \end{aligned}$$

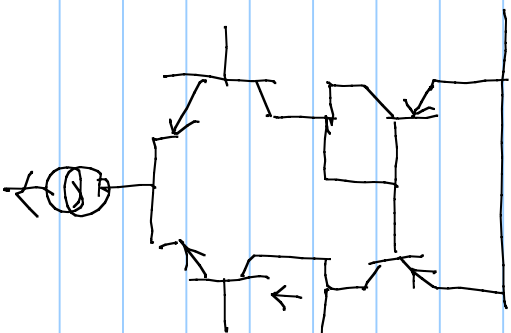

$$v_{c2} - v_{c1} = -v_{out}$$

$$V_{out\ on\ R_{C2}} \Rightarrow V_0 = V_{CC} - R_{C2} \cdot i_{C2}$$

$$i_{C2} = I_{S2} e^{\frac{v_{BE2}}{V_T}} = \alpha I_T \times \frac{1}{e^{\frac{v_{BE}}{V_T}} + 1}$$

$$V_0 = V_{CC} - R_{C2} \cdot \alpha I_T \times \frac{1}{e^{\frac{v_{BE}}{V_T}} + 1}$$

$$A_v = \frac{dv_o}{dv_i} \Big|_{v_i=0} = -R_{C2} \cdot \alpha F_T \cdot \frac{-1}{(e^{v_T/v_T} + 1)^2} \times \frac{1}{v_T} e^{v_i/v_T} \Big|_{v_i=0}$$

$$= \alpha R_{C2} \frac{I_T}{2} \times \frac{1}{2} \times 1 = \alpha R_{C2} \cdot \frac{I_T}{2V_T} = R_{C2} \cdot \frac{g_m}{2}$$

$$= \frac{v_o}{v_i - v_i}$$

for feedback structure  $v_o = v_o \times \frac{R_{S1}}{R_{S1} + R_{S2}}$

$$A_v \cdot (v_i - \frac{v_o R_{S1}}{R_{S1} + R_{S2}}) = v_o \approx \frac{v_o}{v_i} \approx 1 + \frac{R_{S1}}{R_{S2}}$$