

ENEE 417 - Spring 2016

Week #4 starting W 02/22/16

Designs #2: Ring and Phase Shift Oscillator Designs; Spice Design

In this experiment a good reference is Sedra and Smith (pages 1239 & 1345 of the 6th edition)
For the active devices use the 4007 CMOS transistor package and 1458 Op-Amps.

1. Construct both a three stage and a five stage ring oscillator and record via the scope/computer interface the oscillations. Check the results of Figure 15.28 of the above reference.

Insert various capacitors at the outputs of the stages and see the effects. Among the capacitor values use one of the super-capacitors (whose values are on the order of Farads). Check also the effect of using an even number of stages.

2. Using an Op-Amp amplifier realize the phase shift oscillator of Fig. 17.7 using $R=10\text{Kohm}$ and C as $15\text{nFd} = 15,000\text{pFd}$ and 18nFd .

3. In Spice use MOSIS 1.6u level 4 CMOS model parameters, available in the bicmos12.lib files, to design a three stage inverter ring oscillator (for this adjust the W and L so that a symmetric bias yields zero output voltage for zero input voltage; make sure that both W and L are bigger than 7microns).