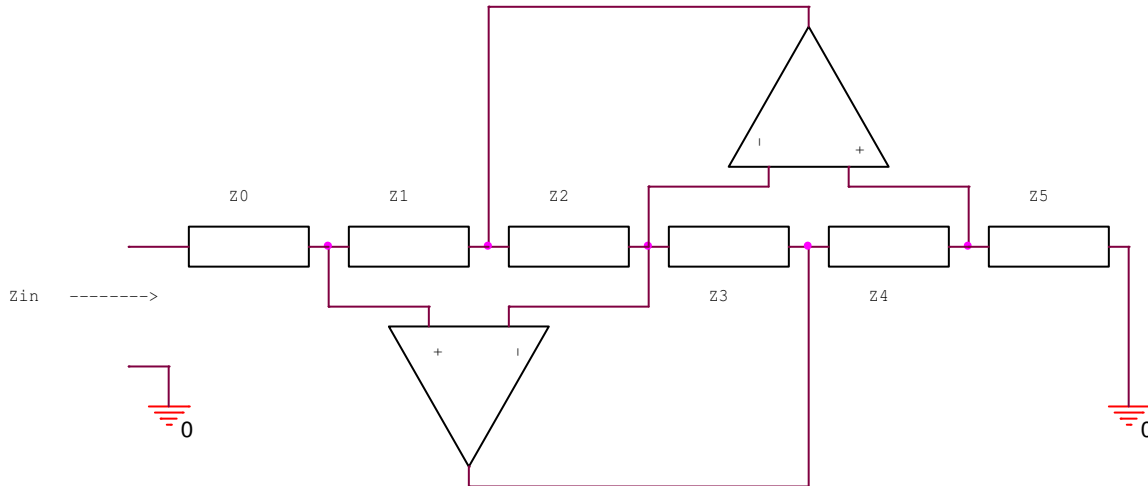


ENEE 307 In Lab Final Spring 2018
Experiments on an Active GIC

1. The following circuit is called a GIC (=General Impedance Converter). When the op-amps are ideal, it is known that (where all Z's are impedances)

$$Z_{in}(s) = Z_0(s) + (Z_1(s) \cdot Z_3(s) \cdot Z_5(s)) / (Z_2(s) \cdot Z_4(s))$$



Assuming only resistors and capacitors are available for the impedances, $Z_i(s)$, and loads; choose one from among the following two possibilities for the input of the above circuit to behave as:

1. A frequency dependent resistor $Z_{in}(s) = R s^2$ (of $R = [\text{value}]/40$ Ohms with value = last 3 digits of ID)
2. A frequency dependent conductor $Z_{in}(s) = R/s^2$ (of $R = [\text{value}] \times 10^6$ Ohms with value = last 3 digits of ID)

Then using 1458 op-amps, as many 10K Ohm resistors as possible, and, where needed, 0.474 MicroFarad capacitors [assume also when possible $Z_0 = 0$] design a circuit and test it (key components will be in your component box, others are available in the lab or through your TA).

In your report

- a) Give your circuit choice with your intended value of R.
- b) Screen shots of your circuit design via Spice (or similar) simulations
- c) Determination of an experimental means to tell if your circuit will give the intended value.
- d) Your experimentally created circuit on your breadboard and experimentally determined characteristics.
- e) Submit a report to your TA prior to the end of the period.

Note that the return of signal current of the op-amps is not shown, allowing the circuit input current to differ from the current in Z_5 . Also a special case is analyzed on p. 1286 of Sedra/Smith, 6th edition.