
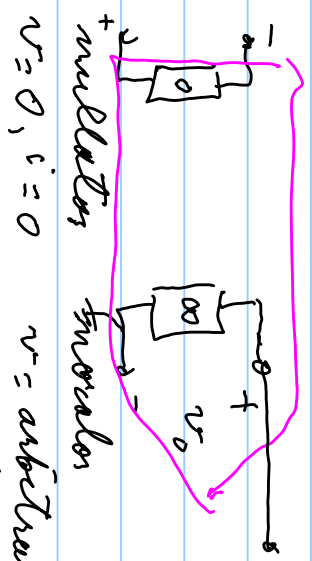


||

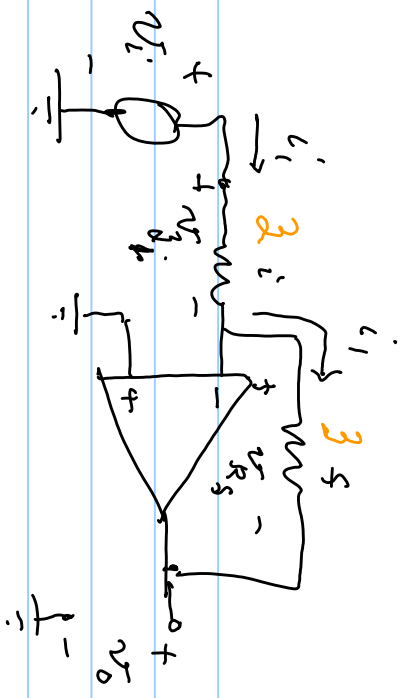

$v = 0, i = 0$ $v = \text{arbitrary}$
 $i = \text{arbitrary}$ & independent of v





$$\frac{v_o}{v_i}(s) = -\frac{g_m}{g_i}$$

$$v_{g_i} = g_i \cdot i_1 \quad ; \quad v_{R_S} = g_s \cdot i_1 = g_s \cdot \frac{v_i}{g_i} = -v_o$$

$$\Rightarrow i_1 = v_i / g_i$$

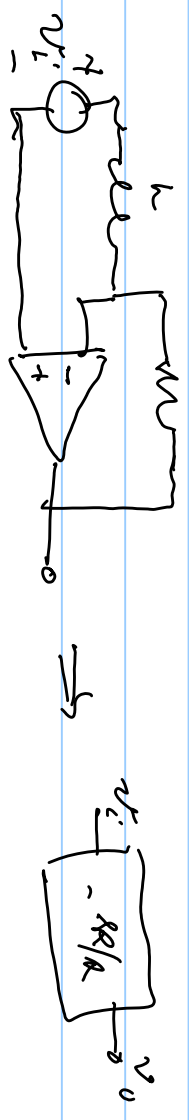if device an integrator = $R/R = v_o/v_i = \frac{R_L}{L R} = -\frac{R_L}{L R}$



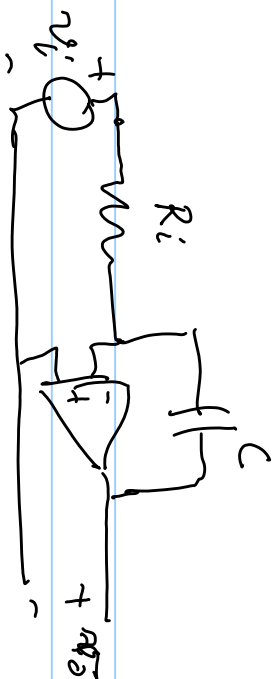


$$\frac{v_o}{v_i} = -\frac{1/cA}{R_i} = -\frac{1}{R_i \cdot cA}$$

for a resistive multiplier

$$i_1 = -v_i / R_i$$

$$v_{R_i} = R_i i_1 = v_i = -v_i$$

"

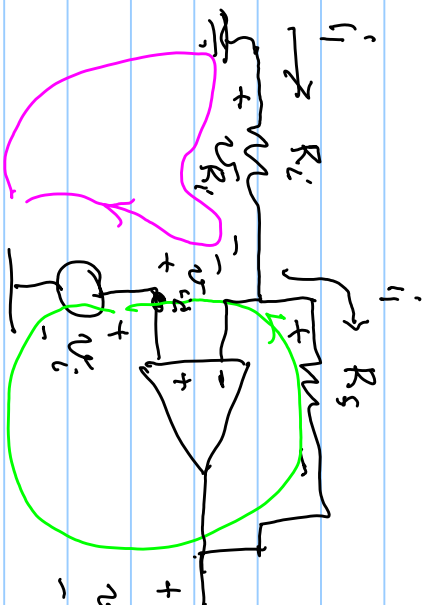

$$v_o = -R_s i_1 + v_i = +R_s \frac{v_i}{R_i} + v_i$$

$$v_o = \left(1 + \frac{R_s}{R_i}\right) v_i \Rightarrow \frac{v_o}{v_i} = 1 + \frac{R_s}{R_i}$$

KVL $\Rightarrow 0 = v_i - v_o - R_s i_1 - v_{R_i} \Rightarrow v_o = v_i - R_s i_1, \quad 0 = v_i + v_{R_i}$

$$v_o = v_i - R_s \left(-\frac{v_i}{R_i}\right) = \left(1 + \frac{R_s}{R_i}\right) v_i \quad i_1 = -\frac{v_i}{R_i} \Leftarrow = v_i + R_i i_1$$

Rectifiers