
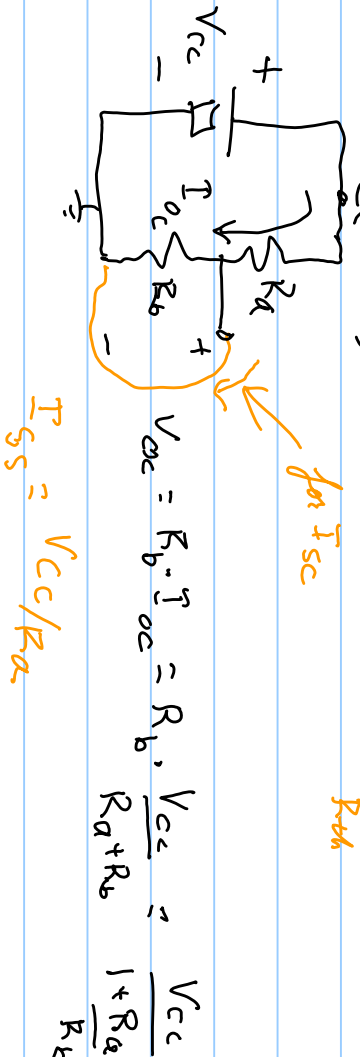
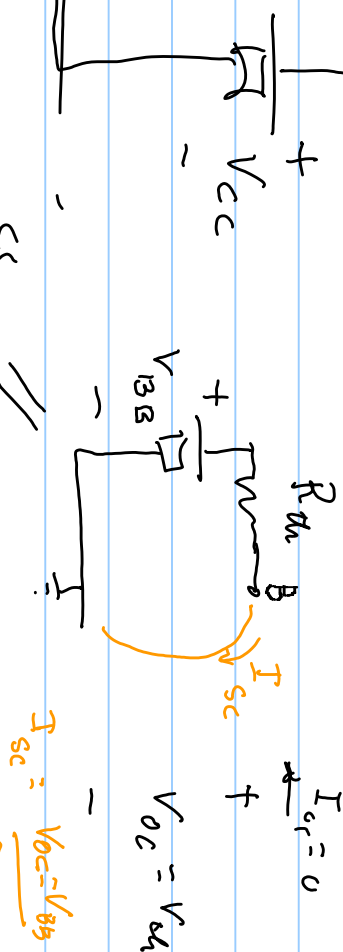


EE307
02/19/18

Biasing of BJT

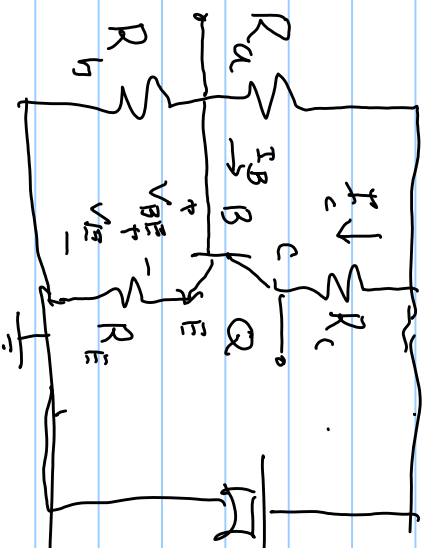

for I_{sc}

$$I_{sc} = \frac{V_{oc} = V_{BB}}{R_{th}}$$

$$V_{oc} = R_b \cdot I_{oc} = R_b \cdot \frac{V_{cc}}{R_a + R_b} = \frac{V_{cc}}{1 + \frac{R_a}{R_b}}$$

$$I_{SS} = V_{cc} / R_a$$

$$R_{Th} \approx \frac{V_{oc}}{I_{G5}} = \frac{R_b \frac{V_{cc}}{R_a + R_b}}{V_{cc}/R_a} = \frac{R_a R_b}{R_a + R_b} \Rightarrow R_{Th} = R_a \parallel R_b$$


$$V_{B12} = V_{oc} = \frac{R_b}{R_a + R_b} \cdot V_{cc}$$

The basic problem is to find R_a , R_b given V_{cc} , I_c from $q_m = \frac{I_c}{V_T}$

R_E , & the BJT $Q(\beta)$
 \Rightarrow given the Q point
 $V_{B12} \approx 0.7V$

we know $V_B = R_E \frac{I_c}{\alpha}$
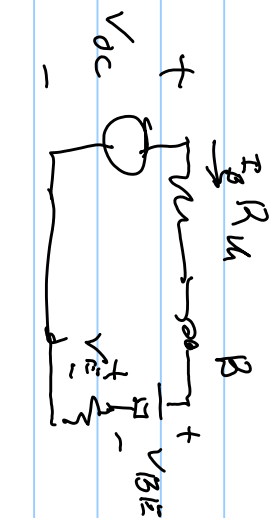
$$\beta = h_{FE} = \frac{\alpha}{1-\alpha} \Rightarrow \alpha = \frac{\beta}{1+\beta}$$



$$V_{Base} = V_{B12} + R_E \cdot \frac{I_c}{\alpha}$$

$$V_{R_{Th}} = R_{Th} \cdot I_B = R_{Th} \frac{I_c}{\beta} = (V_{oc} - V_B)$$

gives one eq. in two unknowns R_a, R_b

$$\frac{R_a R_b}{R_a + R_b} \cdot \frac{I_C}{\beta} = \frac{R_b}{R_a + R_b} \cdot V_C - V_{BE} - R_E \frac{I_C}{\alpha} \quad \text{needs to hold}$$

contains the range of R_a & R_b
 also derive R_a & R_b large to prevent loading from
 loading signals circuit feeding this amplifiers
 [$(R_a || R_b)$ loads]

Darlington

