

$$R_s \Rightarrow v = Ri \Rightarrow i = G^{-1}v, \quad G = 1/R$$

$$C_s \Rightarrow i = C dv/dt = dQ \Rightarrow I_{cas} = AC V'(a)$$

$$L_s \Rightarrow v = L di/dt = d\psi/dt \Rightarrow V_{cas} = aL I'(a)$$

$$M = \begin{bmatrix} aL_{11} & aM_{12} \\ aM_{12} & aL_{22} \end{bmatrix}$$


$$OTA \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ G_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow \text{via differential pairs}$$

FDNR = frequency dependent negative resistors


$$I_{cas} = C^2 R^2 V'(a) \Rightarrow R = j\omega \Rightarrow -C^2 \omega^2 = G(\omega)$$

an equivalent R, L, C, OTA circuit by $R, C, FDNR$ & $OTA's$


Differential pair

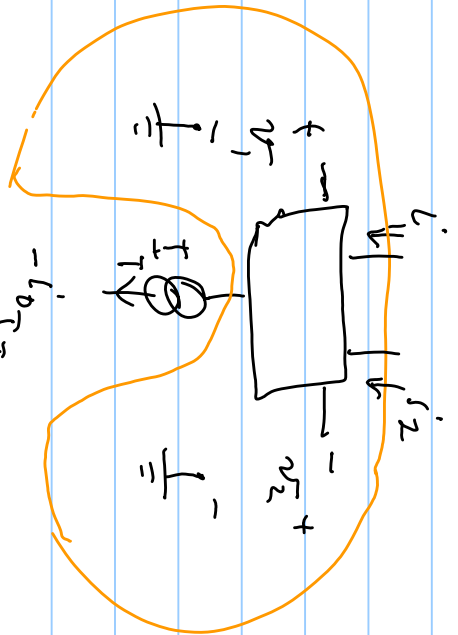

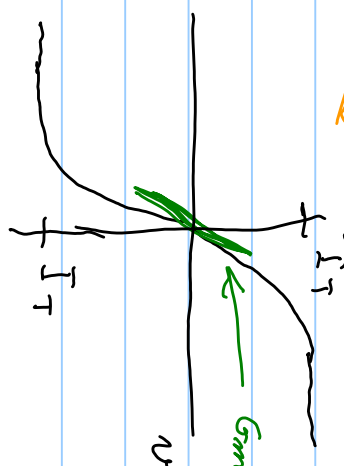$I_T = \text{tail current}$
 $I_T = i_1 + i_2$ by KCL + any current entering input leads to 0
 $I_0 = i_2 - i_1$



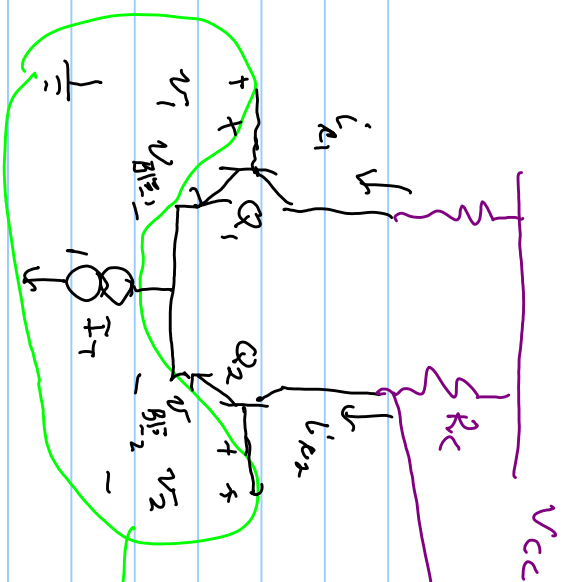$G_m = 0 \text{ at } v_D = 0$
 $v_1 - v_2 = v_D \Rightarrow \text{differential input voltage}$



$$i_{C1} = \alpha I_S e^{V_{BE1}/V_T}$$

$$i_{C2} = \alpha I_S e^{V_{BE2}/V_T}$$

KVL: $0 = -V_1 + V_{BE1} - V_{CE2} + V_2 = V_{BE1} - V_{BE2} = V_1 - V_2$
 $= V_1 - V_2$

$$\frac{i_{C1}}{I_T} = \frac{i_{C2} - i_{C1}}{i_{C2} + i_{C1}} = \alpha I_S \left(\frac{e^{V_{BE2}/V_T} - e^{V_{BE1}/V_T}}{e^{V_{BE2}/V_T} + e^{V_{BE1}/V_T}} \right) = \frac{(1 - e^{(V_{BE1} - V_{BE2})/V_T})}{(1 + e^{(V_{BE1} - V_{BE2})/V_T})}$$

$$= \frac{e^{\frac{V_{BE1} - V_{BE2}}{2V_T}} \left(1 - e^{\frac{V_{BE1} - V_{BE2}}{2V_T}} \right)}{e^{\frac{V_{BE1} - V_{BE2}}{2V_T}} \left(1 + e^{\frac{V_{BE1} - V_{BE2}}{2V_T}} \right)}$$

$$= -\tanh\left(\frac{V_{BE1} - V_{BE2}}{2V_T}\right) \Rightarrow i_O = \alpha I_T \tanh\left(\frac{V_D}{2V_T}\right) ; i_{C1} + i_{C2} = \alpha I_T = - (i_{O1} + i_{O2})$$

$$\tanh x = (e^x - e^{-x}) / (e^x + e^{-x}) \Rightarrow \frac{d \tanh x}{dx} = \frac{e^x + e^{-x}}{(e^x + e^{-x})^2} - \frac{(e^x - e^{-x})(e^x - e^{-x})}{(e^x + e^{-x})^2}$$

$$= 1 - \tanh^2(x)$$

$$\left. \frac{d v_0}{d v_2} \right|_{v_2=0} = -I_T \left(1 - \tanh^2 \left(\frac{v_2}{2v_T} \right) \right) \cdot \frac{1}{2v_T} \Bigg|_{v_2=0} = -\frac{I_T}{2v_T}$$

interested in Lab in $R_e \cdot i_2$

$$\text{But } i_2 = I_T - i_1, \quad i_0 = -I_T \tanh \left(\frac{v_2}{2v_T} \right) = i_2 - i_1 \quad \text{if } \alpha \approx 1$$

$$\Rightarrow i_1 = i_2 - i_0 = i_2 - I_T \tanh \left(\frac{v_2}{2v_T} \right)$$

$$i_2 = I_T - i_1 = I_T - (i_2 - I_T \tanh \left(\frac{v_2}{2v_T} \right)) \Rightarrow 2i_2 = I_T (1 - \tanh \left(\frac{v_2}{2v_T} \right))$$

$$i_2 = \frac{I_T}{2} \left(\frac{e^x + e^{-x} - e^x - (-e^{-x})}{e^x + e^{-x}} \right) = \frac{I_T}{2} \cdot \frac{2e^{-x}}{e^x + e^{-x}} = \frac{I_T}{1 + e^{2v_2/v_T}} = \frac{I_T}{1 + e^{v_2/v_T}}$$

$$v_{out} = V_{cc} - R_c i_c \quad \Rightarrow \quad v_{o(t)} = -R_c \frac{di_c}{dV_{in, output}} \cdot v_i$$