

Solutions Midterm 303 519

#1. $V_{GS} = V_{th}$, $V_{DS} = v_o$; for $v_{in} = V_{th}$, $v_{DS} = v_o = V_{th} - V_{TO} = V_{GS} - V_{th}$

By KVL around outer loop $v_o = V_{DD} - R_L i_D$ and @ $v_{in} = V_{th}$, M_n is in saturation (and in triode region) so

$$v_o = V_{DD} - R_L k (v_{in} - V_{TO})^2 (1 + \lambda v_o) = 12 - 2 \times 10^3 \times 4 \times 10^{-3} (V_{th} - 1)^2 (1 + 0.01 v_o)$$

$$V_{th} - V_{TO} \Rightarrow V_{th} = 13 - 8(V_{th} - 1) \Rightarrow (V_{th} - 1) = 12 - 8(V_{th} - 1)^2$$

$$\text{Let } x = V_{th} - 1 \Rightarrow 8x^2 + x - 12 = 0 \Rightarrow x^2 + \frac{1}{8}x - \frac{12}{8} = 0 \Rightarrow x = \frac{-\frac{1}{8} \pm \sqrt{(\frac{1}{8})^2 + 4 \times \frac{12}{8}}}{2}$$

$$\therefore x = \frac{-\frac{1}{8} (1 \pm \sqrt{1 + 12 \times \frac{1}{8} \times 8})}{2} = \frac{-\frac{1}{8} (1 \pm \sqrt{385})}{2} \approx \frac{-\frac{1}{8} (1 \pm 19.62)}{2} = \frac{-\frac{1}{8} (20.62 \text{ or } -18.62)}{2}$$

or $x = -1.289$ or $+1.164$ as $V_{th} > V_{TO}$ use + sign, $V_{th} = x + 1 = 2.164$

$$\Rightarrow \underline{V_{th} = 2.16 \text{ V}}$$

#2 @ the gate, w/it gnd, $V_G = \frac{R_B}{R_A + R_B} V_{DD} = V_{GS} + R_S I_D$; $V_{GS} = V_{TO} + \sqrt{\frac{I_D}{k}} = 1 + \sqrt{\frac{1}{4}} = 3/2 \Rightarrow V_{GS} = 8 \Rightarrow V_{GS} - V_{TO} = 1/2$

If $k = 2 \text{ mA/V}^2$ is used
then $V_{GS} = 1 + \sqrt{1/2} = 1.707$
 $\Rightarrow V_G = 1.707 + 2 = 3.707$
 $\Rightarrow \frac{R_B}{R_A + R_B} = 3.707$
or $R_A = 2.24 R_B$
 $g_m = 2 \times 2 \times 0.707 \times 10^{-3}$
 $= 2.83 \times 10^{-3}$
 $A_v = -5.86$

$$\Rightarrow \underline{V_{DS} = 8 \text{ V}, V_{GS} = 1.5 \text{ V}, I_D = 1 \text{ mA}}$$


$$\Rightarrow R_A = \left(\frac{2 \times 12}{7} - 1\right) R_B = \frac{17}{7} R_B$$

and $R_A = 2.42 R_B$

b) g_m need $g_m = \frac{\partial i_D}{\partial v_{GS}} = 2k (V_{GS} - V_{TO}) = 2 \times 4 \times 10^{-3} (\frac{3}{2} - 1) = 4 \text{ mMhos}$

and $g_o = \frac{\partial i_D}{\partial v_{DS}} = 0$ @ the input R_A & R_B are parallel

The equivalent circuit is

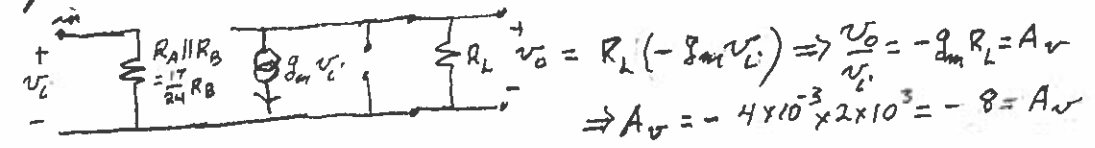

#3. $\frac{v_{mid}}{v_{in}} = \frac{g_{m1} + G}{A C_1 + (g_{m1} + G)}$ from last class & $\frac{v_{out}}{v_{mid}} = -\frac{1}{A C_2} \cdot g_{m2}$ by KCL on OTA₂

$$\therefore \frac{v_o}{v_{in}} = \frac{v_{out}}{v_{mid}} \cdot \frac{v_{mid}}{v_{in}} = \frac{-g_{m2} (g_{m1} + G)}{A C_2 (A C_1 + (g_{m1} + G))} = \frac{-g_{m2} (g_{m1} + G)}{A^2 C_1 C_2 + A C_2 (g_{m1} + G)}$$

$$\text{or } (A^2 C_1 C_2 + A C_2 (g_{m1} + G)) v_o(t) = -g_{m2} (g_{m1} + G) v_{in}(t)$$

$$\Rightarrow C_1 C_2 \frac{d^2 v_o}{dt^2} + C_2 (g_{m1} + G) \frac{d v_o}{dt} = -g_{m2} (g_{m1} + G) v_{in}(t)$$

#4. a) For two fins, $n=2$, we obtain the standard NMOS

b) in saturation $\frac{\partial i_D}{\partial v_{GS}} = n k (v_{GS} - V_{th})^{n-1} (1 + \lambda v_{DS}) \Rightarrow g_m = \frac{n I_D}{(v_{GS} - V_{th})}$

$$\frac{\partial i_D}{\partial v_{GS}} = k (v_{GS} - V_{th})^n \lambda \Rightarrow g_o = \frac{\lambda I_D}{(1 + \lambda v_{DS})}$$

Equivalent circuit

