
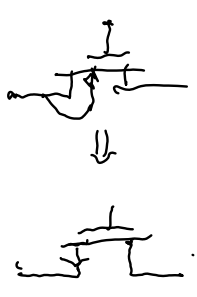
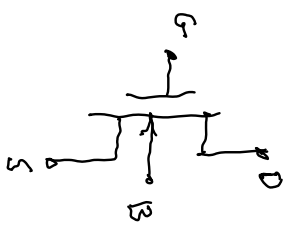


N channel MOS

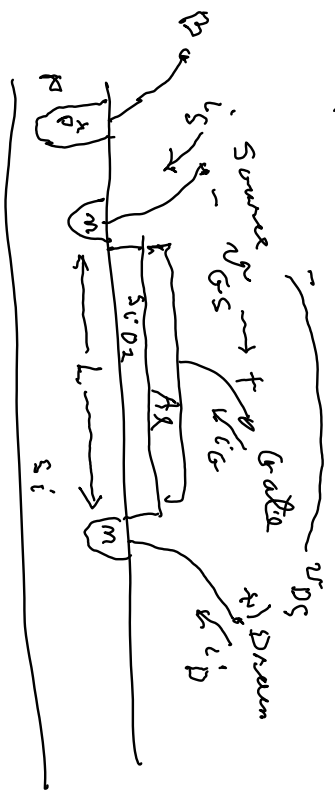


Egn. 3 regions:

off: $i_D = 0$ $V_{GS} < V_{T0} = \text{threshold}$

saturation: $i_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_{T0})^2 (1 + \lambda V_{DS})$ when $V_{GS} - V_{T0} \leq V_{DS}$ (when $V_{SB} = 0$)
 & $V_{GS} > V_{T0}$

triode = ohmic: $i_D = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_{T0}) (V_{DS} - \frac{1}{2} V_{DS}^2) (1 + \lambda V_{DS})$ when $V_{GS} - V_{T0} > V_{DS}$




Table 5.1

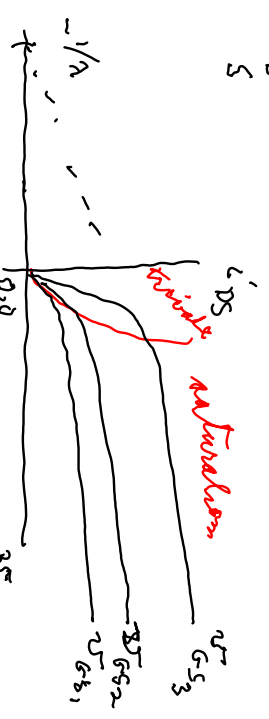


For small v_{DS} (in ohmic range) $i_D \approx \frac{\mu_n C_{ox}}{L} (v_{GS} - V_{TO})^2 v_{DS} = g_m v_{GS} \cdot v_{DS} \Rightarrow$ voltage variable resistor

For large v_{DS} (in saturation)
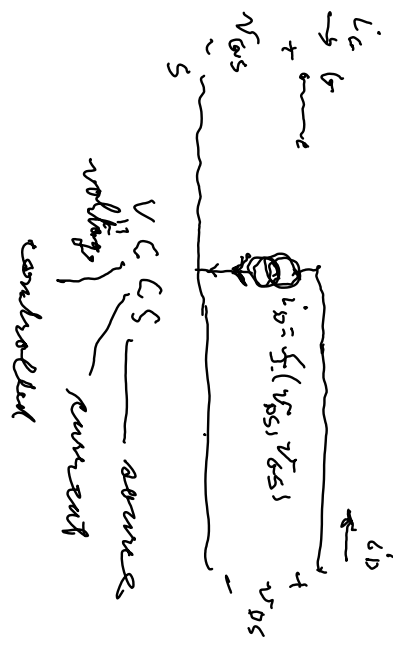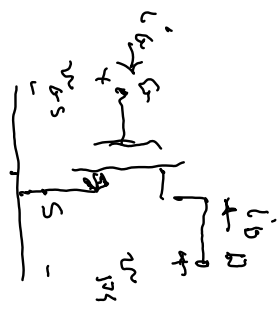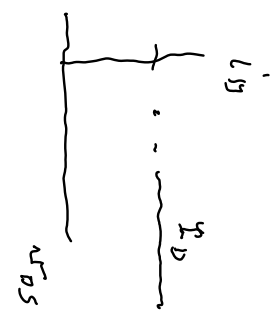
$$i_D \approx \frac{\mu_n C_{ox}}{2L} (v_{GS} - V_{TO})^2 \Rightarrow \text{constant current (for fixed } v_{GS})$$



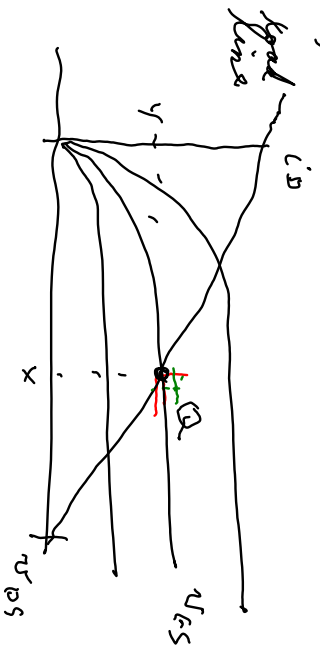Chapter 7, p. 385 \Rightarrow Q point = Bias



Taylor series

$$f(x, y) = z = f(x, y) +$$

$$\frac{\partial f}{\partial x} (x-x) + \frac{\partial f}{\partial y} (y-x)$$

$$+ \left\{ \frac{\partial^2 f}{\partial x^2}, \frac{\partial^2 f}{\partial y^2}, \frac{\partial^2 f}{\partial x \partial y} \text{ etc} \right\}$$

ignores for small signal

$$u_{GS} = V_{GS}$$

$$u_{DS} = V_{DS}$$

$$\uparrow$$

$$Bias = DC \text{ values}$$