


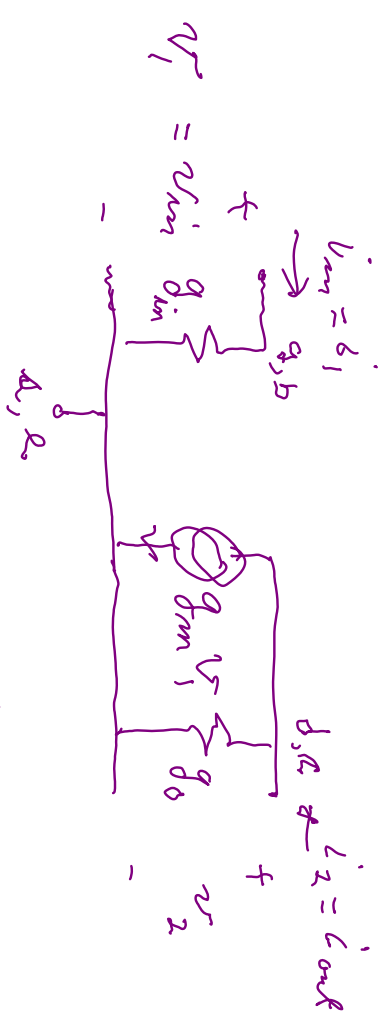
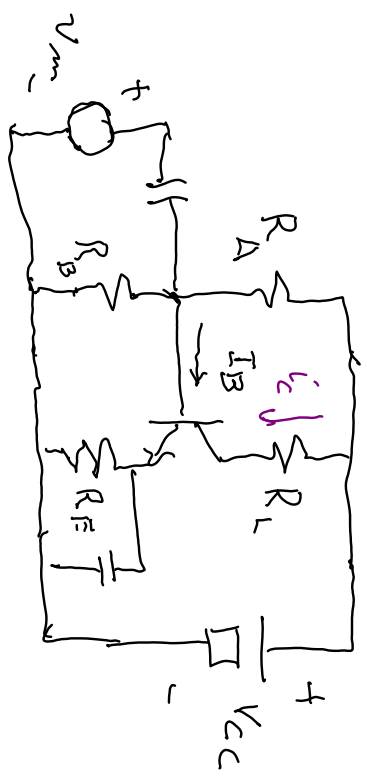
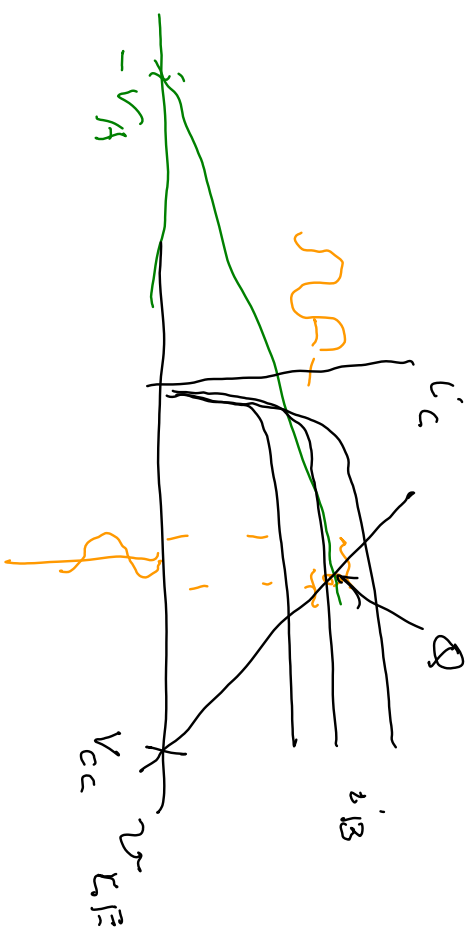



Bias for BJT

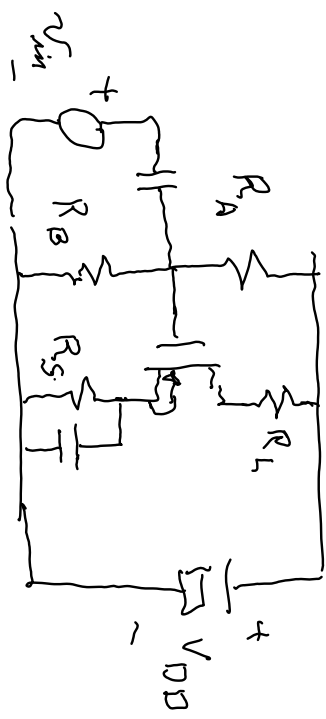

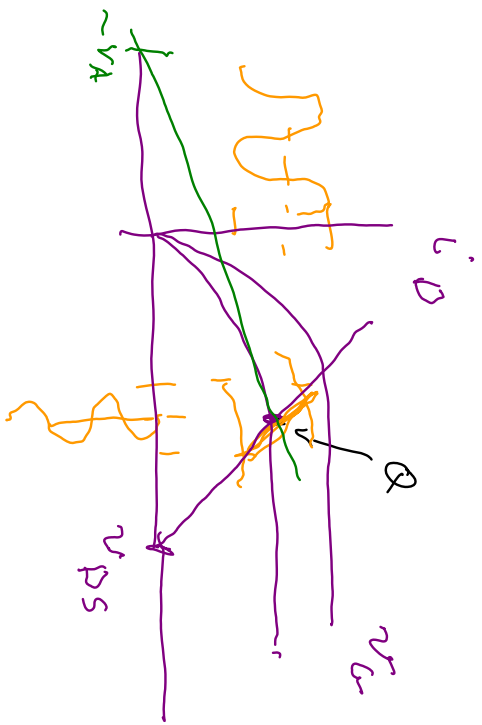$g_{m1} \approx 0$ MOS
 $g_{m1} = \frac{I_C}{V_T}$ BJT
 $g_{m1} = \frac{I_D}{V_{GS}}$ MOS
 $g_{m1} = \frac{I_C}{V_T}$ BJT
 $g_{m1} = \frac{I_D}{V_{GS}}$ MOS
 $g_{m1} = \frac{I_C}{V_T}$ BJT
 $g_{m1} = \frac{I_D}{V_{GS}}$ MOS
 $V_{GS} = \text{overdrive}$
 $= V_{GS} - V_{T0}$
 $V_T = \frac{kT}{q}$
 $\frac{1}{\lambda} = V_A = \text{Early voltage}$



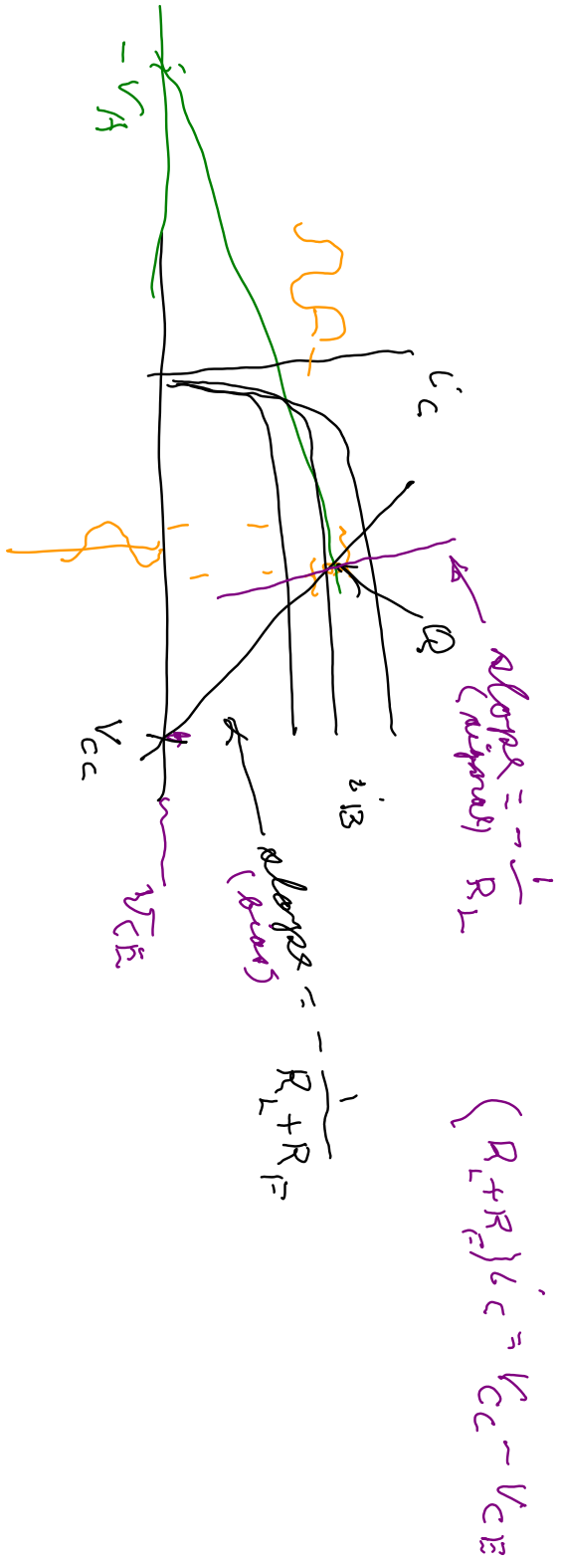

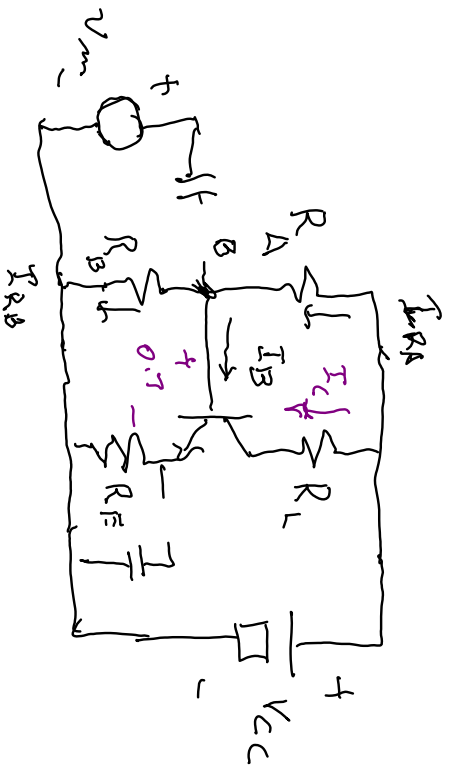

choose $R_A \approx R_B$ to give Q point

$$V_{BE} \approx 0.7$$

know I_C by Q point

β from transistor data

choose R_E & know V_{CC}

$$\text{Q B: } KCL \Rightarrow 0 = I_{R_A} - I_B - I_{R_B} \quad (1)$$

$$I_B = I_C / \beta$$

$$\text{or } R_B > V_{R_B} \approx R_B I_{R_B} = 0.7 + R_E \cdot \frac{I_C}{\beta} \quad (2)$$

$$\text{or } R_A \approx R_B, V_{CC} = R_A I_{R_A} + R_B I_{R_B} \quad (3)$$

$$(1): I_{R_A} = I_{R_B} + I_{R_B} \Rightarrow r R_A \Rightarrow R_A I_{R_A} = R_A \frac{I_C}{\beta} + R_A I_{R_B} \quad (1')$$

$$\text{into (3): } V_{C_C} = R_A \frac{I_C}{\beta} + R_A I_{R_B} + R_B I_{R_B} \approx R_A \frac{I_C}{\beta} (R_A + R_B) I_{R_B} \quad (3')$$

$$\text{from (2): } I_{R_B} = G_{R_B} (0.7 + R_E I_C / \alpha) \quad G_{R_B} = 1/R_B \quad \text{K}_{R_B} \text{ constant}$$

$$\text{into (3)} \quad V_{C_C} = R_A \frac{I_C}{\beta} + (R_A + R_B) G_{R_B} (0.7 + R_E I_C / \alpha) = R_A \frac{I_C}{\beta} + \left(\frac{R_A}{R_B} + 1 \right) (0.7 + R_E \frac{I_C}{\alpha})$$

$$\text{can set } \frac{R_A}{R_B} = K_{R_B} \text{ & solve for } R_A$$

unknown