
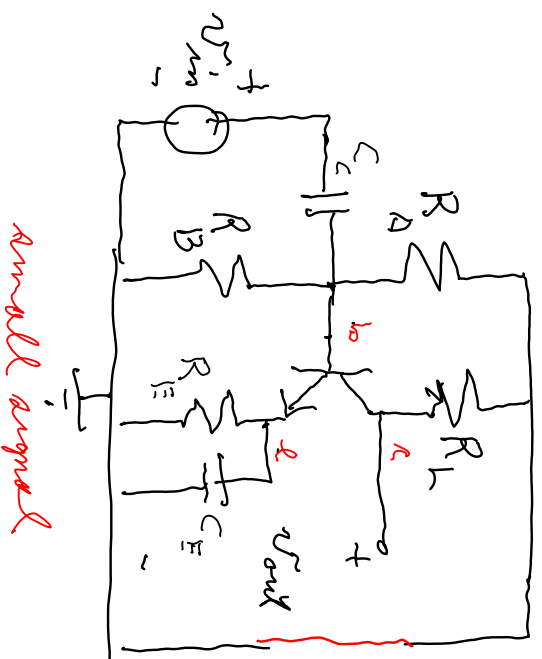


$$R_A = \frac{\beta}{I_C} \left[V_{CC} - (1 + \beta \frac{R_B}{R_A}) (V_{BE} + R_E I_C) \right]$$

0.7V


← Resistor choice for BJT

$$k_{AB} = \frac{R_B}{R_A}$$

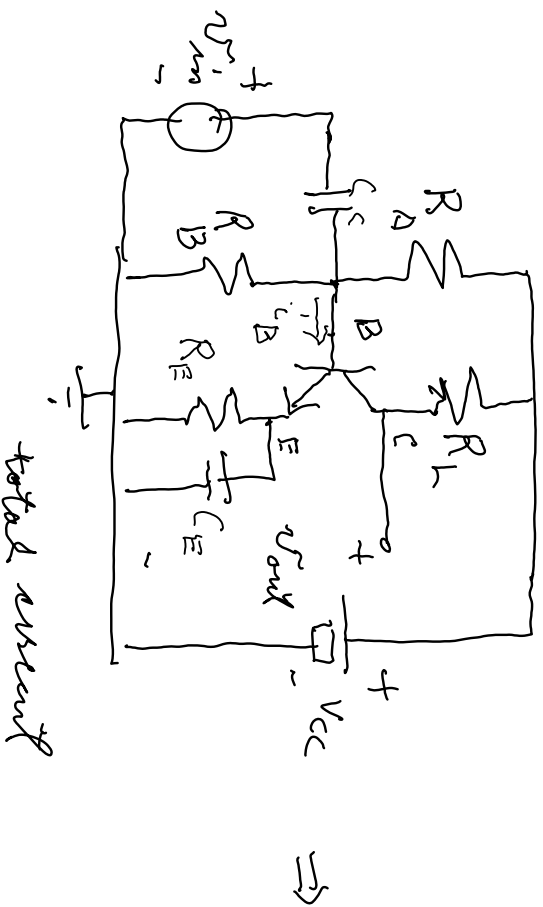


small signal

common emitter

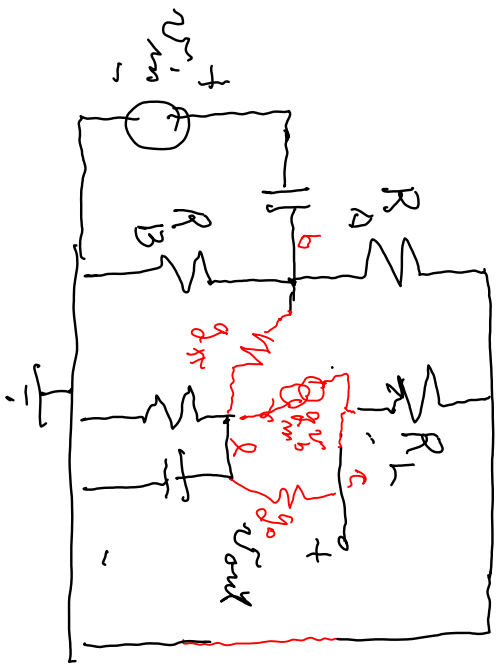

$$i = Y v$$
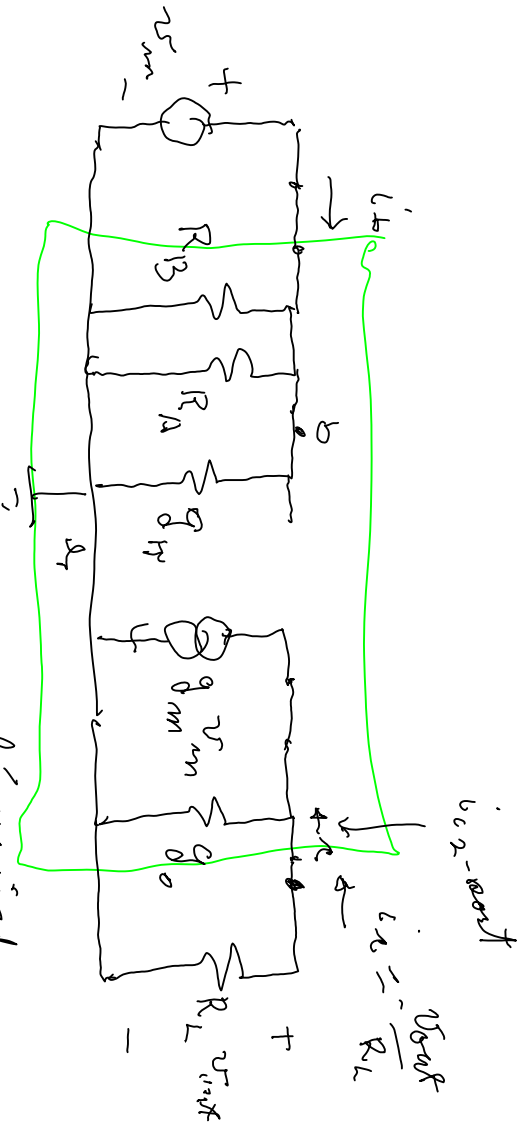
$$\begin{bmatrix} i_b \\ i_c \end{bmatrix} = \begin{bmatrix} g_A + (G_A + G_B) \\ g_m \\ g_o \end{bmatrix} \begin{bmatrix} v_b \\ v_c \end{bmatrix}$$



mid frequency band

linearisiert



$$\begin{bmatrix} v_{in} \\ v_{out} \end{bmatrix} \begin{bmatrix} 0 \\ g_o \end{bmatrix}$$

$$i_e \approx g_m v_{in} + g_o v_{out} = -v_{out}/R_L \quad \text{by KCL}$$

$$A_{v\sigma} = \frac{v_{out}}{v_{in}} \Rightarrow g_m v_{in} = - (g_o + G_L) v_{out}$$



$$\frac{v_{out}}{v_{in}} = \frac{-g_m}{g_o + G_L} \quad R_L \rightarrow g_m/G_L = -g_m R_L = -\frac{I_C}{V_T} R_L \approx 0$$
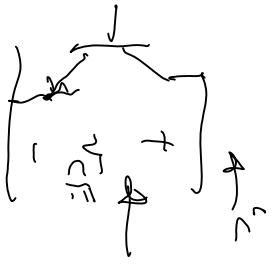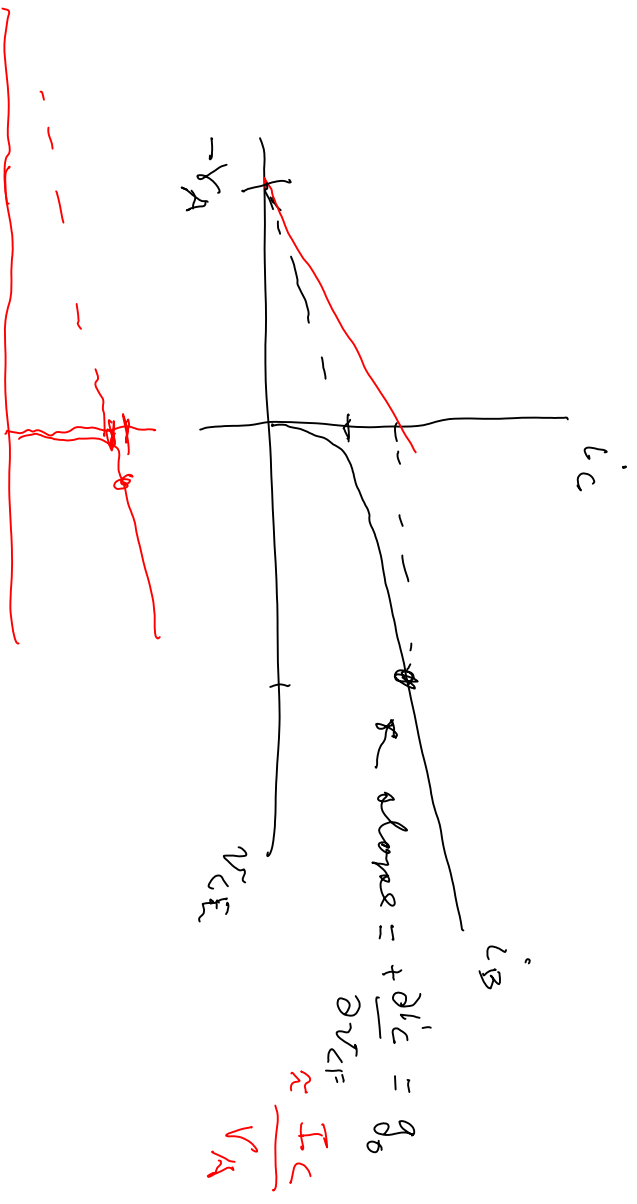
$$\begin{aligned} I_C &= 2.6 \text{ mA} & g_m &= \frac{2.6}{26} = 0.1 \text{ if we choose } R_L = 10 \text{ k}\Omega \\ V_T &= 26 \text{ mV} & & \text{then } A_{v\sigma} = -0.1 \times 10 \times 10^3 = 10^3 \end{aligned}$$



output
 see g_o as
 small signal
 conductance

grounded collector

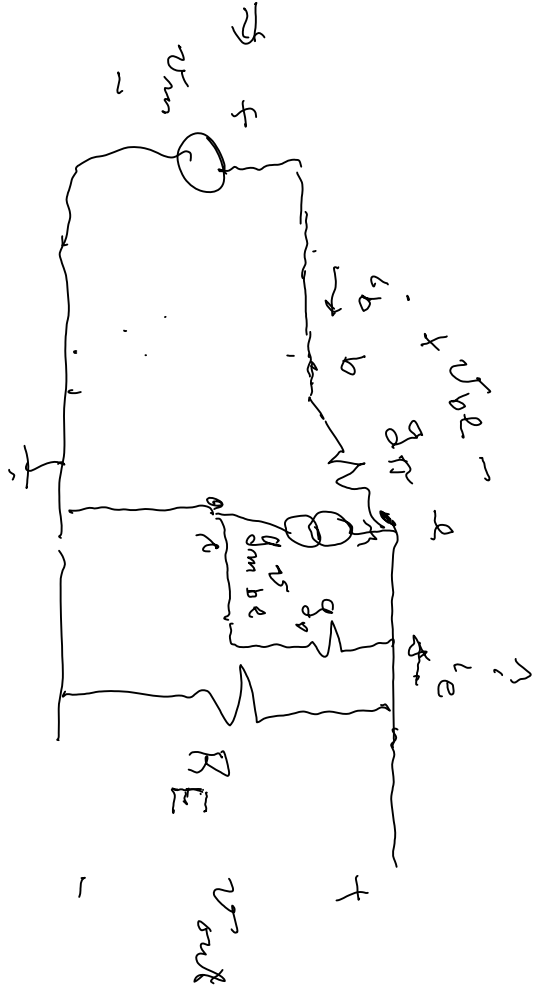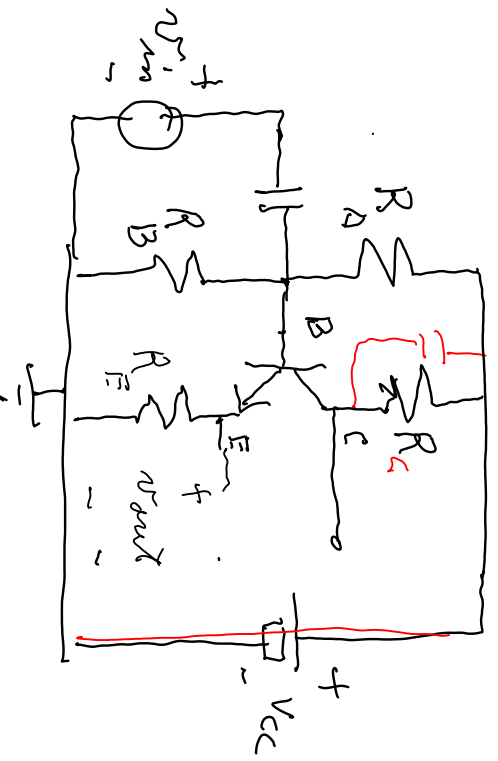

$$v_b' = g_m v_{be} \quad ; \quad v_{out} = -R_E i_c \quad ; \quad KCL: 0 = i_b + g_m v_{be} - g_o v_{out}$$


$$KCL \quad ; \quad \Rightarrow \quad 0 = g_m v_{be} + g_m v_{be} - g_o v_{out}$$

$$KVL \Rightarrow 0 = -V_{in} + V_{be} + V_{out} \Rightarrow V_{be} = V_{in} - V_{out}$$

$$0 = (g_{\pi} + g_m) [V_{in} - V_{out}] - g_d V_{out} \Rightarrow (g_o + g_{\pi} + g_m) V_{out} = (g_{\pi} + g_m) V_{in}$$


$$A_{vs} = \frac{V_{out}}{V_{in}} = \frac{(g_{\pi} + g_m)}{(g_o + g_{\pi} + g_m)} \approx \frac{g_m}{g_m} \approx 1 \Leftarrow \text{gain of ground collector} \\ = \text{emitter follower}$$


current mirror

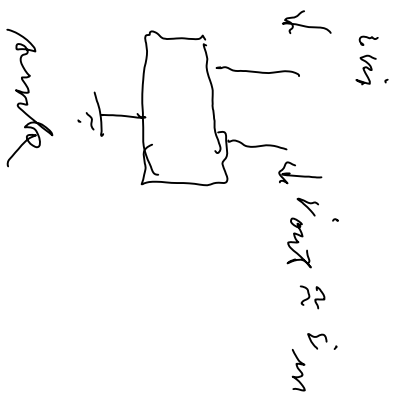

\Rightarrow used to replicate loads


from sources.

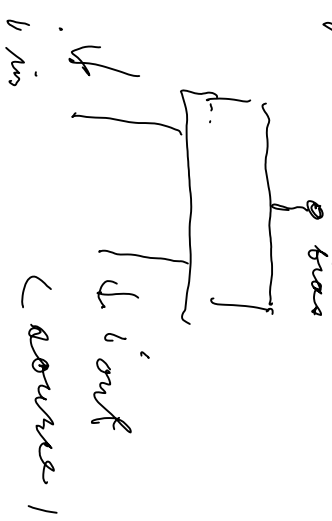

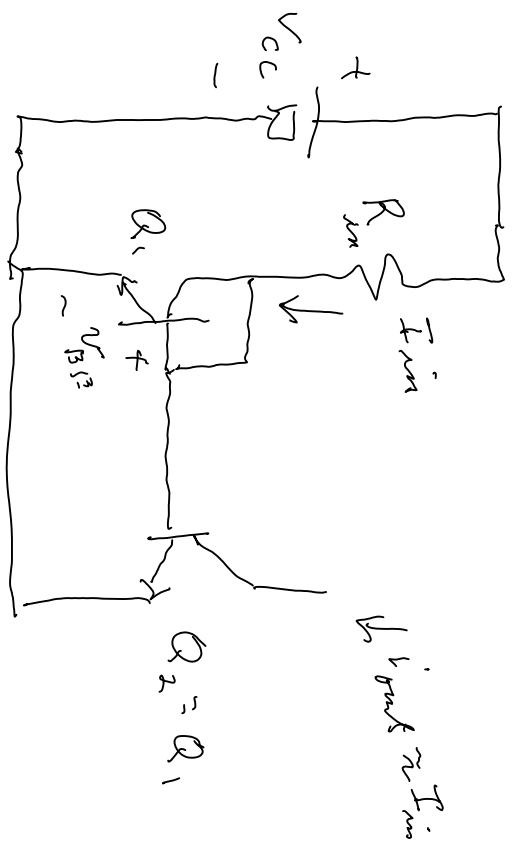


$$R_m I_{in} = V_{cc} - V_{BE}$$

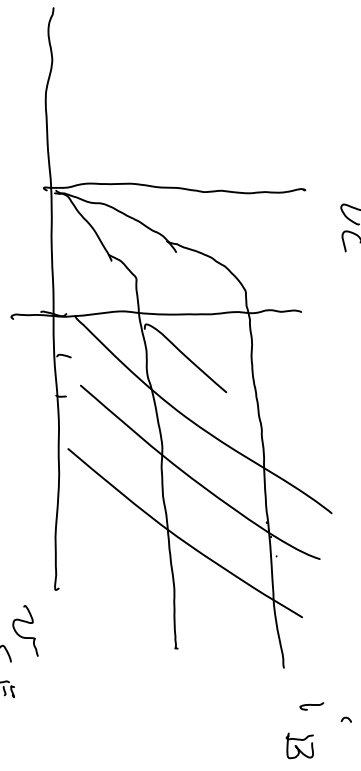
$$\Rightarrow R_m = \frac{V_{cc} - V_{BE}}{I_{in}}$$



used to be in forward active region

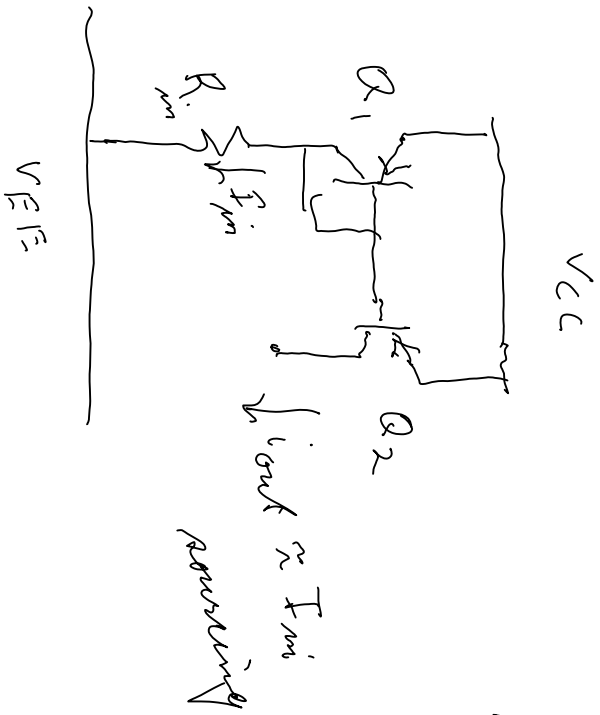
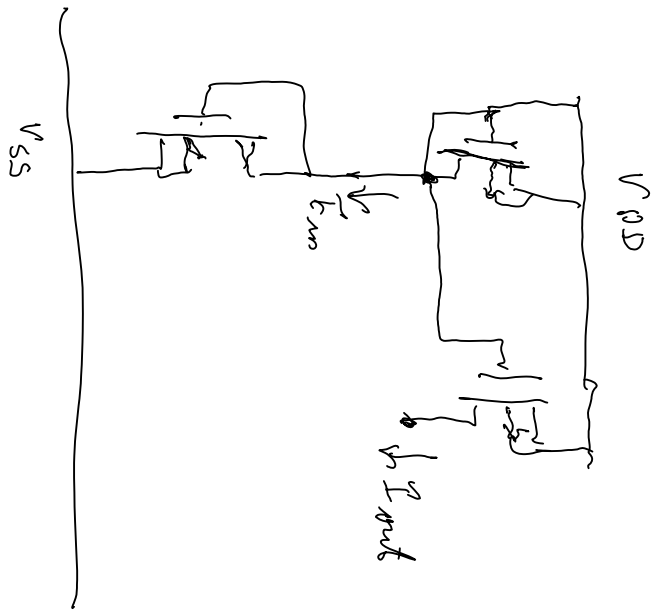
$$R'_{in} = \frac{(V_{CC} - V_{BE}) - (V_{BE})}{I_{in}}$$



[Handwritten signature]

