


BJT $f_T \Rightarrow$ p. 720, eq. 10.41, C_{π} & C_{μ} p. 718

MOS, C_g


C_{gR}

C_{gd}

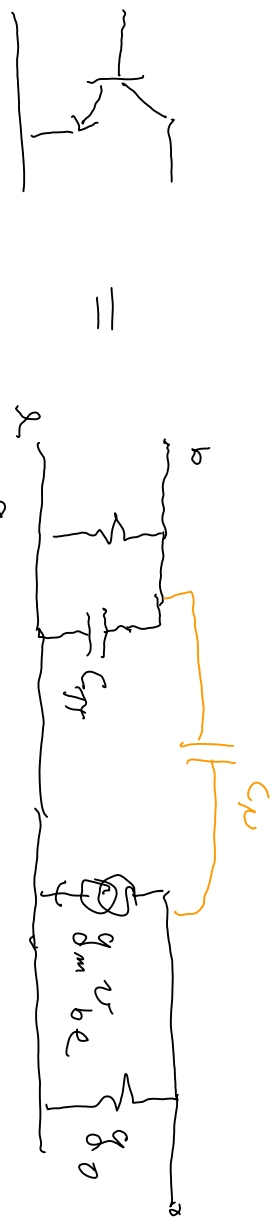Differential pairs, chapters 9, MOS, p. 596, 606
BJT, p. 614, 619



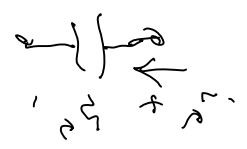
$$g_{\pi} \approx g_{\mu} + \beta C_{\mu}$$



$$i_c = C \frac{dv_c}{dt}$$

$$y = \begin{bmatrix} g_{\pi}(\alpha) + \beta C_{\mu} & -\beta C_{\mu} \\ g_{\mu} + \beta C_{\mu} & g_o + \beta C_{\mu} \end{bmatrix} ; i_c = y v_c$$
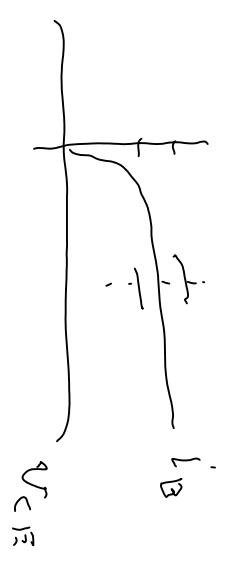
$$v_c = \begin{bmatrix} v_{be} \\ v_{ce} \end{bmatrix}$$



if $v_c = V_c e^{At}$

$$I_c e^{At} = i_c = \frac{d}{dt} v_c = V_c A e^{At} = \beta v_c$$

$$e^{At} = e^{(g + j\omega)t} = e^{gt} e^{j\omega t}, \quad j = \sqrt{-1}$$

if $\sigma = 0$ $e^{At} = e^{j\omega t} = \cos \omega t + j \sin \omega t$
 $\omega = 2\pi f$

To get $\beta = \frac{i_c}{i_b}$,

$$\begin{bmatrix} i_b \\ i_c \end{bmatrix} = \begin{bmatrix} g_\pi + A(C_\pi + C_\mu) & -A C_\mu \\ g_m - A C_\mu & g_o + A C_\mu \end{bmatrix} \begin{bmatrix} v_{b2} \\ v_{c2} \end{bmatrix} \leftarrow v_{c2} = 0 \text{ to get } \beta$$

$$\begin{aligned} i_b &= g_{\pi1} v_{b2} & \text{if } v_{c2} = 0 \\ i_c &= g_{\pi2} v_{b2} & v_{c2} \neq 0 \end{aligned} \Rightarrow \frac{i_c}{i_b} = \frac{g_{\pi2}}{g_{\pi1}} = \frac{g_m - A C_\mu}{g_\pi + A(C_\pi + C_\mu)} \quad \text{eq. (10.41)}$$


(cancels)

$$\begin{aligned} \beta_d &= \beta @ DC \\ &= \frac{g_m}{g_m / \beta_d} \end{aligned}$$

for f_T , this is when $|\beta(j\omega_f)| = 1$

$$\frac{g_m}{g_\pi} \cdot \frac{1}{1 + \frac{A(C_\pi + C_\mu)}{g_\pi}} = \beta_d \frac{1}{1 + \frac{A(C_\pi + C_\mu)}{g_m}}$$
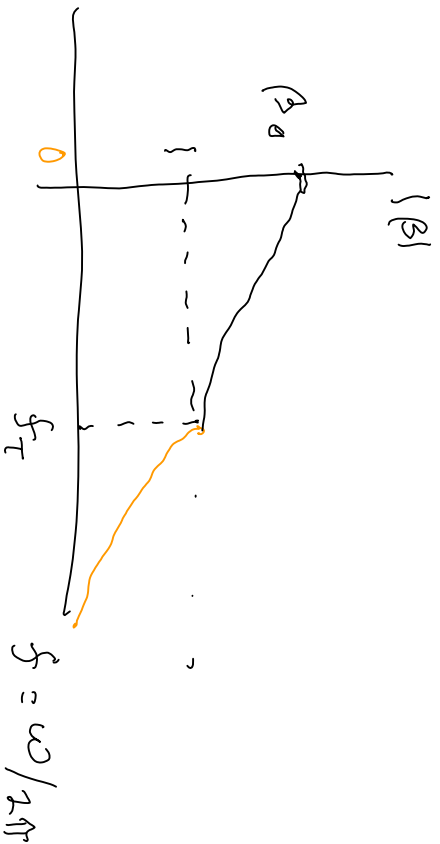
$$g_m \cdot \frac{1}{1 + \frac{A(C_\pi + C_\mu)}{g_m}}$$



$$\text{Aussage } f_T \Rightarrow \left| 1 + j\omega \frac{(C_T + C_P)}{g_T} \right| = \beta_0$$



$$\omega_T \frac{(C_T + C_P)}{g_T} \approx \beta_0$$

$$f_T = \frac{\omega_T}{2\pi} \approx \frac{g_T \times \beta_0}{C_T + C_P} = \frac{g_m}{C_T + C_P}$$

Eq. (10.41)

$$\left| \frac{\beta_0}{1 + j\omega \frac{(C_T + C_P)}{g_T}} \right| = 1 \Rightarrow \frac{\beta_0}{\sqrt{1 + \omega^2 \frac{(C_T + C_P)^2}{g_T^2}}} = 1 \Rightarrow 1 + \omega^2 \frac{(C_T + C_P)^2}{g_T^2} = \beta_0^2 \Rightarrow \omega_T \uparrow$$

MOS

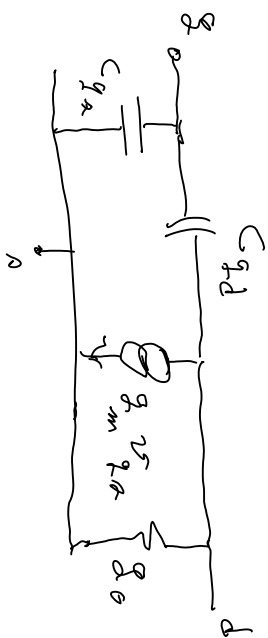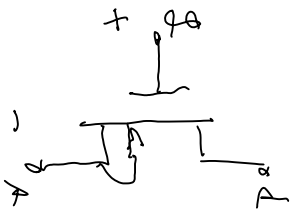


$$C_{gA} + C_{gD} = C_g = \text{gate capacitor} \approx$$

$$W \times L \times \frac{\epsilon_{SiO_2}}{t} = W \times L \times C_{ox}$$

Thickness of oxide

gate area


unit area capacitance

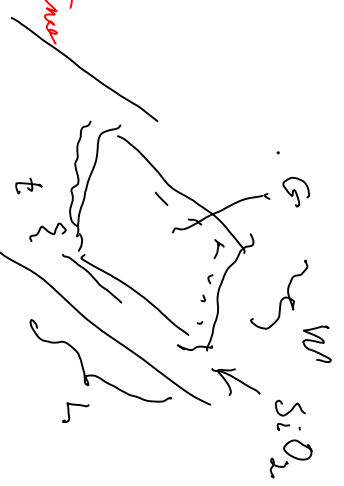

$$C_{gA} = \frac{1}{2} C_g = \frac{2}{3} C_g$$

$$C_{gD} = \frac{1}{2} C_g = \frac{1}{3} C_g$$

Annotation *triode*

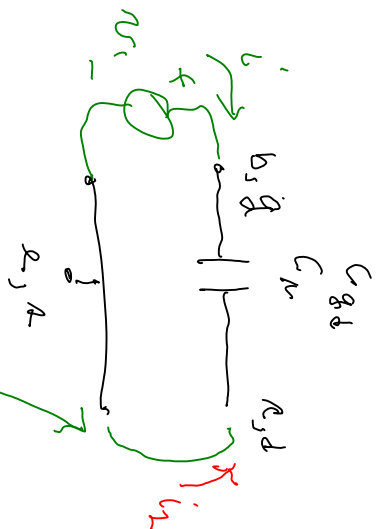

$$y_{11} = \left. \frac{i_i}{v_i} \right|_{v_2=0}$$

a short


$$y = \begin{bmatrix} \\ \end{bmatrix} = \begin{bmatrix} A C_p & -A C_p \\ -A C_p & A C_p \end{bmatrix} \text{ or } \begin{bmatrix} A C_{gd} & -A C_{gd} \\ -A C_{gd} & A C_{gd} \end{bmatrix}$$

$$i = A C \cdot v \Rightarrow i_1 = A C p, v_1 \text{ or } A C q_2$$

$y_{11} = y_{22}$ & $y_{12} = y_{21}$ by symmetry \parallel

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} = \frac{v_i}{v_1} = -A C p$$

$$= y_{12}$$

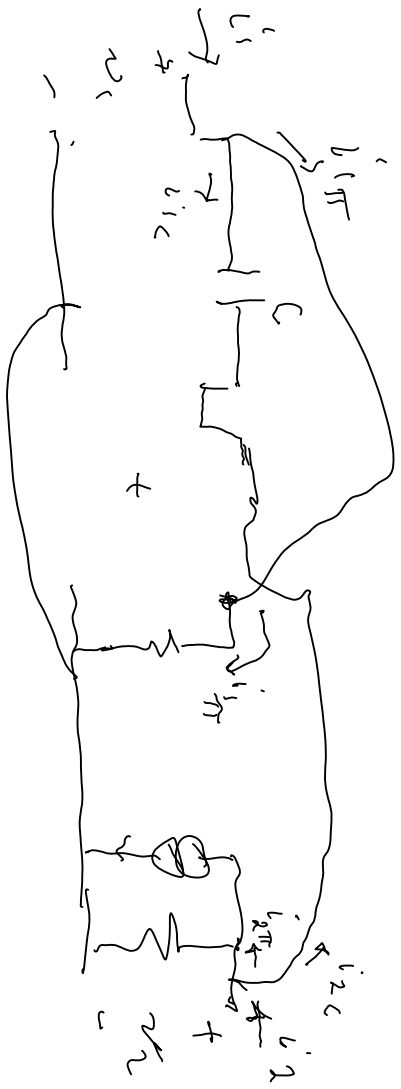

$$\Rightarrow Y = \begin{bmatrix} Y_1 \\ Y_2 \end{bmatrix}, \quad i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$(i_c + i_{\pi}) = i = (Y_C + Y_{\pi}) \cdot u \Rightarrow Y = Y_C + Y_{\pi}$$

$$\Downarrow$$

$$i = Y \cdot u$$

$$\parallel$$


$$\begin{bmatrix} Y_C & -Y_C \\ -Y_C & Y_C \end{bmatrix} + \begin{bmatrix} Y_{\pi} & 0 \\ 0 & 0 \end{bmatrix}$$


$$Y = \begin{bmatrix} g_{\pi} + \mu C_{\mu} & -\mu C_{\mu} \\ g_m - \mu C_{\mu} & g_o + \mu C_{\mu} \end{bmatrix} \quad \left. \begin{array}{l} \text{for BJT} \\ \text{or } C_{\mu} \rightarrow C_{gd} \end{array} \right\} \quad \left. \begin{array}{l} \text{for MOS} \\ g_{\pi} \rightarrow C_{gs} \cdot \omega \end{array} \right\}$$

differential pairs \Rightarrow OTA = operational transconductance amplifiers


(g_m = mutual conductance = transconductance)
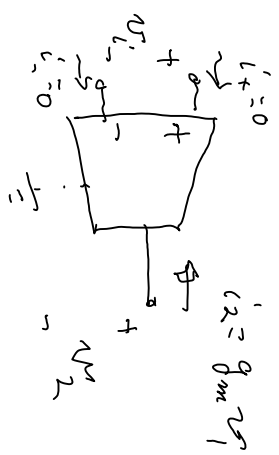
$$\text{OTA} \Rightarrow Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \Rightarrow$$




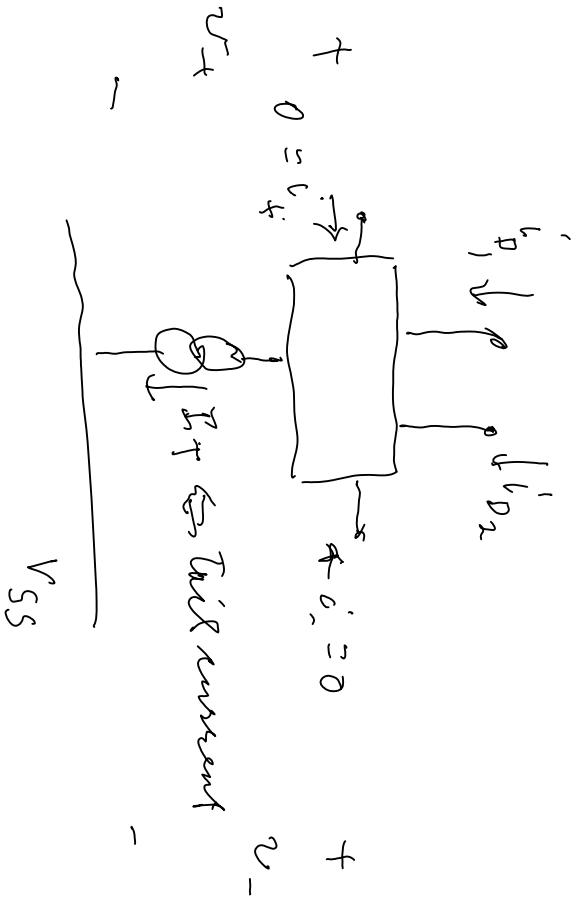

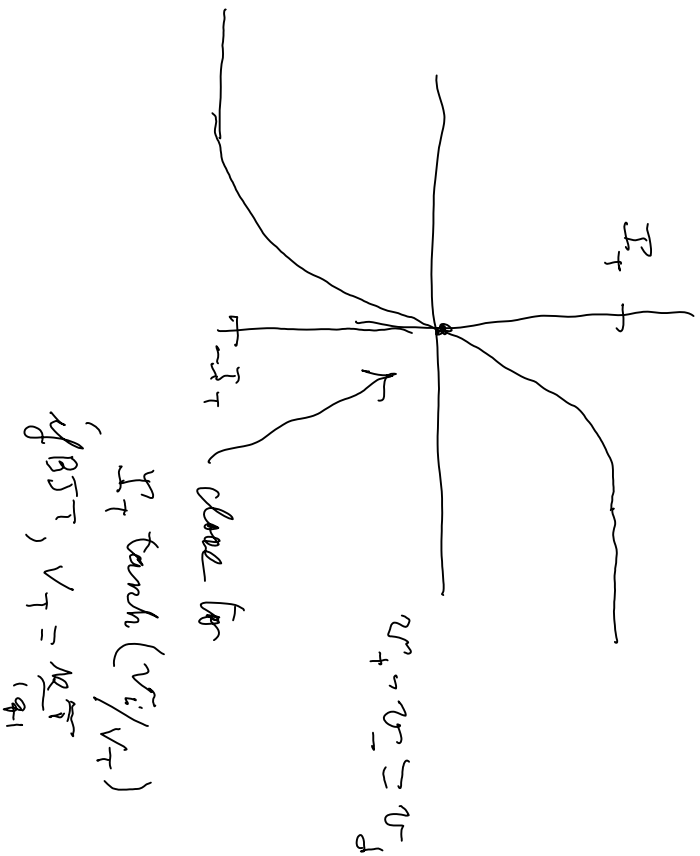by KCL: $i_{D1}' + i_{D2}' = I_T$
 $i_{D2}' = i_{D1}'$



BJT
diff. pair

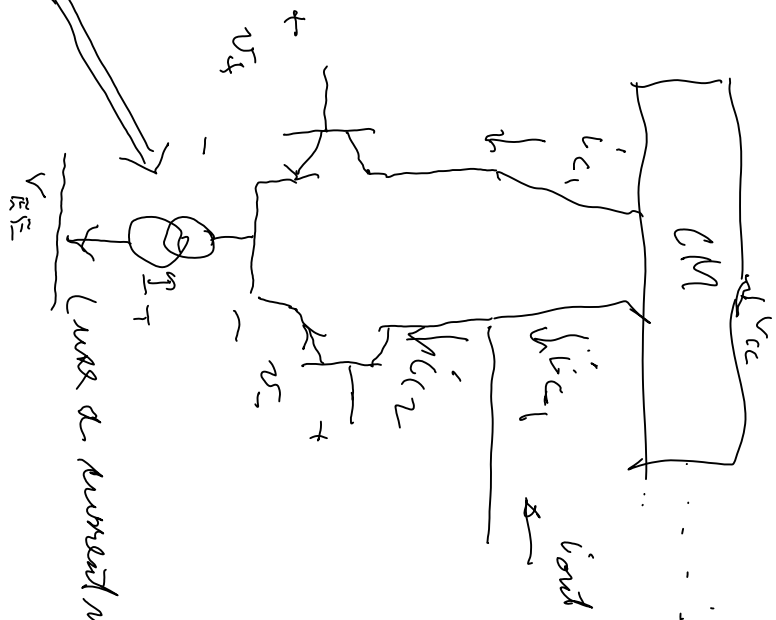

device
 $i_B = 0$
 not get
 i_B from
 generating

device a
 great I_T
 get from
 substrate
 mirrors

$i_{out} = I_T \tanh\left(\frac{v_T - v_-}{2v_T}\right)$

$\approx I_T \tanh\left(\frac{v_d}{2v_T}\right) = -i_{out}$
 (red underline) $\approx \frac{I_T}{2} \frac{e^{(v_T - v_-)/2v_T} - e^{-(v_T - v_-)/2v_T}}{e^{(v_T - v_-)/2v_T} + e^{-(v_T - v_-)/2v_T}}$

ratio $\approx -i_{out} = \frac{e^{v_T/v_T} - e^{-v_-/v_T}}{e^{v_T/v_T} + e^{-v_-/v_T}}$

$i_{C1} = \alpha I_S e^{v_+/v_T}$; $i_{C2} = \alpha I_S e^{v_-/v_T}$
 $i_{out} \approx i_{C1} - i_{C2} = \alpha I_S (e^{v_+/v_T} - e^{-v_-/v_T})$
 $I_T = i_{C1} + i_{C2} = \alpha I_S (e^{v_+/v_T} + e^{-v_-/v_T})$

Linearized @ $v_D = 0 \Rightarrow \left. \frac{d(-i_{out})}{dv_D} \right|_{v_D=0} = I_T \left(1 - \tanh^2 \left(\frac{v_D}{2V_T} \right) \right) \times \frac{1}{2V_T} \Bigg|_{v_D=0} = \frac{I_T}{2V_T} = g_m$ of OTA
 as $\tanh(0) = 0$

$\therefore g_m = \frac{I_T}{2V_T}$ is set by the tail current via a current mirror