


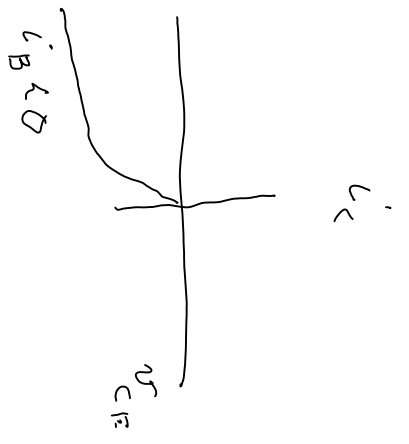
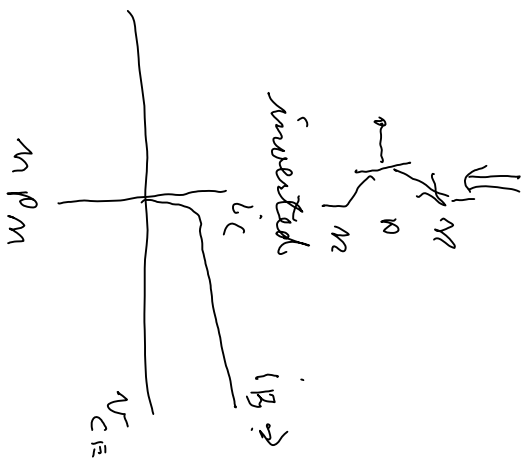


$$\theta = \text{beta} = h_{fe} ; \quad i_c = \beta i_b$$


$$\approx B_R$$

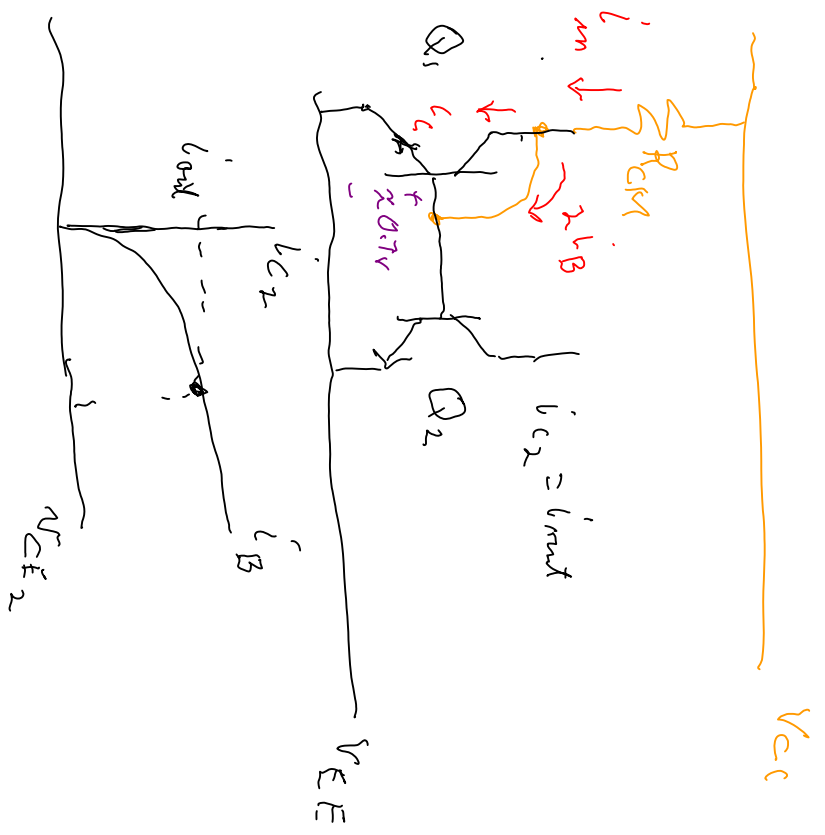

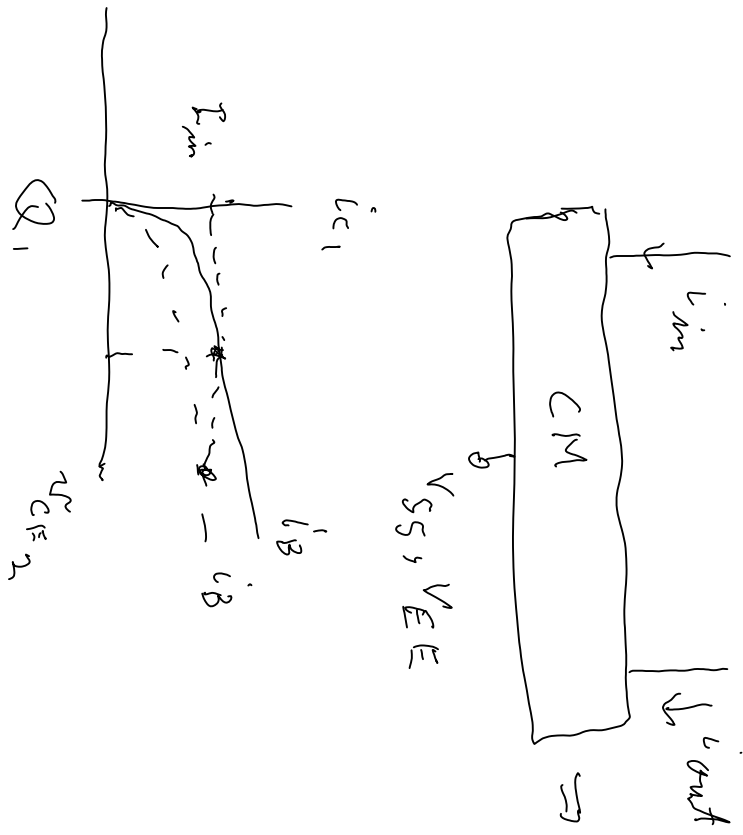

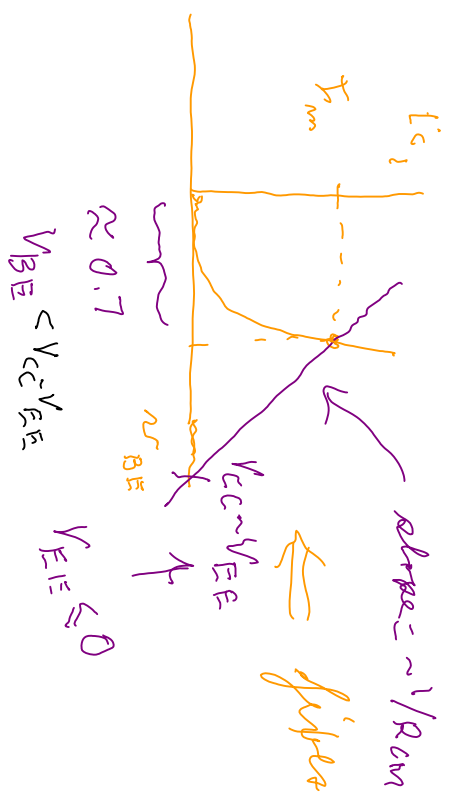


I_{BE} given I_m

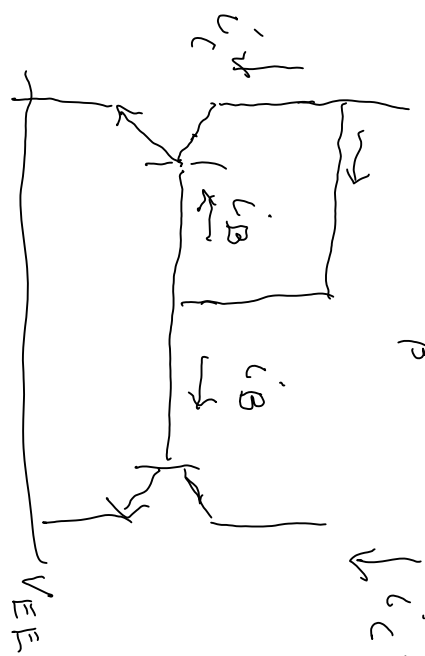


$I_{c_{no}} = I_c + \beta I_B$
 $I_{c_{no}} = I_c + \frac{2}{\beta} I_c$

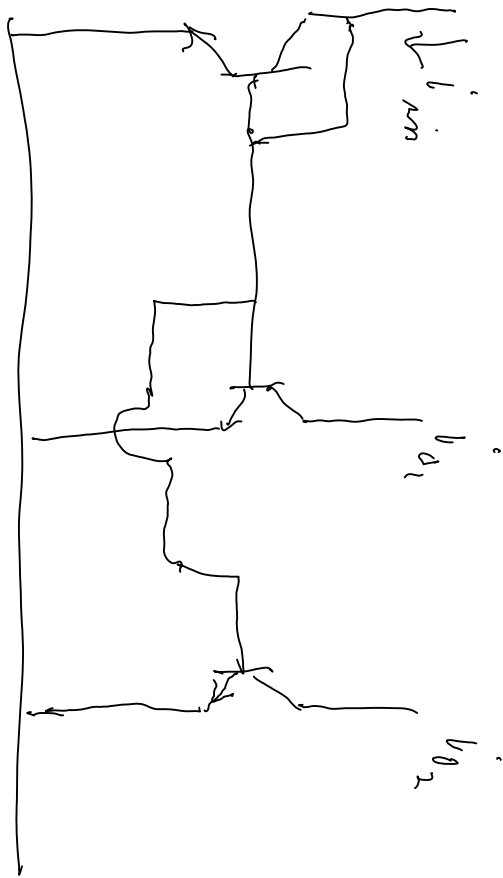
$I_{c_{out}} = I_c$
 $I_{c_{out}} = \beta I_B$
 $I_{c_{out}} = \frac{I_{c_{no}}}{1 + 2/\beta} \approx I_{c_{no}}$



can send l_1 to memory l_0

OTA2 Buffering

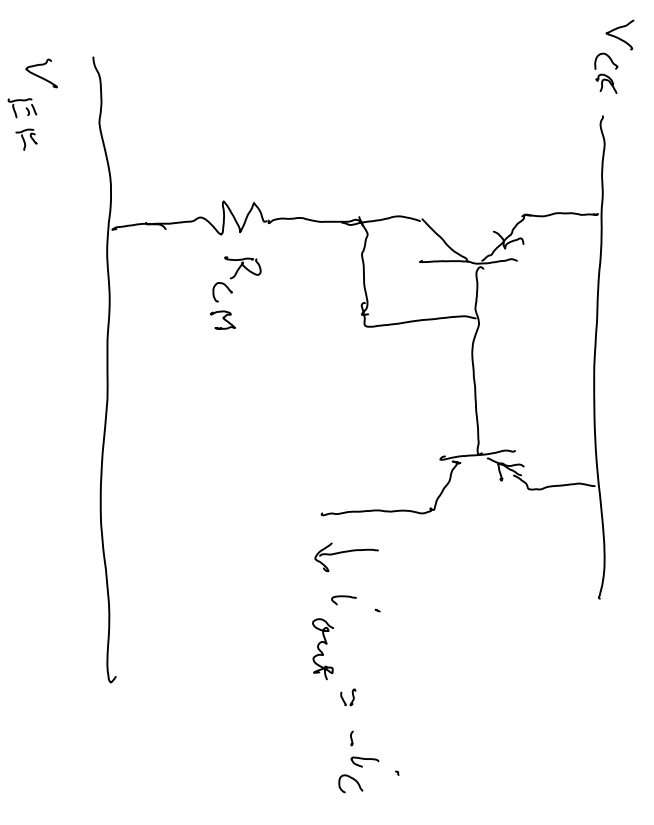


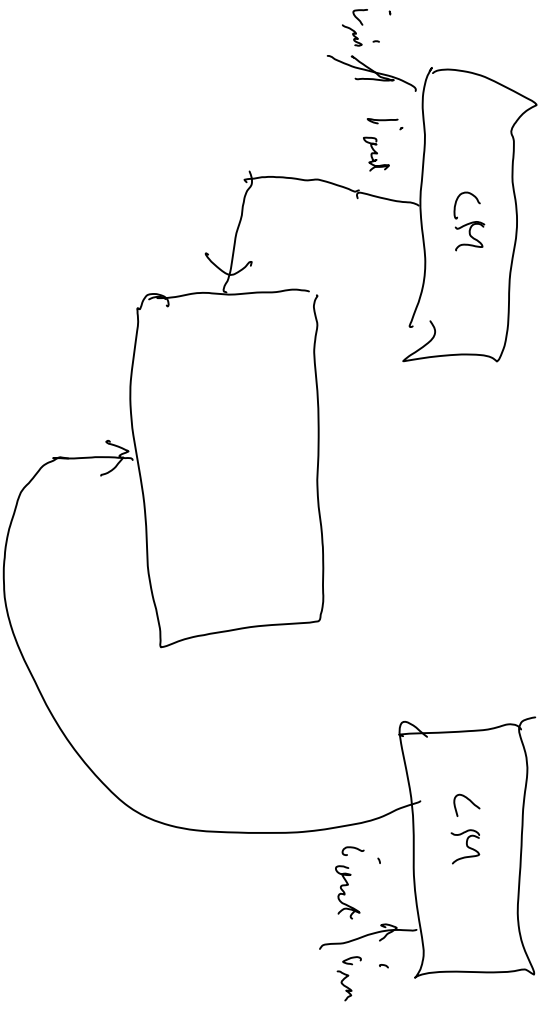


for answering


CE using pnp

for n p n

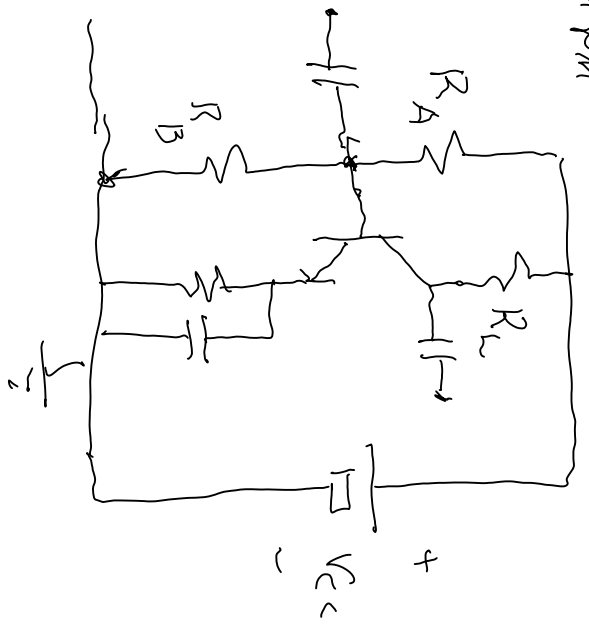

for p n p

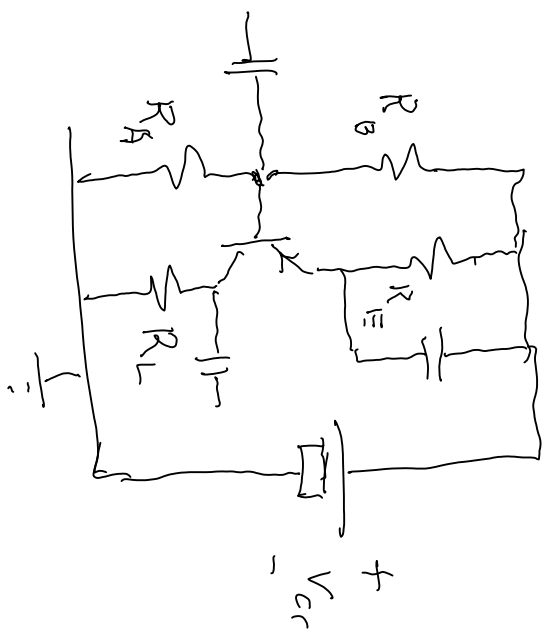

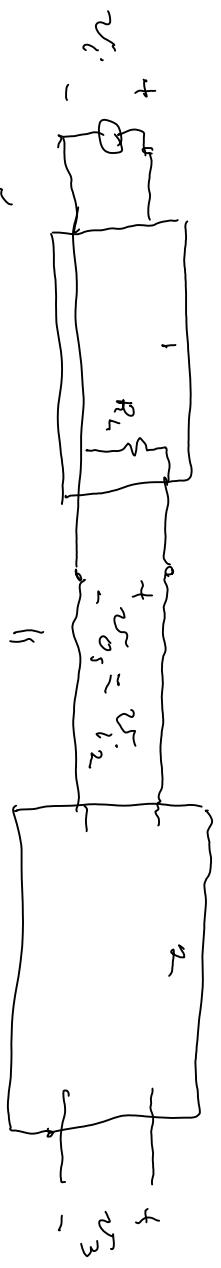

load connection


$$v_3 = -g_{m1} R_{L1}$$

$$\frac{v_3}{v_i} = \frac{v_3}{v_{L1}} \cdot \frac{v_{L1}}{v_i}$$

where v_{L1} is the voltage across R_{L1}

$$= (g_{m1} R_{L1} \text{ loaded})$$

$$\times (-g_{m2} R_{L2})$$

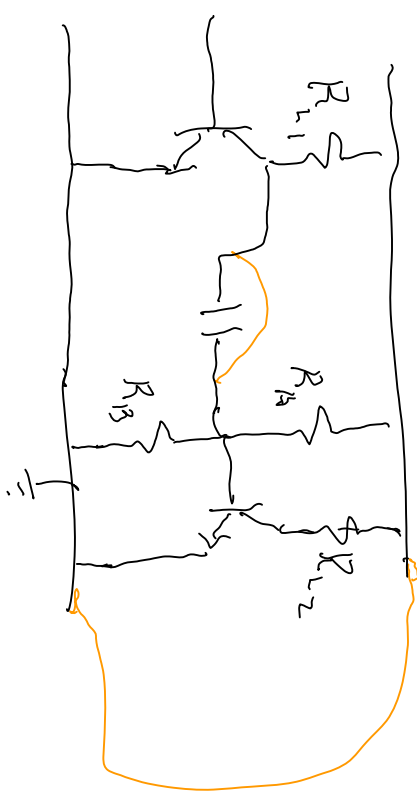



small signal

$$R_{L1} \Rightarrow R_{L1} \text{ in parallel with } \frac{R_A R_B}{R_A + R_B}$$

$R_{L1} \text{ loaded}$

$$R_{L1} \text{ load} = \frac{R_{21} \times \frac{R_A R_B}{R_A + R_B}}{R_{L1} + \frac{R_A R_B}{R_A + R_B}}$$


diff pair \Rightarrow OTA

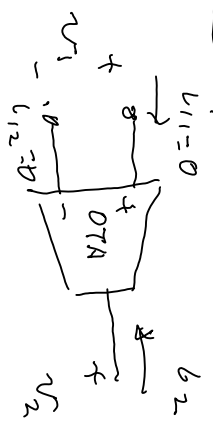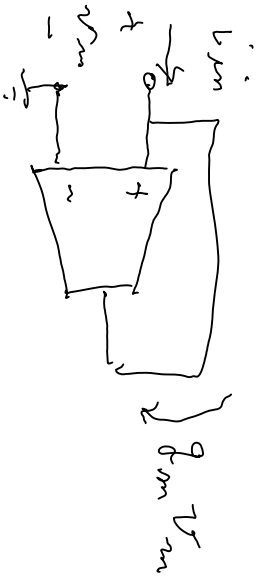


OTA = operational transconductance amplifier
= differential pair with current mirrors load


MOS = p. 646, 9.32
BJT = p. 651, 9.36

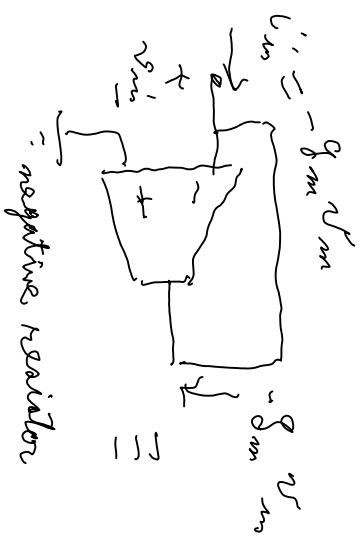
$$Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}; \quad \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



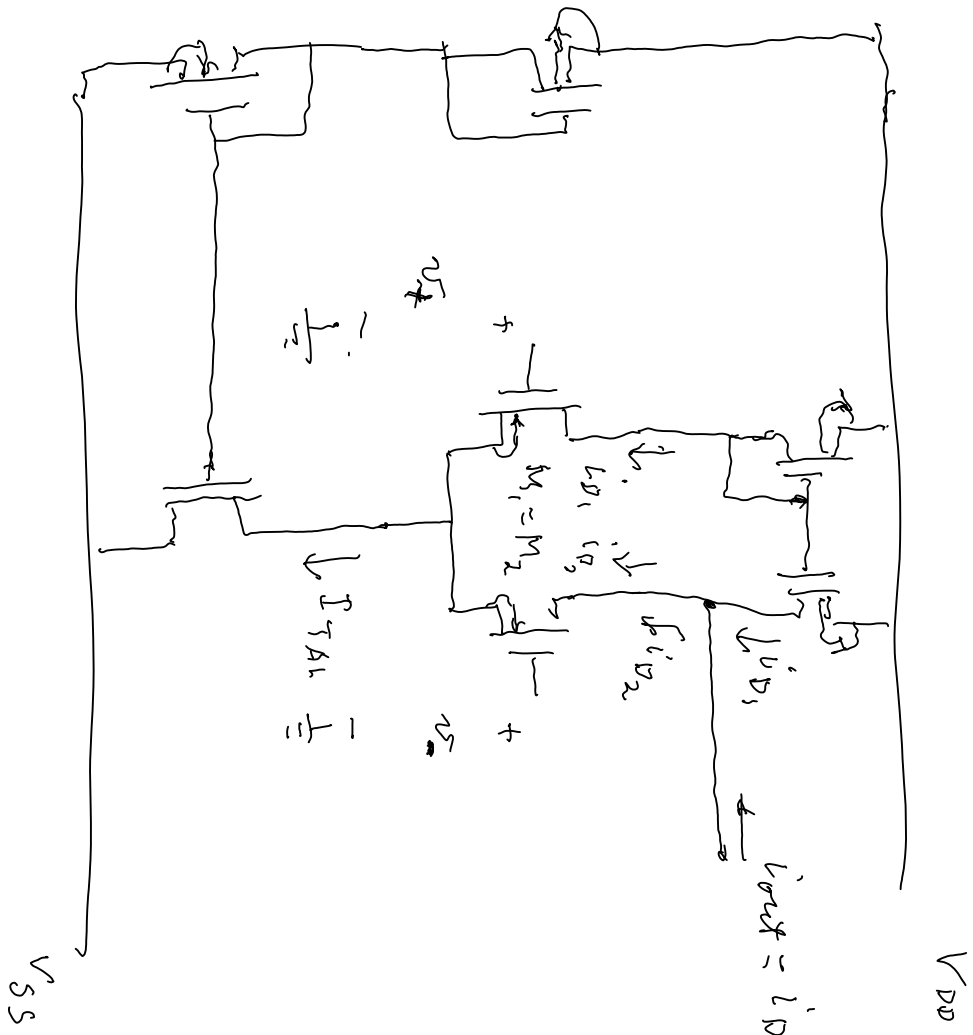

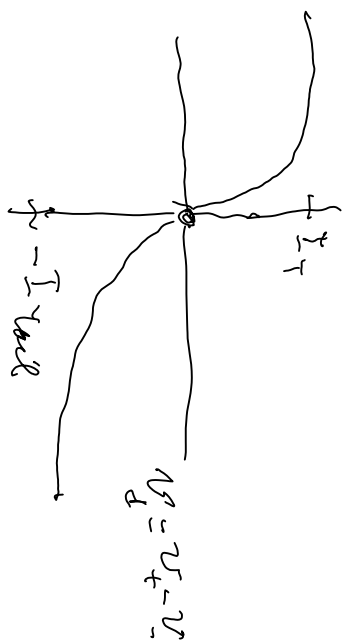V_{DD}
 if $M_1 = M_2 \Rightarrow Q_1 = Q_2$
 \downarrow
 $= -I_T \tanh\left(\frac{v_T^+ - v_T^-}{2v_T}\right)$



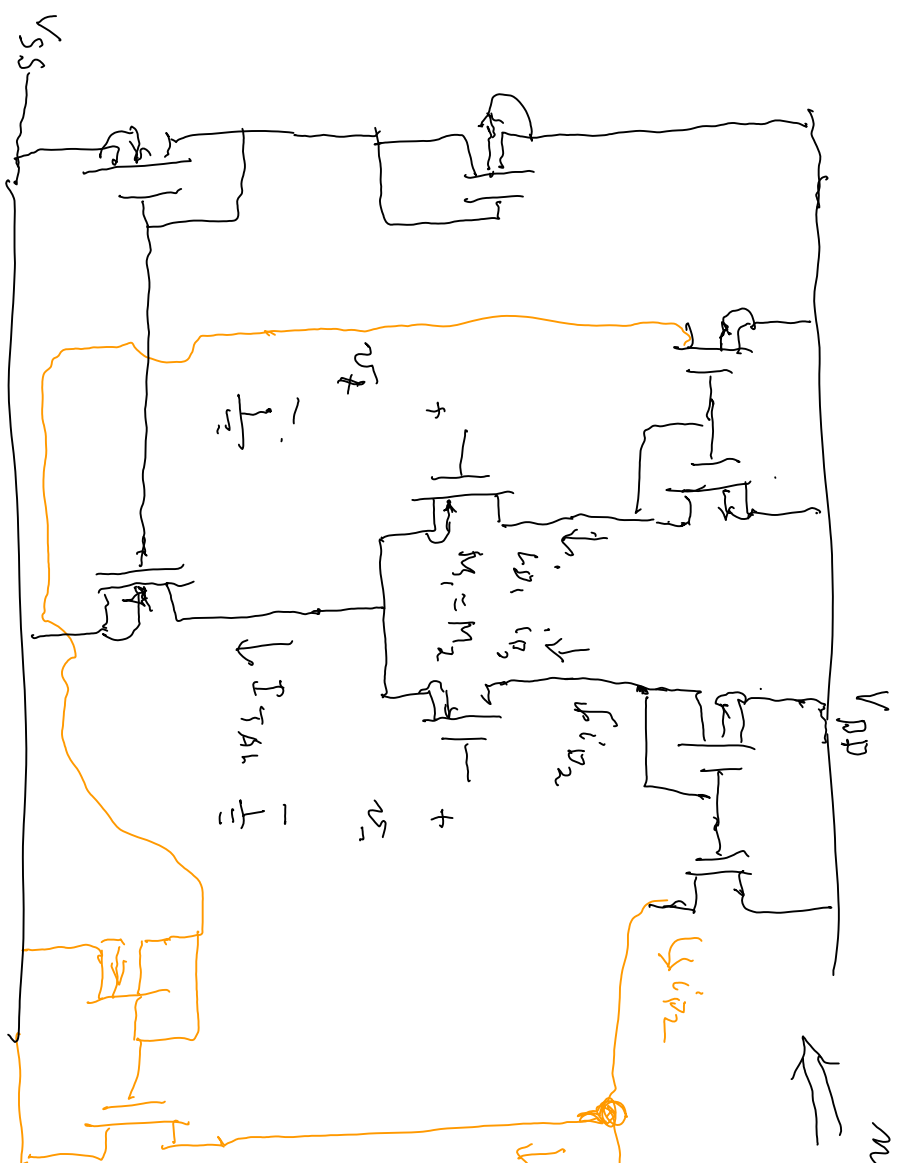

↔ for equal load on M_1 & M_2
 near CM

