

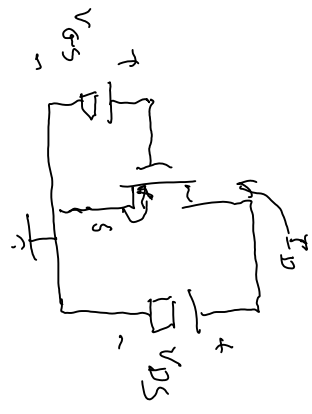


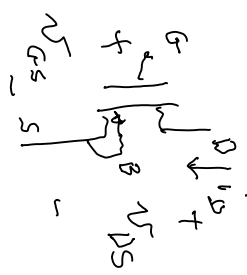dr. saturation  $\approx I_D \approx \frac{K_D}{2} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$




for  $\lambda$  series

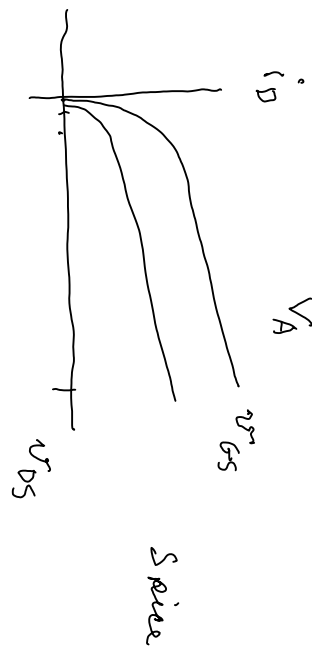$\lambda = \frac{1}{V_A} = 15 \mu\text{m} = 15 \times 10^{-3} = 0.015$




input from previous stage

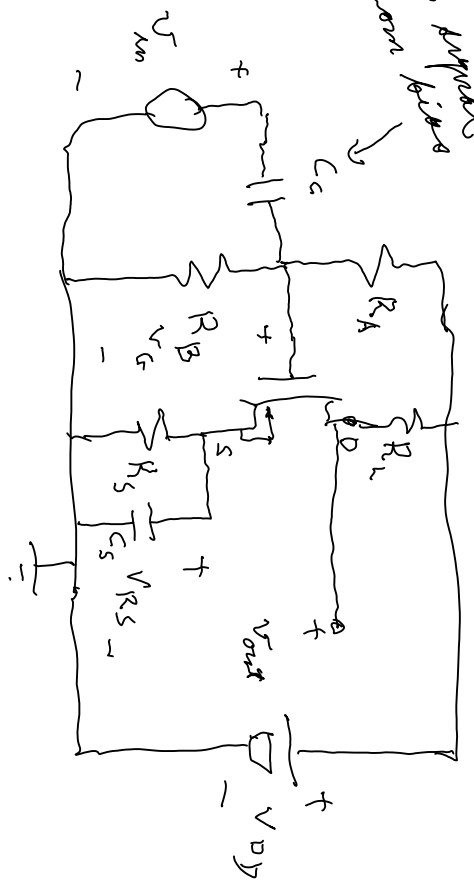

$$\frac{V_{out}}{V_{in}} = A_v \approx -g_m R_L$$

$$g_m \approx \frac{2I_D}{(V_{GS} - V_{th})}$$

$C_C$  &  $C_S$  = shorts for signal

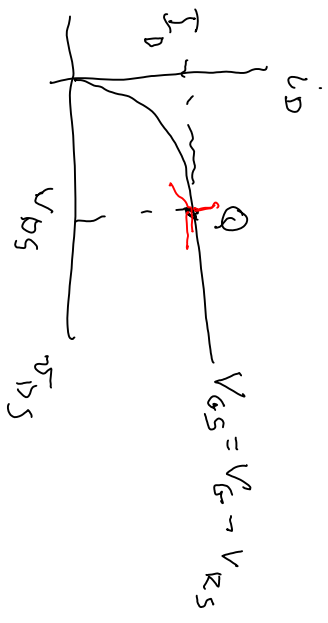

$$V_G = \frac{R_B}{R_A + R_B} \cdot V_{DD} = \frac{1}{\frac{R_A}{R_B} + 1} \cdot V_{DD}$$

assume  $R_S \rightarrow 0$  for signal due by use of  $C_S \approx R_S \parallel \frac{1}{C_S} \approx \frac{1}{\frac{1}{R_S} + C_S \omega} = \frac{1}{\frac{1}{R_S} + C_S \omega}$  at  $S$

at  $DS \rightarrow \omega = 0 \quad Y_{CS}(0) = \frac{1}{R_S}$

$$Y(j\omega) = G_S + jC\omega \Rightarrow |Y(j\omega)| = \sqrt{G_S^2 + (C\omega)^2} \Rightarrow \text{for signal the impedance seen by the source has } |Z(j\omega)| = \frac{1}{|Y(j\omega)|} = \frac{1}{\sqrt{G_S^2 + (C\omega)^2}}$$

at  $\omega \gg 0, |Z(j\omega)| \approx 0$

puts a short on source to ground  $\Rightarrow$  CS amplifier


use large  $C_S$

Source  $I_T = I_{DC}$

OTA

P.646  
Chap 9.33

Chap 9.26  
P.638

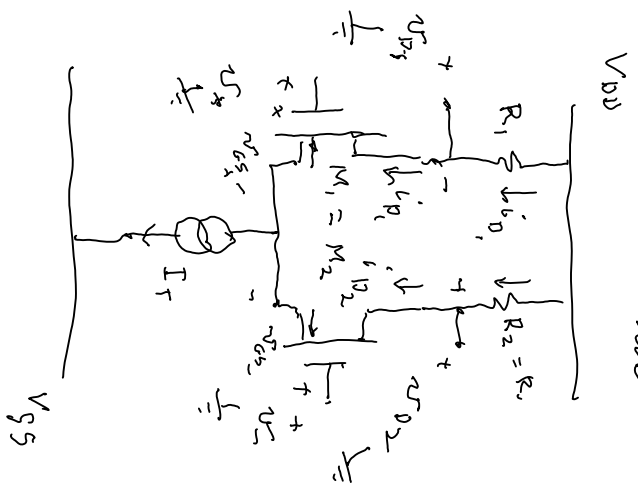


@ S: KVL  $\Rightarrow 0 = -V_T + V_{GS1} - V_{GS2} + V_{DS1} - V_{DS2}$

$V_T - V_{DS1} = V_{GS1} - V_{GS2} = V_{DS1} - V_{DS2}$


@ D: KVL  $\Rightarrow 0 = -V_{DS1} - R_1 i_{D1} + R_2 i_{D2} + V_{DS2}$

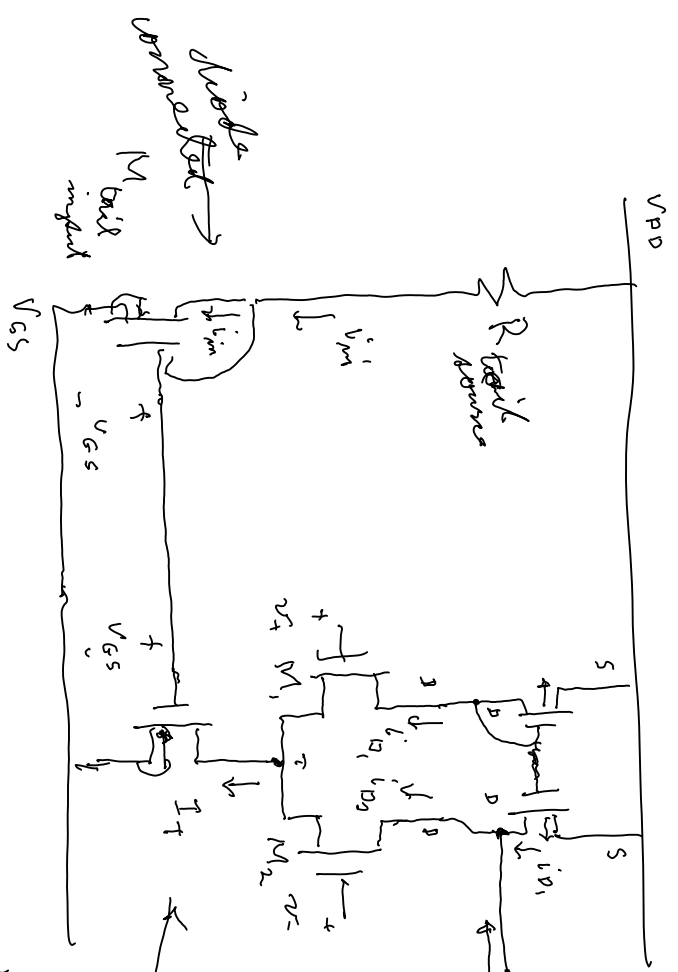$V_{DS1} - V_{DS2} = R_1 (i_{D1} - i_{D2}), R_2 = R_1$



differential  
input

differential  
output

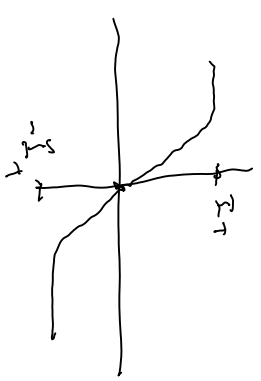

$$i_D = i_{D1} - i_{D2}$$

$$v_{in} = v_+ - v_-$$

KCL @ D

$$0 = i_D + i_{D1} - i_{D2}$$


$$i_D = i_{D2} - i_{D1}$$

KCL @ T

$$0 = I_T - i_{D1} - i_{D2}$$

$$I_T = i_{D1} + i_{D2}$$

$I_D$  for triode output

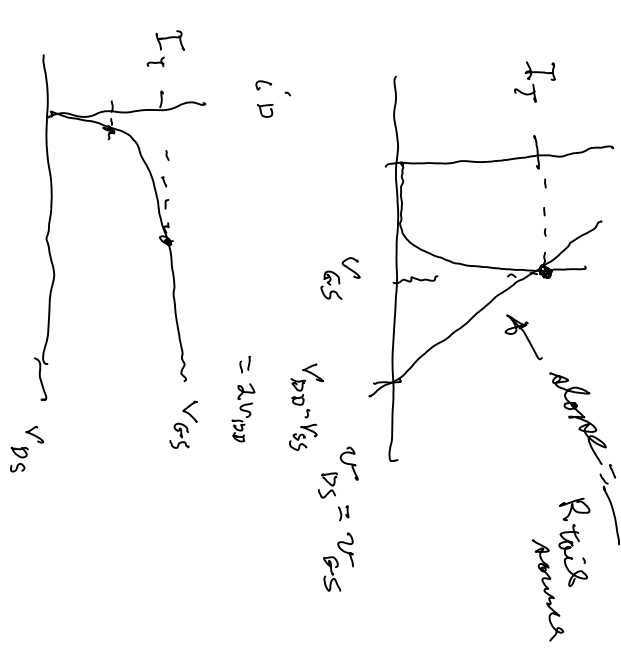

$$v_{DS} = v_{GS} = V_{DD} - V_{GS} = 2V_{DD}$$

Resistor  
Network



small signal  $i_o = g_m v_m$

$$i_1 = g_{m2} (-v_2)$$


$$i_L = R_{CL} v_2 \Rightarrow v_2 = + \frac{i_L}{R_{CL}}$$

$$i_1 = -g_{m2} \cdot \frac{i_L}{R_{CL}}, \quad i_2 = -i_1$$

$$= -g_{m2} (-i_2) \cdot R_{CL}$$

$$i_2 = g_m v_m$$
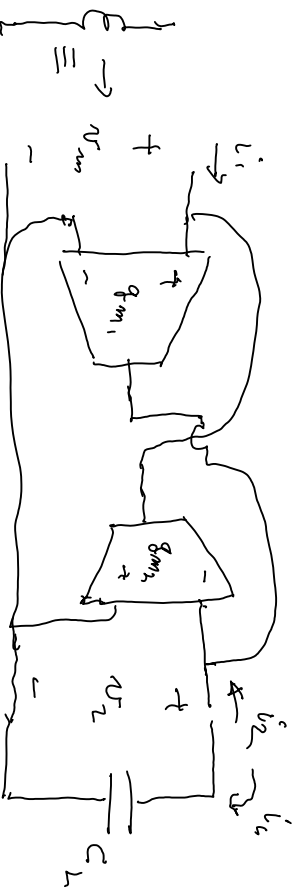
$$i_1 = + \frac{g_{m2}}{R_{CL}} \cdot g_m v_m$$



generator

$$i_1 = i_{in} = \frac{g_{m2} g_m}{R_{CL}} v_m = g_m (A) ; \quad g_m (A) = \frac{1}{g_m} = \frac{C_L}{g_{m1} g_{m2}} \cdot A \leftarrow \text{an inductor}, \quad L = \frac{C_L}{g_{m1} g_{m2}}$$