
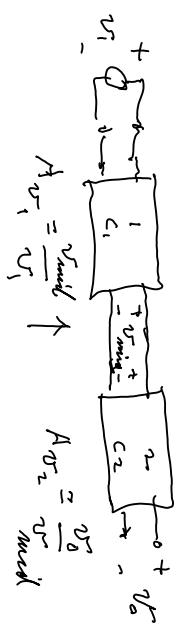
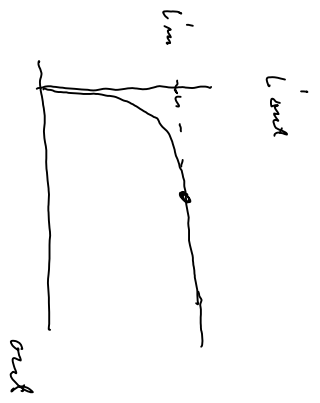


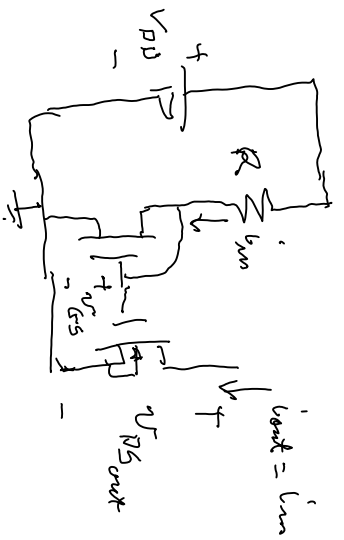Example connection, p. 85, Fig. 1.17
 Example connection, p. 547, Fig. 8.29




$$A_{v1} = \frac{v_{mid}}{v_1}$$


$$A_{v2} = \frac{v_0}{v_{mid}}$$

$$A_{v0} = \frac{v_0}{v_1} = \frac{v_0}{v_{mid}} \cdot \frac{v_{mid}}{v_1} = A_{v2} \cdot A_{v1}$$


when C_2 is connected

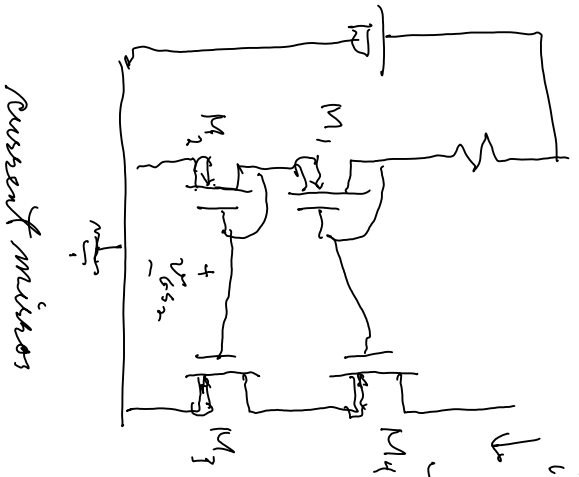

current mirrors

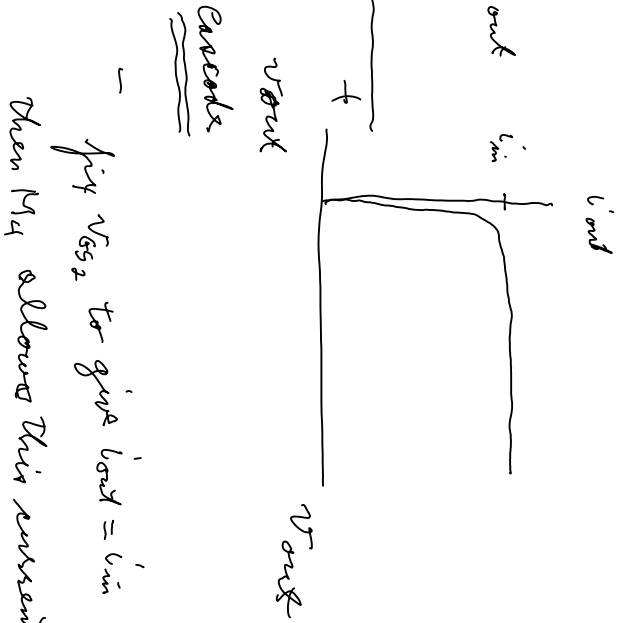

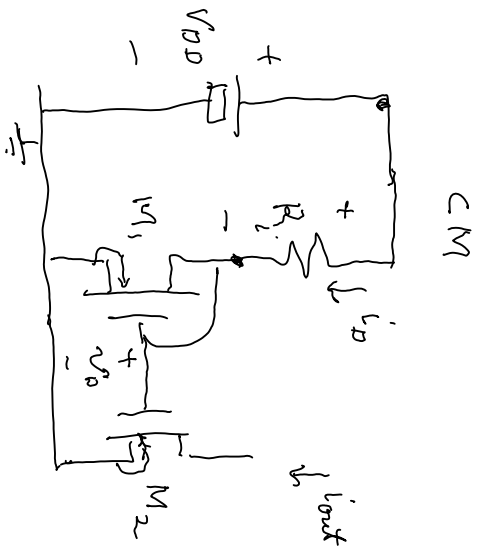
then M_2 allows this current for almost all output voltages



$$v_D = v_{DS} = v_{GS} > v_{GS} - V_{T0}$$

$$v_{DS} > v_{GS} - V_{T0}$$

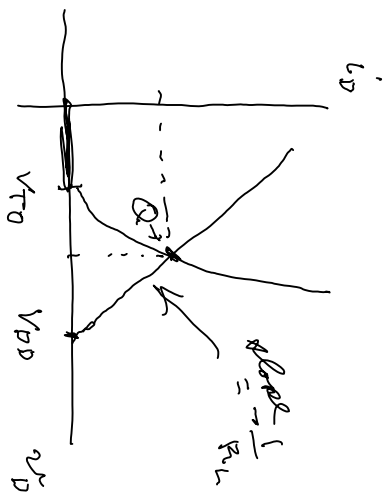M_1 is in saturation if V_{DD} is big enough to keep $v_{GS} > V_{T0}$



Load line

$$i_D = -\frac{1}{R_L} v_D + \frac{V_{DD}}{R_L}$$

$$i_D = k(v_{D0} - V_{T0})^2 (1 + \lambda v_D) \approx k(v_{D0} - V_{T0})^2, \quad k = \frac{k_p}{2} \cdot \frac{W}{L}$$

given $i_{out} \text{ ref} = i_D = i_{in}$

" V_{DD}
" M_1
find R_L

$$KVL \text{ @ } -V_{DD} + R_L i_D + v_D$$

$$R_L i_D \approx V_{DD} - v_D$$





device v_D gives $i_{in} = k (v_D - v_{T0})^2$ (x (1 + λv_D)) but λ small

$$v_D = v_{T0} \pm \sqrt{\frac{i_{in}}{k}}$$

but $v_D = v_{GS} > 0$ as $v_D - v_{T0} > 0$ (as M_1 turned on)
 for use + on $\sqrt{\dots}$

$$0 = -V_{DD} + R_L i_{in} + (v_{T0}) + \sqrt{\frac{i_{in}}{k}} \implies R_L = \frac{(V_{DD} - v_{T0} - \sqrt{\frac{i_{in}}{k}})}{i_{in}} \text{ for known } R_L$$

all don't like resistors

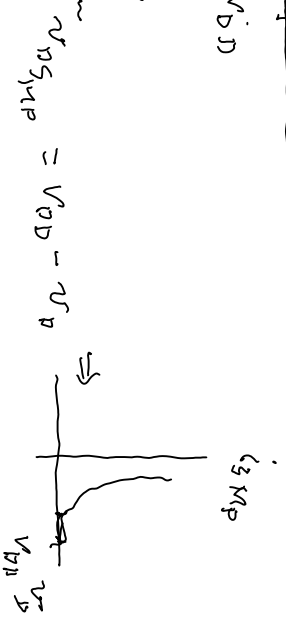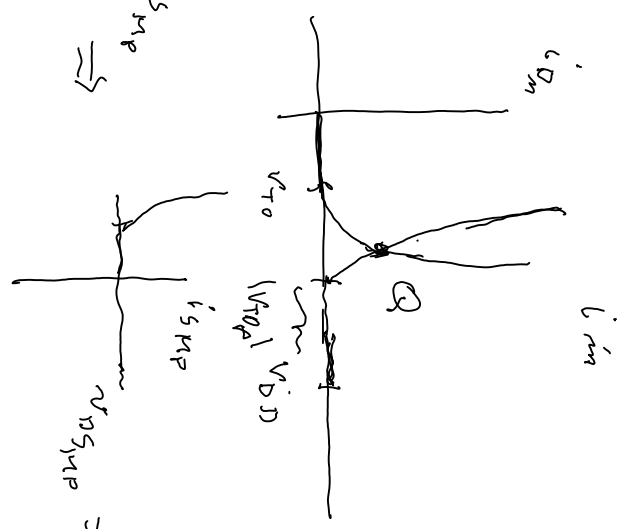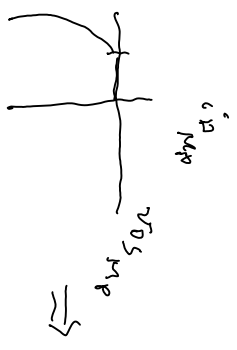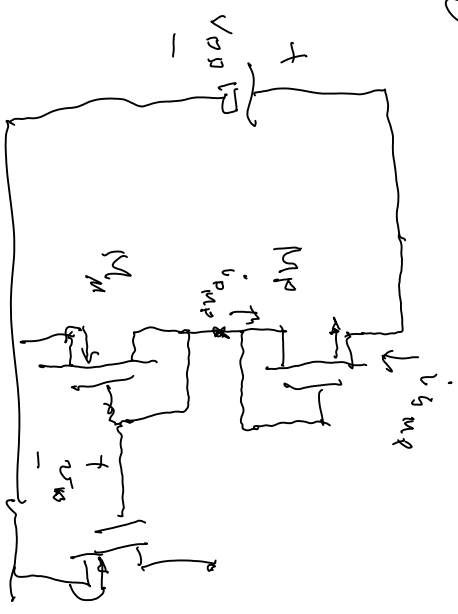

$$v_{DS,MP} = V_{DD} - v_D$$

$$I_{S_p} \approx I_{D_p} (V_{D_0} - V_D - |V_{T_{op1}}|)^2 = I_{D_n} \approx I_{D_n} (V_D - V_{T_{D_n}})^2$$


take $\sqrt{\quad} \Rightarrow \sqrt{\frac{I_{D_p}}{K_{p1}} (V_{D_0} - |V_{T_{op1}}| - V_D)} = \sqrt{V_D - V_{T_{D_n}}}$


if M_p & M_n are complementary

then $K_p = K_n$, $|V_{T_{op}}| = V_{T_{D_n}}$

for complementary $\rightarrow (V_{D_0} - V_D) = V_D \Rightarrow V_D = \frac{1}{2} V_{D_0}$

Testing OTA

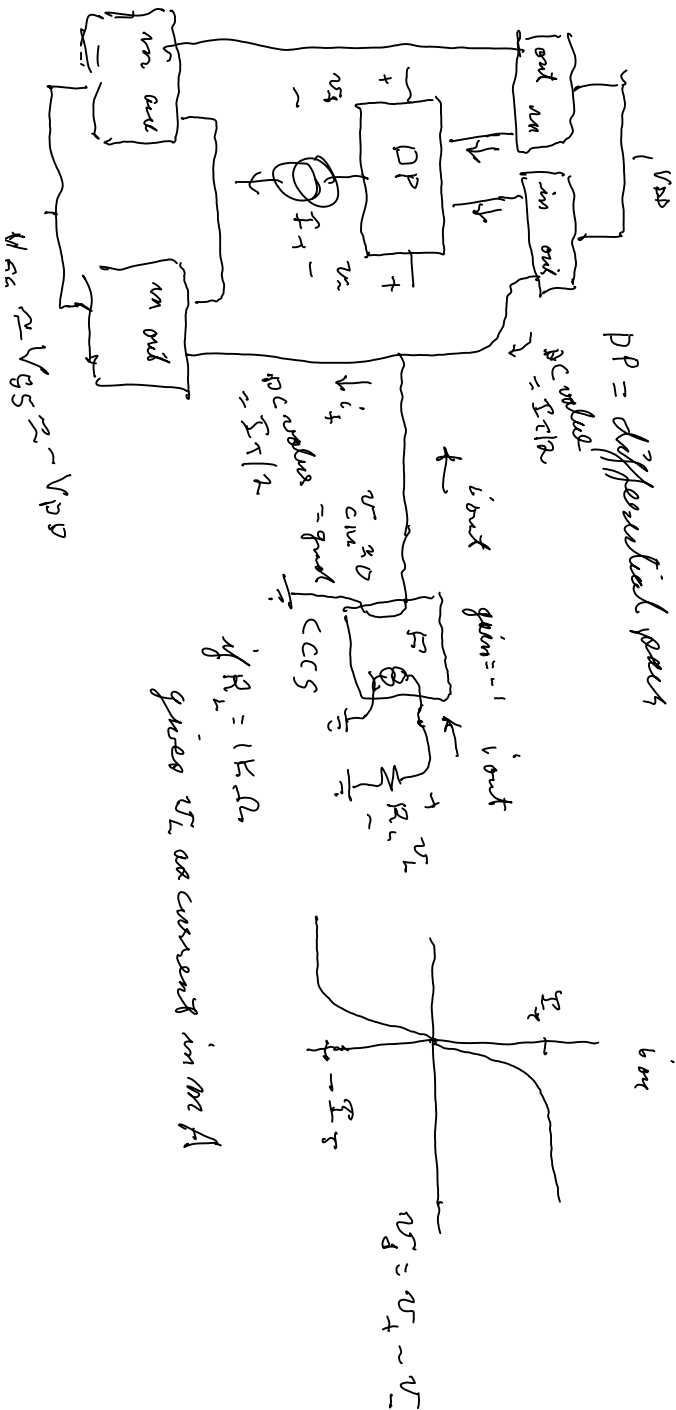


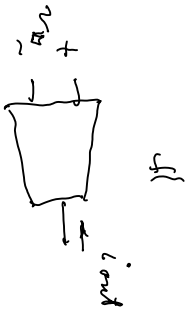

if V_{GS} is from BJT then $i_o = I_T \cdot \tanh\left(\frac{V_D}{2V_T}\right)$ $V_T = \frac{kT}{q}$

Exp for MOS OTA

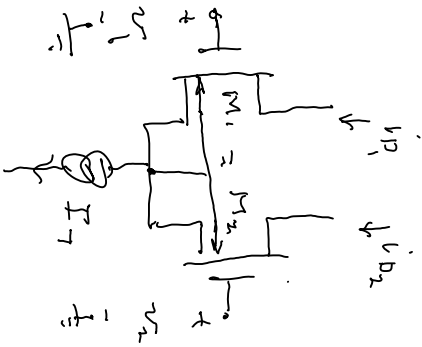P. 2.66, NIMOS
P. 6.17 for DP, i_{D1} , i_{D2} eq. (9.45)



KVL $v_{GS1} = 0 = -v_{D1} + v_{GS1} - v_{GS2} + v_{D2}$ $\Rightarrow v_{D1} - v_{D2} = v_{GS1} - v_{GS2} = v_D$ input

in saturation $i_{D1} = k(v_{GS1} - V_{T0})^2$, $i_{D2} = k(v_{GS2} - V_{T0})^2$

$$\sqrt{\frac{i_{D1}}{k}} = v_{GS1} - V_{T0}, \quad \sqrt{\frac{i_{D2}}{k}} = v_{GS2} - V_{T0} \Rightarrow v_D = v_{GS1} - v_{GS2} = (v_{GS1} - V_{T0}) - (v_{GS2} - V_{T0}) = \sqrt{\frac{i_{D1}}{k}} - \sqrt{\frac{i_{D2}}{k}}$$

$$v_d^2 \approx \frac{v_{D1}^2}{k} + \frac{v_{D2}^2}{k} - 2 \sqrt{\frac{v_{D1}^2 v_{D2}^2}{k^2}} \approx \frac{I_T}{k} - \frac{2}{k} \sqrt{v_{D1} (I_T - v_{D1})} \quad \text{reduces for } v_{D1}$$

$$\left(v_d^2 - \frac{I_T}{k} \right)^2 \approx \frac{4}{k^2} (v_{D1}^2 - I_T v_{D1}) \Rightarrow v_{D1}^2 - I_T v_{D1} + \frac{k^2}{4} \left(v_d^2 - \frac{I_T}{k} \right)^2 = 0$$

$$v_{D1} = \frac{I_T}{2} + \frac{1}{2} \sqrt{I_T^2 - 4 \frac{k^2}{4} \left(v_d^2 - \frac{I_T}{k} \right)^2}$$

reduces for v_{D1} (max-)
 v_{D2} (max-)