

$$i_{D1} = \frac{I_T}{2} + \frac{1}{2} \left\{ I_T^2 + 4 \frac{k}{4} \left( \frac{V_D^2}{R} - \frac{I_T}{k} \right)^2 \right\} = \frac{I_T}{2} + \frac{1}{2} \left\{ I_T^2 - (k^2 V_D^4 - 2k^2 I_T V_D^2 + I_T^2) \right\}$$

$$= \frac{I_T}{2} + \frac{\sqrt{I_T}}{2} \cdot \sqrt{I_T} \sqrt{R} V_D \sqrt{1 - \frac{k^2 V_D^2}{2 I_T k}}$$

for small max



$$I_T = \frac{I_T}{2} + \left\{ \frac{I_T k}{2} V_D \sqrt{1 - \left( \frac{V_D}{\sqrt{2 I_T / k}} \right)^2} \right\}^2$$

$$\approx \frac{I_T}{2} + \frac{I_T}{2} \left( \frac{V_D}{\sqrt{2 I_T / k}} \right)^2$$




$$\text{(@ } V_D \approx V_{Dmax}, I_T = \frac{I_T}{2} + \frac{I_T}{2} \left( \sqrt{1 - \frac{1}{2}} \right) = I_T$$

$$i_{D2} \sim i_{D1} \approx I_T \cdot R \left( \frac{V_D}{\sqrt{2 I_T / k}} \right) \cdot \left( 1 - \left( \frac{V_D}{\sqrt{2 I_T / k}} \right)^2 \right)$$

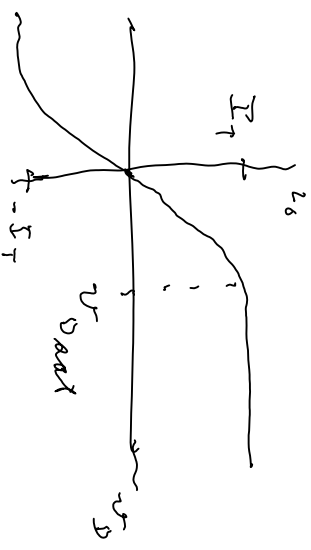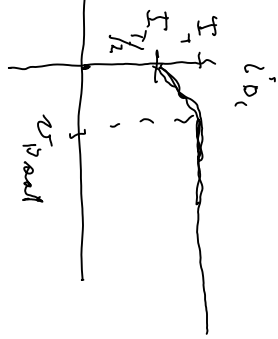achieve of  $\left( \frac{V_D}{\sqrt{2 I_T / k}} \right)^2 = \frac{1}{2} \Rightarrow V_{Dmax} = \sqrt{\frac{2 I_T}{k}}$



Buckle

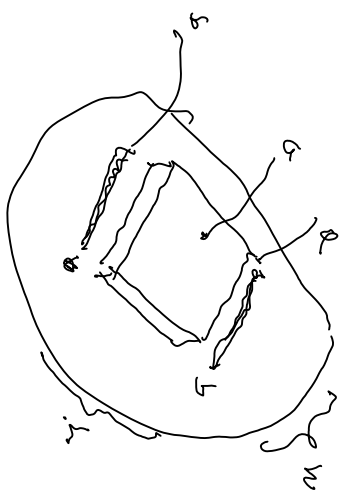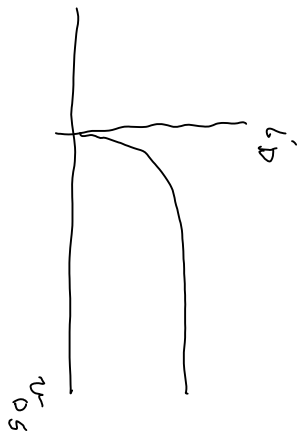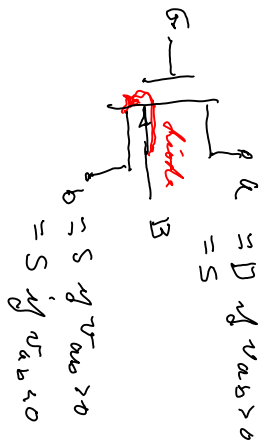

$$I_B = I_{B_{SAT}} \left( e^{V_{Bb}/V_T} - 1 \right)$$

if  $v_{Bb} \gg \frac{1}{2}$  then diode current, diode normally  $i_B = 0$

thus if  $v_B$  is smaller than any other voltages in the circuit or  $v_{Bb} = 0$

often see



here  $B = b$

as if  $v_a < v_b$  then trouble as Buck to lower terminal becomes forward biased  $\Rightarrow i_B$  extremely large

potentials


P. 288 Body effect

$$V_{th} = V_{T0} + \gamma \left[ \sqrt{(2\phi_s + V_{SB})} - \sqrt{2\phi_s} \right]$$

$$\gamma = \text{LAMBDA}, \phi = \text{PHI}$$

$$\gamma = \text{GAMMA}$$

# Use of OTA

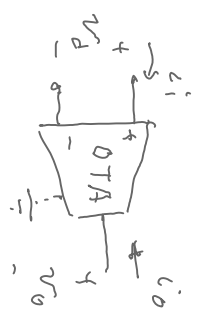


$$i_1 = 0$$

$$i_0 = g_m v_D$$



open load

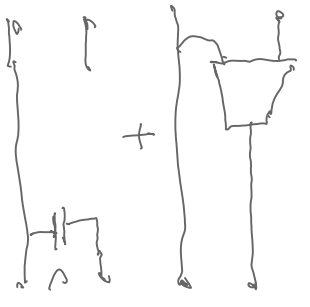

$$Y_1 = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$

$$Y_2 = \begin{bmatrix} 0 & 0 \\ 0 & aC \end{bmatrix}$$

$$Y \Rightarrow \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_D \\ v_0 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_0 \end{bmatrix}$$

$$i_1 = i_1 + i_2$$



$$i_1 + i_2 = i_2$$

$$v_1 = v_1 + v_2$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y_1 \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_2 \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = (Y_1 + Y_2) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y = \begin{bmatrix} 0 & 0 \\ g_m & aC \end{bmatrix} \text{ and } i_1 = 0, v_1 = \text{input}$$

$i_2 = 0$  for open circuit  
 $v_2 = v_0 = \text{output}$


$$0 = g_m v_1 + aC v_0 \Rightarrow v_0 = -\frac{g_m}{aC} v_1$$

$$\frac{1}{s} \Rightarrow \int_0^t + IC \Rightarrow \text{this circuit is an integrator}$$

When also


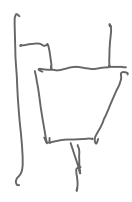
$$Y = \begin{bmatrix} 0 & -g_{m2} \\ g_{m1} & 0 \end{bmatrix}$$



$$Y_1 = \begin{bmatrix} 0 & 0 \\ g_{m1} & 0 \end{bmatrix}$$




$$Y_2 = \begin{bmatrix} 0 & -g_{m2} \\ 0 & 0 \end{bmatrix}$$

Power into this original

$$v_1^{(+)} \cdot i_1^{(+)} + v_2^{(+)} \cdot i_2^{(+)} = v_1^{(+)} (g_{m2}) v_2^{(+)} + v_2^{(+)} (g_{m1}) v_1^{(+)} = \begin{pmatrix} g_{m1} & -g_{m2} \\ -g_{m2} & 0 \end{pmatrix} v_1^{(+)} v_2^{(+)}$$

if  $g_{m1} = g_{m2}$  then  $P_i = 0$

### Darlington Transistor

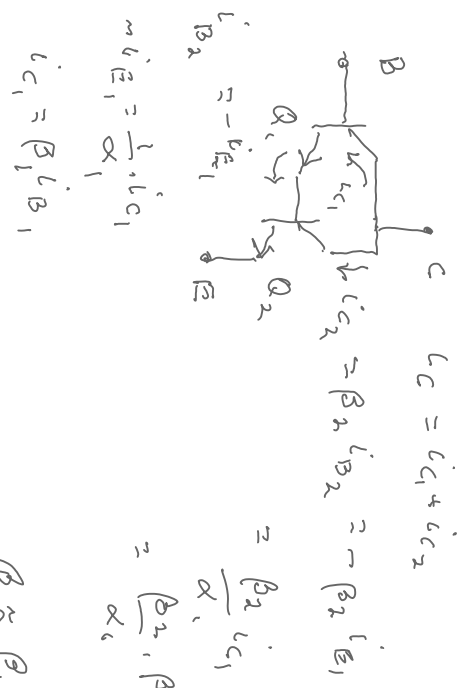

$$i_{C1} = \beta_1 i_{B1}$$

$$i_{E1} = \frac{1}{\alpha_1} i_{C1}$$

$$\beta \approx \beta_1 \beta_2 \approx \beta_2$$

$$= \frac{\beta_2}{\alpha_1} \beta_2 i_{B1}$$

$$\Rightarrow i_C = \beta_1 i_{B1} + \frac{\beta_2}{\alpha_1} \beta_1 i_{B1} = \left( \beta_1 + \frac{\beta_1 \beta_2}{\alpha_1} \right) i_{B1}$$

$$i_C = i_{C1} + i_{C2}$$

$$\approx -\beta_2 i_{E1}$$

$$= \frac{\beta_2}{\alpha_1} i_{C1}$$

$$i_C = \beta i_{B1}$$


$\beta = \text{BETA}$ ,  $\alpha = \text{ALPHA}$

$$i_C \approx -\alpha i_{E1}$$

$$\beta = \frac{\alpha}{1-\alpha}$$



Charakter

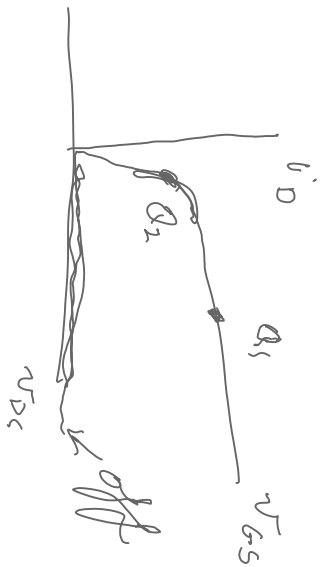

CMRR, p. 838, eq. (9.81)

Class A = small signal linear, p. 923

Class B =  $\frac{1}{2}$  time on,  $\frac{1}{2}$  time off, p. 929

Class AB = on but not linear, p. 935

Class D = p. 965

multitons class C = p. 923