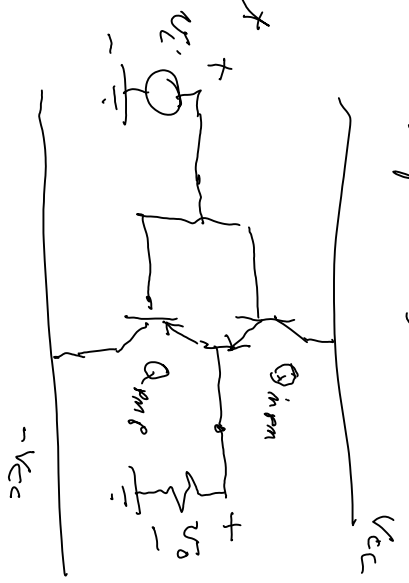


Power Prod, p. 929, Fig. 12.5


Millics effect, p. 725, Eq. (10.45)

Class B  
for power output  
stages








Body effect, p. 288, Eq. (5.30)

System a week from Th

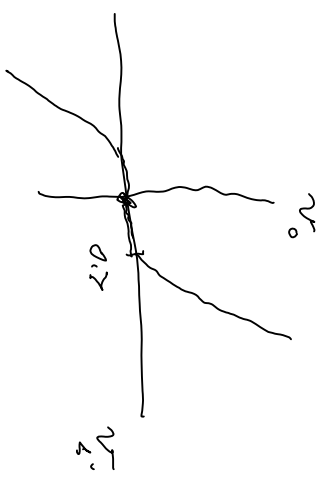

# Miller's effect

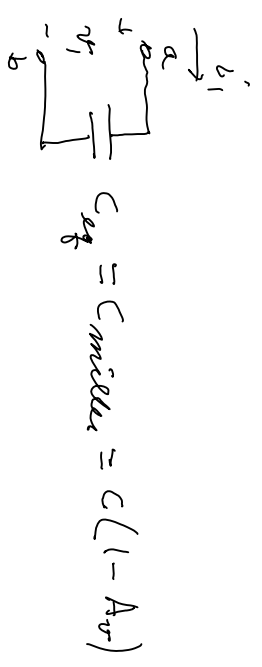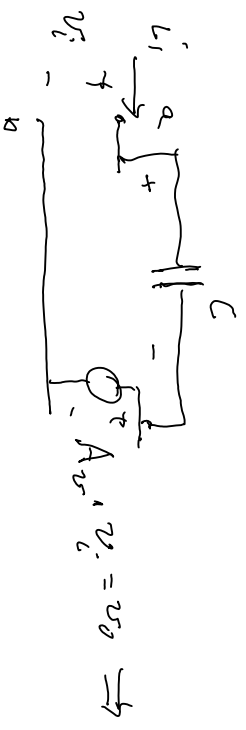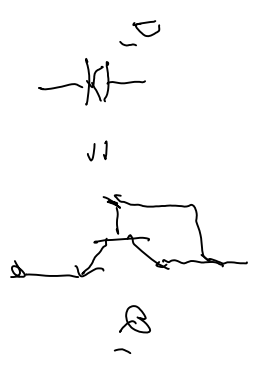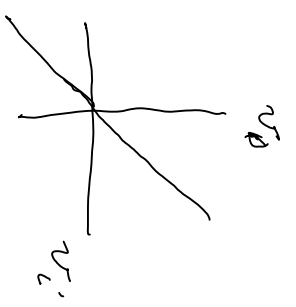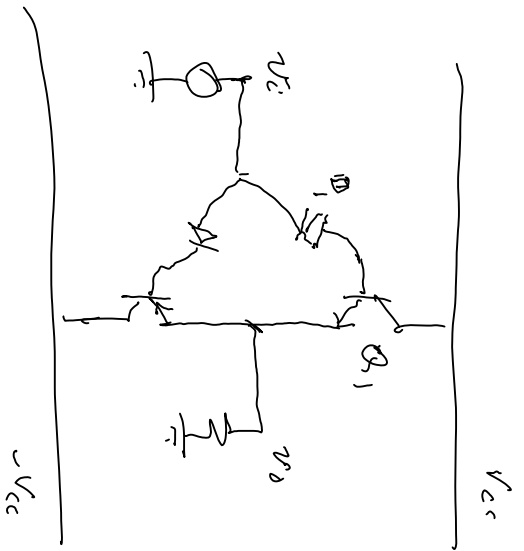


$$i'_1 = AC(v'_i - v_o)$$

$$= AC(v'_i - A_v v'_i) = AC(1 - A_v)v'_i = AC_M v'_i$$


normally  $A_v \approx -g_m R_L \Rightarrow C_{Miller} = C(1 + g_m R_L) \gg C$

Body effect:

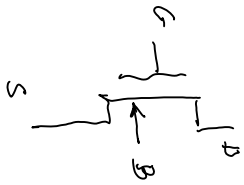

$$V_{th} = V_{T0} + \gamma \left( \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$

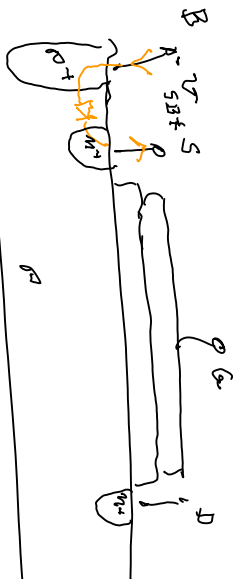
$V_{th}$  = threshold voltage increases if  $V_{SB} > 0$



if  $V_{SB} > 0$  diode S-B is turned off

but if  $V_{SB} < 0.6V$  then this diode is on

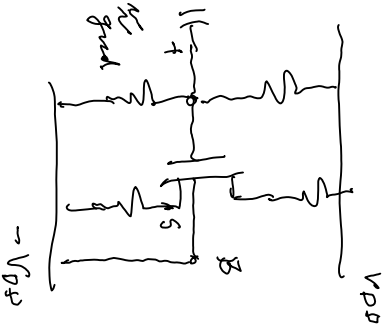$\therefore$  tie the bulk to lowest potential



given  $V_{SB} \approx V_{DD}$


if in saturation  
 $I_D = K (V_{GS} - V_{th})^2$

$$\frac{4.00}{-0.64} = \frac{3.36}{3.36}$$

Ex:  $V_{T0} \approx 1V$ ,  $\gamma = 1/2$ ,  $2\phi_f \approx 0.64V$ ,  $\sqrt{2\phi_f} = 0.8$ ,  $V_{DD} = 3.36$

then  $\gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}) = \frac{1}{2} (\sqrt{2} - \sqrt{0.64}) = \frac{1}{2} (1.414 - 0.8) = 0.307$

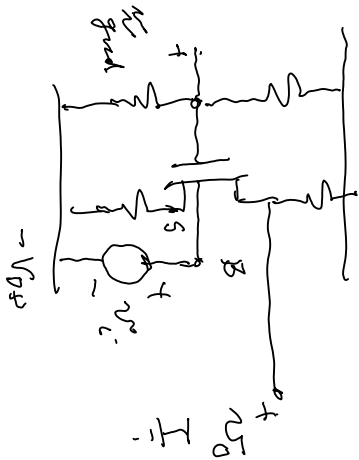$V_{T0}$  changes to  $V_{th}$ , from 1 to 1.6V  $\Leftarrow$  a big change. Here  $V_{SB} = V_{DD}$  as seen



$$g_{m1} \approx \frac{k_n}{2} \frac{I_{D1}}{(V_{GS} - V_{th})^2}$$

$$g_{m1} = \frac{\partial I_D}{\partial v_{GS}} = g_{m1b} \quad \therefore I_D = k_n (V_{GS} - V_{th}(V_{SB}))^2$$


$$\frac{\partial I_D}{\partial v_{GS}} = \frac{\partial I_D}{\partial v_{GS}} \cdot \frac{\partial v_{GS}}{\partial v_{GS}} = 2k_n (v_{GS} - v_{th}(v_{SB})) \cdot \frac{1}{2} \frac{1}{2k_n + v_{SB}} \quad (-1)$$

$$\frac{\partial v_{GS}}{\partial v_{GS}} = 1 \cdot \frac{1}{2k_n + v_{SB}}$$



$\therefore$  we can use this as another type of amplifier

$$\text{if } v_{SB} = -0.2 \text{ get } \frac{1}{2k_n + v_{SB}} > 1$$

Barkley's Bias

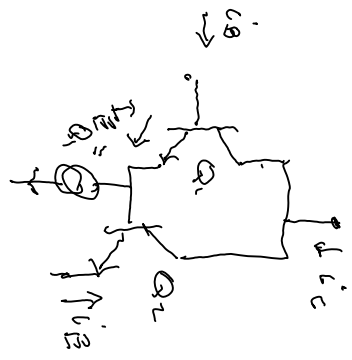


8 in  
LM139

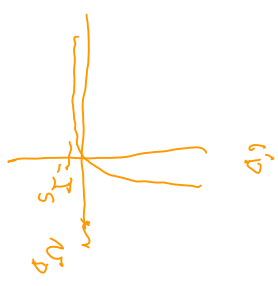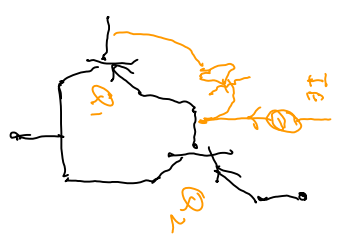


Amnesta, Chap. 14, P. 1091


CMOS

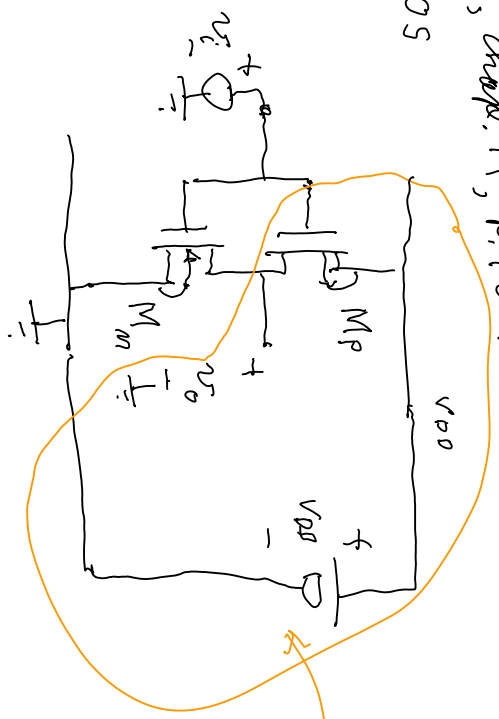


acts as a load on Mn

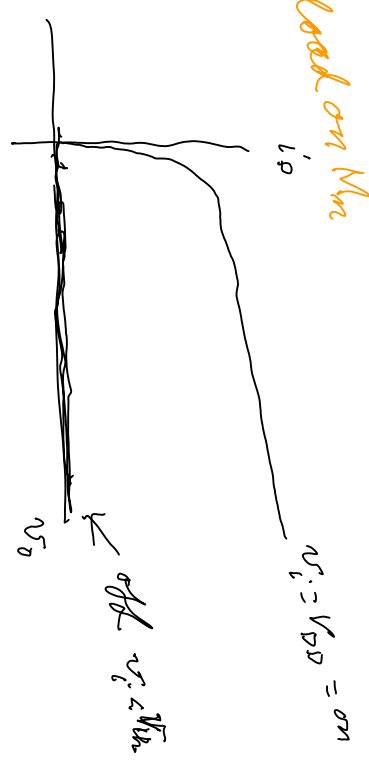

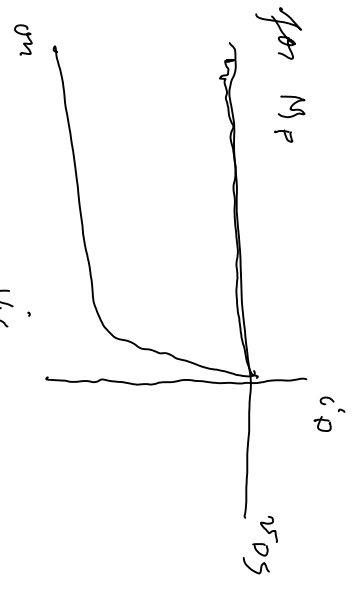allows base & emitter resistors for Q1 when the base is open circuit



combine

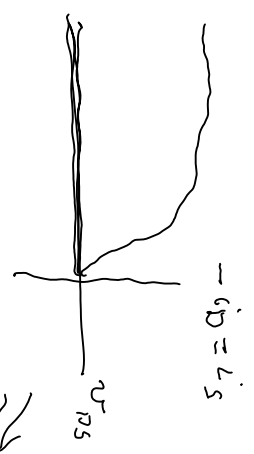

$$v_{SD} + v_{SD} - V_{DD} = 0$$

$$v_{SD} = -v_{SD} + V_{DD}$$

