
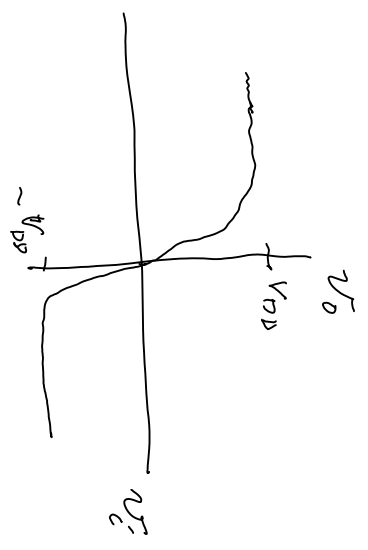


Inverter

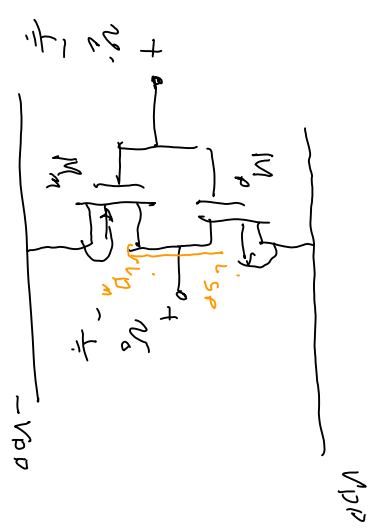

with no load
 $i_{SP} = i_{DP}$

$$i_{SP} = \frac{K_P}{2} \left(\frac{W}{L}\right)_P (v_{GS} - V_{T0})^2 (1 + \lambda_P v_{SD})$$

$$i_{DP} = \frac{K_N}{2} \left(\frac{W}{L}\right)_N (v_{GS} - V_{T0})^2 (1 + \lambda_N v_{DS})$$


note that M_p & M_n are in saturation @ bias ($v_o = v_i = 0$)

as $v_{GS} = V_{DD}$, $v_{DS} = V_{DD}$ $V_{DD} = v_{DS}$ $v_{GS} - V_{T0} = V_{DD} - V_{T0}$, $V_{T0} > 0$ if enhancement mode transistors
 $\therefore v_{DS} > v_{GS} - V_{T0}$ @ origin

gives a formula for $v_p = v_p \left(\frac{K_P W}{K_P L} \right) \left(\frac{W}{L} \right) \left(\frac{V_{DD} - V_{Tn}}{V_{DD} - V_{Tn}} \right)^2 \frac{(1 + \lambda V_{DD})}{(1 + \lambda V_{DD})}$

if $M_p \Rightarrow$ a fast complement of M_n uses $v_p = v_n$

Bias & small signal

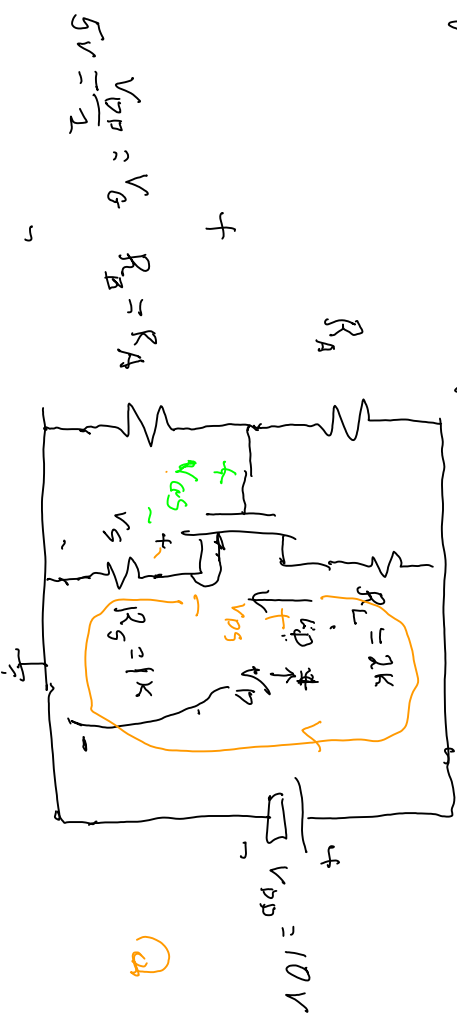

$V_{GS} = V_G$
 $R_D = R_A$
 $V_{DD} = 10V$
 $V_{GS} = 5 - I_D \Rightarrow I_D = 5(5 - I_D - 1)^2$
 $I_D = 10^{-3} A$
 $V_{T0} = 1V$

if in saturation
 $I_D = I_0 \times 10^{-3}$
 $R_S = V_G \times 10^3$, $R_L = V_L \times 10^3$

$V_{DS} = V_{DD} - I_D R_L - I_D R_S = V_{DD} - (R_S + R_L) I_D$
 $V_{GS} = V_{DD} - I_D R_S = 5 - 1 \cdot I_D$; $V_{DS} = 10 - (3) I_D$

$K_P W = 5 \times 10^{-3} A$
 $V_{T0} = 1V$

$$I_D = 5(4 - I_D)^2 \Rightarrow \frac{I_D}{5} = 16 - 8I_D + I_D^2 \Rightarrow I_D^2 - (8 + \frac{1}{5})I_D + 16 = 0$$

$$I_D = -\left(-\frac{41}{5}\right) \pm \frac{1}{2} \left(\sqrt{\left(\frac{41}{5}\right)^2 - 4(16)} \right) = \frac{41}{5} \left(1 \pm \sqrt{1 - \frac{4 \times 16 \times 25}{(41)^2}} \right) \approx \frac{41}{5} \left(1 \pm \left[1 - \frac{1}{2} \left(\frac{4 \times 16 \times 25}{41^2} \right) \right] \right)$$

$$\approx \pm \text{sign} \frac{41}{5} \left(2 - \frac{1}{2} \left(\frac{4 \times 16 \times 25}{41^2} \right) \right) \approx \frac{41}{5} \left(2 - \frac{1}{2} \right) = \frac{40 \times 3}{2} = 4 \times 3 = 12$$

$$- \text{sign} = \frac{41}{5} \left(\frac{1}{2} \cdot \left(\frac{4 \times 16 \times 25}{41^2} \right) \right) = \frac{41}{5} \cdot \frac{1}{4} = 2$$

assumption

$$V_{GS} = 10 - (3) \cdot I_D \quad \rightarrow \quad V_{GS} - V_{T0} = 5 - I_D - 1 \approx 4 - I_D \Rightarrow 10 - 3I_D > 4 - I_D$$

$$6 > 4I_D \Rightarrow I_D < \frac{3}{2} = 1.5$$

\therefore must use the - sign $\Rightarrow I_D \approx 2$

$$\therefore V_{GS} = 5 - I_D = 3V; \quad V_{DS} = 4V \quad \& \quad V_{DS} > V_{GS} - V_{T0}$$

$$Q = I_D = 2 \text{ mA}, \quad V_{DS} = 4V, \quad V_{GS} = 3V$$

$$\frac{\frac{8}{10} \times \frac{4 \times 16 \times 25}{41 \times 40 \times 40}}{10} = \frac{8 \times 5}{2 \times 40} = \frac{30}{40} = \frac{3}{4} = \frac{1}{2}$$