

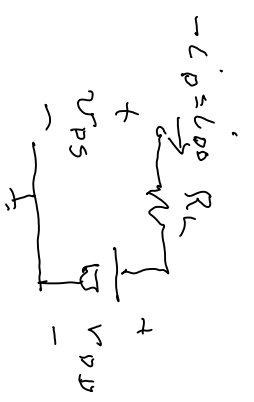
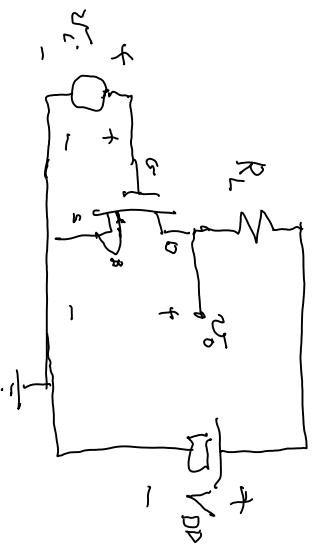


# R<sub>1</sub> I<sub>DD</sub> inverters

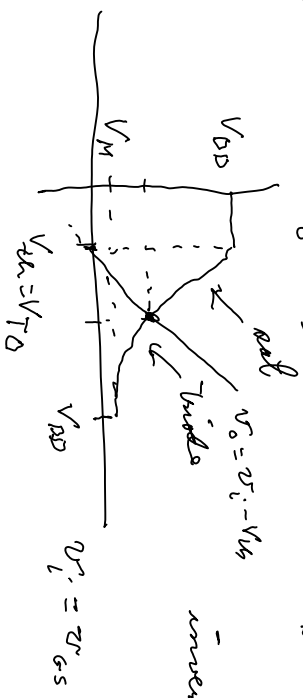

$$v_o = V_{DD} - R_L I_D$$

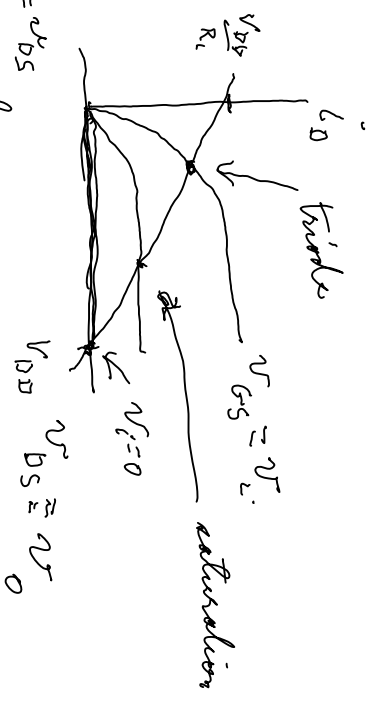

in saturation  $v_{GS} = v_{GS} > v_{GS} - V_{th} = v_i - V_{th}$  , in triode  $v_{GS} = v_o < v_i - V_{th}$

inverters curve

Common point  $v_o = v_i = v_{th}$

$$R = \frac{K_P}{2} \cdot \frac{W}{L}; \quad K_P = \mu C_{ox}$$

$$C_{ox} = \frac{\epsilon \text{ gate dielectric}}{\text{gate dielectric thickness}}$$

Assume  $v_o = R_i (v_i - V_{T0})^2 = R_i (2(v_i - V_{T0})v_o - v_o^2)$  as  $v_o = v_i - V_{T0}$  gives


$$v_o = V_{DD} - R_L (K_P [v_o + V_{T0}]^2) \text{ gives } v_o \text{ given } R_L, K_P, V_{T0}, V_{DD}$$

When input =  $V_{DD}$  (a binary 1) then  $v_o \neq 0$  (a binary 0)  
 $v_o = V_M = V_{minimum}$


$$V_M \approx v_o = V_{DD} - R_L K_P (2(V_{DD} - V_{T0})v_o - v_o^2) \Rightarrow \text{can find a quadratic in } v_o$$

$$\left( \frac{v_o - V_{DD}}{K_P R_L} \right) = v_o^2 - 2(V_{DD} - V_{T0})v_o \Rightarrow v_o^2 - 2(V_{DD} - V_{T0} - \frac{1}{K_P R_L})v_o + \frac{V_{DD}}{K_P R_L} = 0$$

to make a capacitor from a CMOS inverter

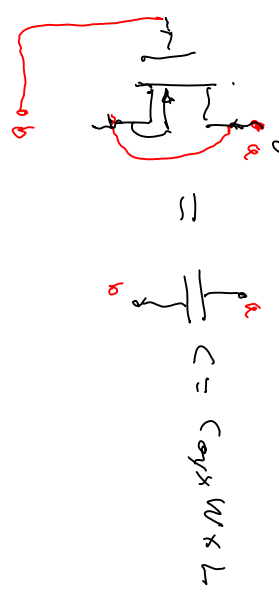
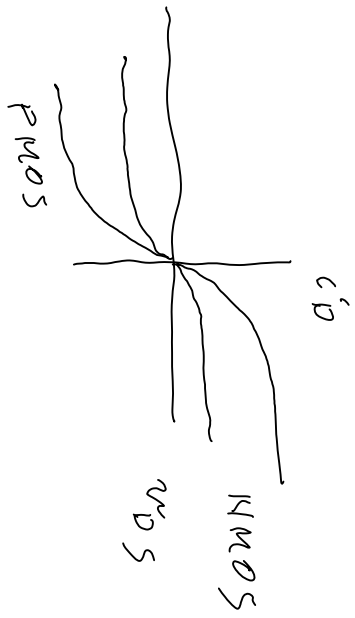
$$= \frac{1}{C} \quad C = C_{ox} W \times L$$



$$V_{SDP} = V_{SGP} > V_{SGP} - |V_{T0P}|$$



↓  
M<sub>P</sub> is in saturation

Here we take for a given  $v_i$  with  $i'_D = i'_S = -i'_{DP}$


$$\text{for } M_n \text{ in saturation} \quad k_n (v_i - V_{T0n})^2 = k_p (V_{DD} - v_o - |V_{T0p}|)^2$$

$$v_o = V_{DD} - |V_{T0p}| + \sqrt{\frac{k_n}{k_p}} \cdot V_{T0n} - \sqrt{\frac{k_n}{k_p}} \cdot v_i$$

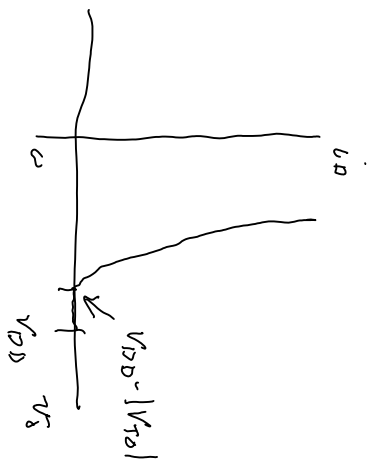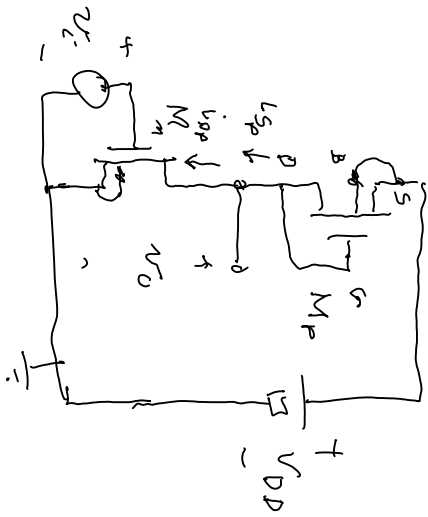if  $M_p$  is completely complementary then  $v_o = -v_i$



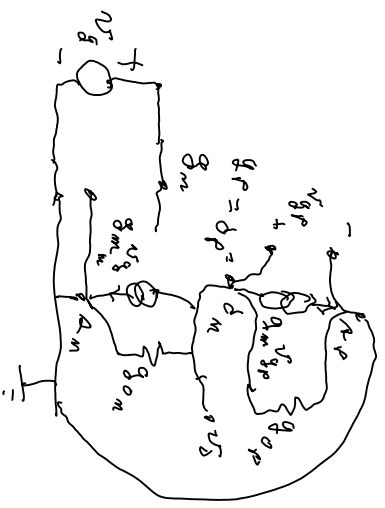If  $V_i = V_G + v_g$ ,  $V_G = \text{bias on gate}$  &  $v_g$  small signal,  $\{v_g\} \ll V_G$   
 to get small signal gain use equivalent circuits




$$G_L = g_{dm} + g_{dp} + g_{mp}$$

$$\frac{v_o}{v_i} = -g_{m_n} \frac{v_i}{G_L} = -g_{m_n} R_L$$

OTA  $Y = \begin{bmatrix} 0 & 0 \\ g_{m_n} & 0 \end{bmatrix}$


Leaky integrator

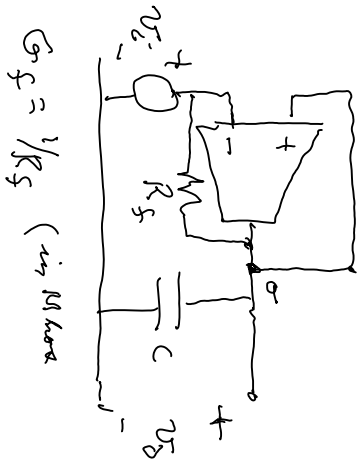

KCL:  $0 = g_m(v_o - v_i) + G_S(v_o - v_i) + R_C(v_o)$

@  $\omega$
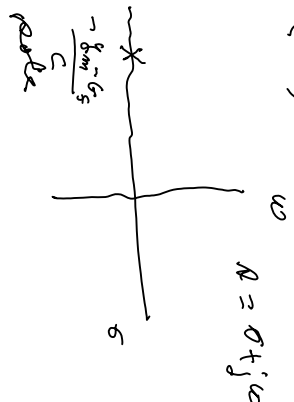
$$\frac{v_o}{v_i} = \frac{g_m + G_S}{R_C + (g_m + G_S)} = \frac{(g_m + G_S)/C}{R + (g_m + G_S)/C}$$



$$C \frac{dv_o}{dt} + (g_m + G_S)v_o = (g_m + G_S)v_i$$

$$i = \frac{dq}{dt}, \quad q = Cv$$

$$= \frac{dC}{dt} v + C \frac{dv}{dt}$$

$i(t) = \text{constant} \Rightarrow i = C \frac{dv}{dt} = R \cdot v$

$R = d/dt$

$dv = R \int dv = Y(s)$

$$= \int_{-\infty}^{\infty} v(t) e^{-st} dt$$