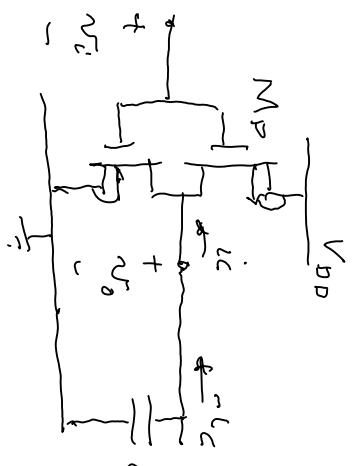




P. 1269 = OTA or error

P. 1151, string 14.39 \Rightarrow charging current, P. 1150 power in

pp. 1130-1135 C load on inverters


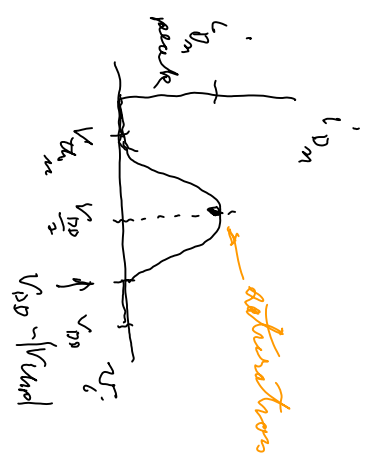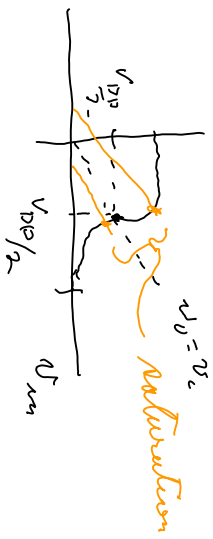
$$C \Rightarrow i_c = C \frac{dV_c}{dt} = \frac{dQ}{dt}, \quad Q = C \psi$$



$$i_{peak} = R \left(\frac{V_{DD}}{2} - V_{th} \right)^2 \left(1 + \lambda \frac{V_{DD}}{2} \right)$$

$$Power\ from\ V_{DD} = P_{average} = V_{DD} i_{avg}(t) = V_{DD} i_{Dp}(t)$$

$$Energy = \int_0^{t_r} P_{average} dt = \int_0^{t_r} V_{DD} \cdot i_{Dp}(t) dt = V_{DD} \cdot q(t_r)$$

If we start with C not charged, $V_D = 0$
 & we pull V_i to charge C \Rightarrow turn on M_p & off $M_n \Rightarrow$ as $q(t) = C v(t)$
 $\Rightarrow q(t_r) = C \cdot V_{DD}$

$$Energy\ from\ bias\ source = C V_{DD}^2$$


$$Energy\ into\ a\ capacitor \Rightarrow E_{HS} = \int_0^{t_r} v(t) i(t) dt \Rightarrow \int_0^{t_r} v(t) \cdot C \frac{dv(t)}{dt} dt = \int_{v(0)}^{v(t_r)} C v dv$$

$$= \frac{1}{2} \left(C v^2(t) \Big|_0^{t_r} \right) = \frac{1}{2} C V_{DD}^2$$

Energy into the inverter to charge C is

$$C V_{DD}^2 - \frac{1}{2} C V_{DD}^2 = \frac{1}{2} C V_{DD}^2$$

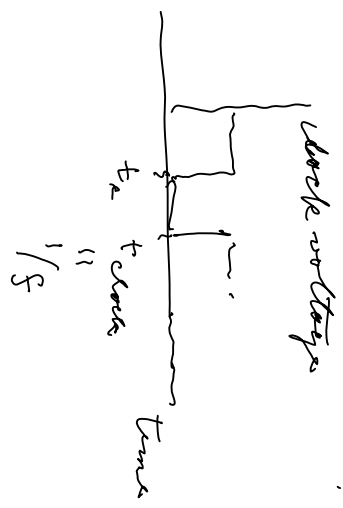On a clock of frequency f then we do this every half cycle



$$\lim_{dt \rightarrow 0} \frac{\Delta \text{Energy}}{\Delta t_{\text{rise}}} = \frac{\text{Energy}}{dt} \approx \frac{(\frac{1}{2} C V_{DD}^2) \times 2}{1/f}$$

= power into the inverter


$$= f C V_{DD}^2$$

\uparrow clock rate
 \uparrow C load capacity
 \uparrow V_{DD} bias supply

C is from other transistors & something like $W \times L \times \epsilon_{\text{ox}} / t_{\text{ox}}$

discharge of a C into an NMOS

determines component speed & structure

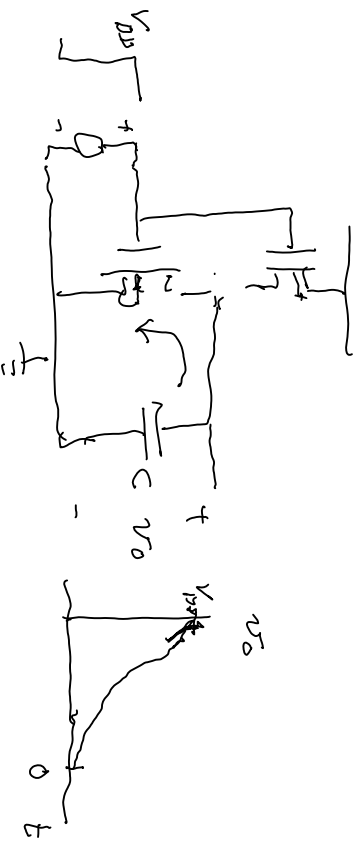

② $t = 0$ NMOS $v_{GS} = V_{DD}$
 $v_{DS} = V_{DD}$



M_n is in saturation & stays there until v_{DS} drops to $v_{DS} = v_{GS} - v_{th}$ (or $v_{DD} - v_{th}$)


① $t = 0 +$ initial $v_{DS} = V_{DD} - V_{th}$
 $i_{Dn} = I_{Dn} = k_n (V_{DD} - V_{th})^2 \Rightarrow I_{Dn} = -i_c = -C \frac{dv_{DS}}{dt} = I_{Bn}$

$k_n = k_n' \frac{W}{L}$

$= k_n' C_{ox} \frac{W}{L}$

$v_{DS}(t) = \int_0^t -\frac{1}{C} I_{Dn} dt = -\frac{1}{C} I_{Dn} t + (V_{DD})$ for $0 < t \leq T_{tr}$

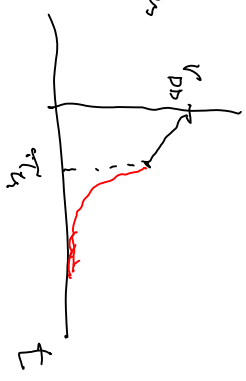② $t = T_{tr}$ transition from saturation to triode state for M_n
 then for $t > T_{tr}$, $i_{Dn} = k_n (2(v_{GS} - v_{th})v_{DS} - v_{DS}^2)$



for fixed v_0 , $T_3 \leq t < \infty$

$$Re(2(V_{D0}-V_{A0})^2 v_0 - v_0^3) = i c \Rightarrow a Riccati equation$$

$$-\frac{K}{c} dt = \frac{dv_0}{2(V_{D0}-V_{A0})^2 v_0 - v_0^3} \Rightarrow \int_{T_3}^t -\frac{K}{c} dt = \int_{v_0(t)}^{v_0} \frac{1}{2(V_{D0}-V_{A0})^2 v_0 - v_0^3} \cdot dv_0$$

$$\underbrace{-1}_{-1} \quad Re t = 2(V_{D0}-V_{A0})^2 \quad \left(\frac{1}{2(V_{D0}-V_{A0})^2 v_0 - v_0^3} \right) v_0$$

$$= \frac{-1}{v_0(2v_0 - a)} = \frac{K_1}{v_0} + \frac{K_2}{2v_0 - a} \quad \left. \begin{aligned} K_1 &= \frac{-2v_0}{v_0(2v_0 - a)} = -\frac{1}{v_0 - a} \\ K_2 &= \frac{1}{v_0 - a} \end{aligned} \right\} \quad \left. \begin{aligned} K_1 &= \frac{-1}{-a} = 1/a \\ K_2 &= \frac{1}{v_0 - a} \end{aligned} \right\} \quad \left. \begin{aligned} Re t v_0 &= 0 \end{aligned} \right\}$$

$$\text{for } K_2: \quad K_2 = \frac{-(2v_0 - a)}{v_0(2v_0 - a)} - \frac{K(2v_0 - a)}{v_0} \quad \left. \begin{aligned} Re t v_0 &= a \\ v_0 &= v \end{aligned} \right\} = \frac{-1}{v_0} \quad \left. \begin{aligned} v_0 &= v \end{aligned} \right\} = \frac{-1}{a}$$

$$-\frac{K}{c} \int_{T_0}^t dx = -\frac{K}{c} t + \frac{K}{c} T_0 = \int_{v_0(T_0)}^{v_0(t)} \frac{-1}{v_0(v_0 - a)} dv_0 = \int_{v_0(T_0)}^{v_0(t)} \left(\frac{1/a}{v_0} + \frac{-1/a}{v_0 - a} \right) dv_0$$

$$= \frac{1}{a} \left\{ \ln(v_0(t)) - \ln(v_0(T_0)) - \ln(v_0(t) - a) + \ln(v_0(T_0) - a) \right\} - \int_{v_0(T_0)}^{v_0(t)} \frac{1/a}{(v_0 - a)} dv_0$$

gives

$$\frac{1}{a} \ln \left[\frac{F(v_0(t))}{F(v_0(T_0))} \right] = -\frac{K}{c} t + \frac{K}{c} T_0$$

$$\Rightarrow F(v_0) = C \left(-\frac{K}{c} t + \frac{K}{c} T_0 \right) \quad T_0 < t < \infty$$

$$- \frac{1}{a} \ln \left[\frac{(v_0 - a)}{(v_0(T_0) - a)} \right] - \ln(v_0(t) - a)$$

where $F(v_0) = \frac{v_0(t) / v_0(T_0)}{(v_0(t) - a) / (v_0(T_0) - a)} \Rightarrow$ can solve for $v_0(t)$ now, $T_0 \leq t < \infty$

