

303 Spring 2019 – Homework 1 Due 02/07/19 **see 02/05 corrections**

Note: The 1N4007 diode Spice model the diode library in the path

Cadence/SPB_17.2/tools/capture/library/pspice ad is on the course web page and copied here as:

```
.MODEL D1n4007 d
+IS=7.02767e-09 RS=0.0341512 N=1.80803 EG=1.05743
+XTI=5 BV=1000 IBV=5e-08 CJO=1e-11
+VJ=0.7 M=0.5 FC=0.5 TT=1e-07
+KF=0 AF=1
```

1. (50 points, diode DC curves)

- In Spice do a DC run to get the DC diode curve of diode current, i_D , versus diode voltage, v_D , for the 1N4007 diode, submitting your curve. Run the curve over the diode voltage $-0.8V$ to $+0.8V$. The model should be in the PSpice diode library under D1n4007 but if not found use a Breakout diode with the above model.
- Repeat the curves for the pnp transistor 2N3906 formed into a diode by connecting the collector to the base. This transistor is found in the PSpice bipolar library under **Q2N3906 Q2N3904**.
- Repeat part b) but with the diode formed by connecting the emitter to the base.
- Comment on differences and why they come about.

, V_T

2. (50 points, Diode DC curves).

For the analytic DC diode equation $I=IS(e^{(V/V_T)} - 1)$

- Use any mathematical program (MathCad, MatLab, Mathematica) and plot this equation for IS which is that of the 1N4007 at room temperature, $V_T=36mV$, over the range $-1 < V < 0.8$ Volts.
- Compare any difference between the above Spice run using the above model for the 1N4007 and discuss any differences.
- Analytically find the derivative dI/dV and plot under the same conditions. The curve is of the small signal diode conductance, g .
- Analytically solve for V vs I and repeat parts a) and c) for V vs I and dV/dI over the range of current I obtained in part a). The derivative curve, dV/dI , is the small signal diode resistance, r . Compare the small signal resistance with $1/g$.
- Draw a tangent to the I vs V curve which intersects the V axis at $0.6V$ and ones at $0.65V$ and $0.7V$ and compare their slopes.