

303 Spring 2019 – Homework 3 due Th 02/21/19

The transistors are ones used in teaching labs here; some useful data is on the course web page. For the MC4007=CA3600 CMOS models use KP, W, L, Vto and Lambda. Curves are on the web page and KP is k in the text book.

```
.model nch nmos(Level=1 Tox=300n Uo=600 Kp=20.54u W=144u L=8u Vto= 1.3
+          Lambda=15m Cbd=4p Cbs=4p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
.model pch pmos(Level=1 Tox=300n Uo=300 Kp=10.32u W=328u L=8u Vto=-1.5
+          Lambda=15m Cbd=8p Cbs=8p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
```

1. (35 points, Q point values)
 - a. For the NMOS transistor assume a Q point in the saturation region at $V_{DS}=V_{GS}=7V$. Find the bias current I_D .
 - b. Repeat for the Q point in the triode region at $V_{DS}=2V$ and $V_{GS}=5V$.
 - c. Repeat for the PMOS transistor with a Q point at $V_{DS}=V_{GS}=-7$ and compare with the result of part a.

2. (35 points, CMOS Y matrix)
 - a. For the NMOS of Problem 1 above biased at the two stated Q points give the low frequency small signal admittance matrices (one for each Q point)
 - b. Repeat for the PMOS in saturation.
 - c. Draw the small signal equivalent circuits for each transistor when in saturation and compare. Be sure to label g, d, and s nodes.

3. (30 points, CS amplifier)

Assume a common source NMOS 4007 transistor is biased at the Q point of Problem 1 above with a 9V power supply ($=V_{DD}$).

 - a) Find the load line resistor resistance R_L and sketch the load line on a copy of the NMOS transistor curve.
 - b) Give the ideal voltage gain $A_v = -g_m R_L$ and compare with the voltage gain in the presence of the transistor output resistance r_o .
 - c) Give gate bias resistors in the MegOhm range to achieve the Q point and A_v .

3. (50 points, CMOS biasing)

Separately bias the two amplifiers of problem 2 and check in Spice your circuits' time domain responses to an input 2KHz sinusoid of 5mV amplitude.

Older holdover:

From possible homework 1:

2. (50 points, Diode biasing and ac & transient analysis).


For the following voltage multiplier circuit assume that the diodes are 1N4007s working at room temperature.

a) For this circuit calculate by hand the bias point (= Q point) current and voltage of the diode.

b) Determine (also by hand) the small signal gain of the circuit $v_o(s)/v_i(s)$, first with symbols (r_d , R_1 , L , R_L) and then with numerical values.

c) Set up the circuit in Spice and: b1) check the simulated Q point, then b2) do a magnitude frequency response (=AC run) from 1Hz to 1MEG Hz.

 d) Comment upon your simulation results versus your hand calculation.



```
.model nch nmos(Level=1 Tox=300n Uo=600 Kp=20.54u W=144u L=8u Vto= 1.3
+          Lambda=15m Cbd=4p Cbs=4p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
.model pch pmos(Level=1 Tox=300n Uo=300 Kp=10.32u W=328u L=8u Vto=-1.5
+          Lambda=15m Cbd=8p Cbs=8p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
```