

Solutions to Homework 5

Spring 2019

TA: Yidi Shen

MOSFET Model:

```
.model nch nmos(Level=1 Tox=300n Uo=600 Kp=20.54u W=144u L=8u Vto= 1.3  
+ Lambda=15m Cbd=4p Cbs=4p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
```

```
.model pch pmos(Level=1 Tox=300n Uo=300 Kp=10.32u W=328u L=8u Vto=-1.5  
+ Lambda=15m Cbd=8p Cbs=8p Cgdo=1.7n Cgso=1.7n Rs=1 Rd=1)
```

Design

1a)

$$V_{DD} = 6V, \quad C_1 = C_2 = 10\mu F, \quad R_S = 1k\Omega$$

Use 4007 NMOS

$$k_n' = 20.54\mu, \quad V_{t0} = 1.3V$$

$$W = 144\mu(m), \quad L = 8\mu(m), \quad \lambda = 15m(V^{-1})$$

DC Bias Calculation

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_{t0})^2 (1 + \lambda V_{DS})$$

$$\begin{cases} I_D = 0.5\text{ mA} \\ V_{DS} = 3V \end{cases} \Rightarrow V_{GS} = 2.90881V$$


$$V_D = I_D R_S + V_{DS} = 0.5\text{ mA} \times 1k\Omega + 3V = 3.5V$$

$$R_L = \frac{V_{DD} - V_D}{I_D} = \frac{6V - 3.5V}{0.5\text{ mA}} = 5k\Omega$$

$$g_m = \frac{2I_D}{V_{GS} - V_{t0}} = \frac{2 \times 0.5\text{ mA}}{(2.9 - 1.3)V} = 0.6216\text{ mS}$$

$$g_o = \lambda I_D = 15 \times 10^{-3} \times 0.5 \times 10^{-3} = 7.5 \times 10^{-6}\text{ S}$$
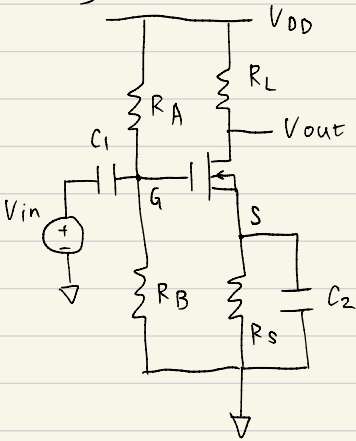
$$A_v = -g_m (R_L // r_o) = \frac{-g_m}{\frac{1}{R_L} + g_o} = -2.996$$



$$V_G = V_{GS} + I_D R_S = 2.909 \text{ V} + 0.5 \text{ mA} \times 1 \text{ k}\Omega$$

$$= 3.409 \text{ V}$$

$$\frac{R_A}{R_B} = \frac{V_{DD} - V_G}{V_G} = 0.76$$

$$R_A = 100 \text{ M}\Omega, \quad R_B = 131.58 \text{ M}\Omega$$


1C) $\frac{R_A}{R_B} = 0.76$, set $R_A = 10 \Omega$

$$\rightarrow R_B = 13.16 \Omega$$

for 2nd-stage

With the existence of 2nd stage amplifier, the small-signal equivalent circuit of 1st stage CS amplifier becomes:

 [We treat bypass capacitor short at the frequency of the small signal here]




$$A_{v1} = \frac{V_{out}}{V_{in}} = -g_m (R_L \parallel R_{L1} \parallel R_{A2} \parallel R_{B2})$$

when R_{A2} & R_{B2} big enough, they could be neglected in the A_{v1} expression, otherwise, A_{v1} will be much lower.


current sourcing mirror

2a)

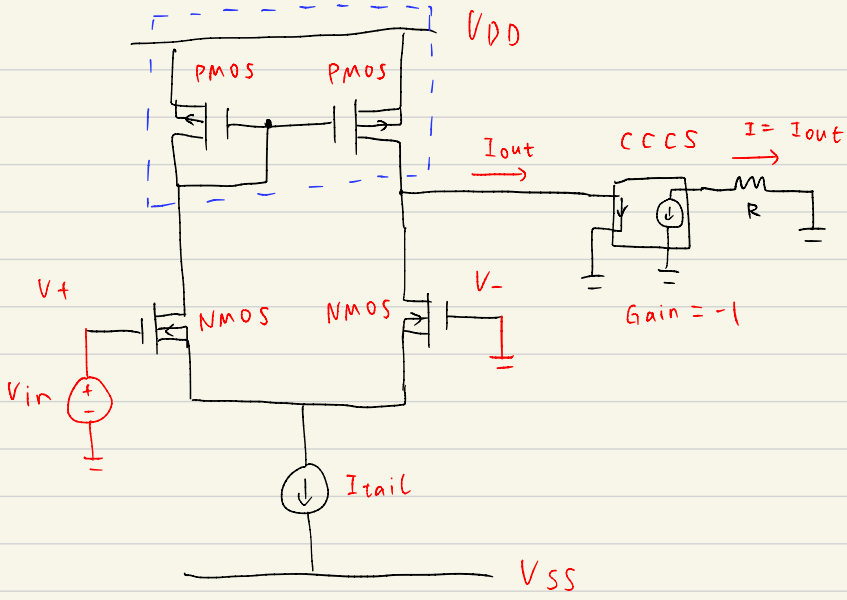


Check in Pspice:

1a)

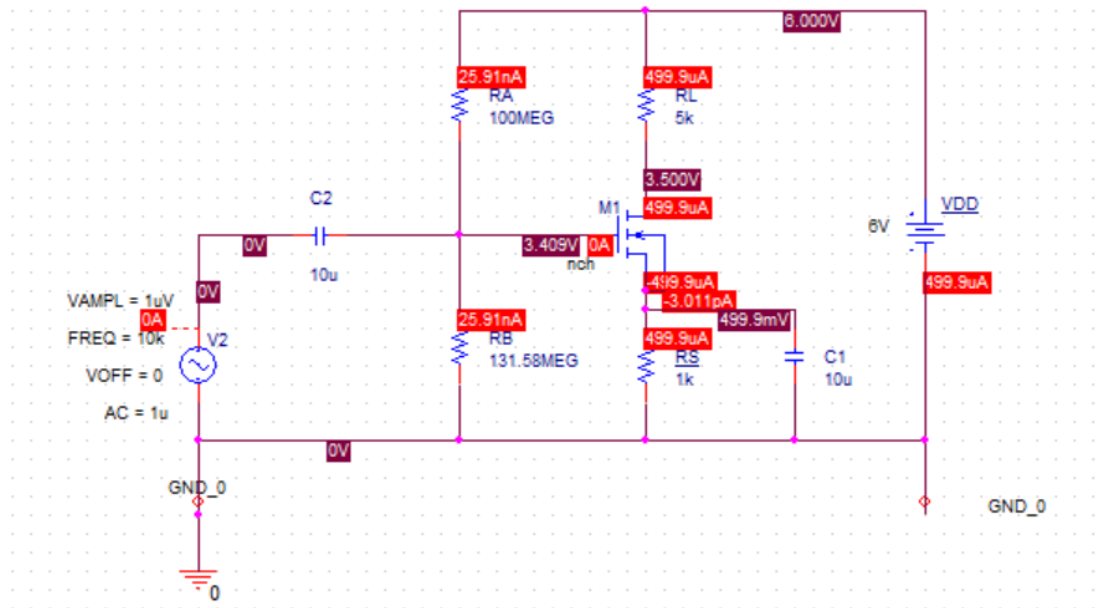


$i_D = 500\mu A = 0.5\text{mA}$, and $V_{DS} = V_D - V_S = 3.5\text{V} - 0.4999\text{V} = 3\text{V}$

 Use the method of frequency sweep to check the (mid frequency band) gain.



This plot shows the magnitude of V_{out}/V_{in} changes with frequency, so we can read from the curve that the magnitude of mid frequency band voltage gain is about 2.9981.


Trace Name	Y1
X Values	1.2711K
V(RL:1)/ V(C2:2)	2.9978

 


Phase response shows that the phase of voltage gain is about -180. So the voltage gain of the circuit is -2.9881.

1b)

Cascade two of the above circuits:

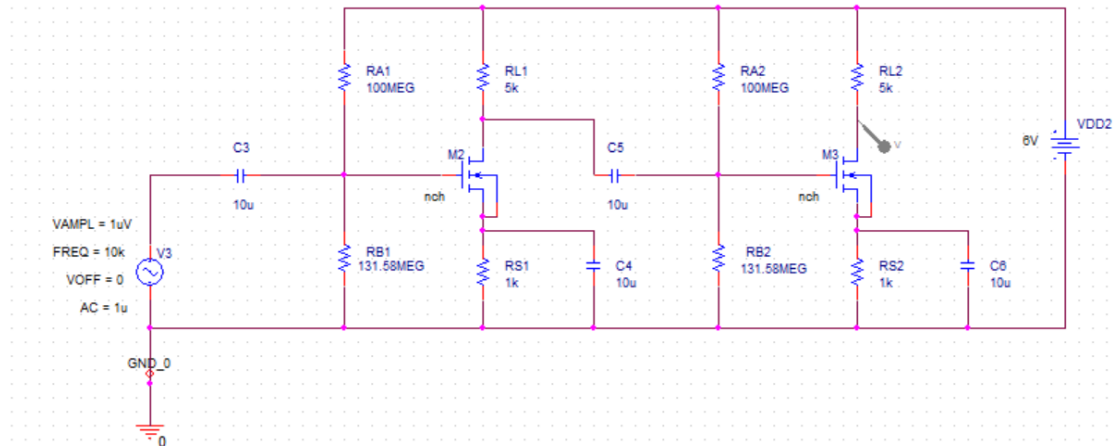


 Magnitude of V_{out}/V_{in} frequency sweep:



Read from the plot that the magnitude of mid frequency band voltage gain is about 8.9879.


Trace Color	Trace Name	Y1
	X Values	5.2148K
CURSOR 1,2	V(RL2:1)/ V(C2:2)	8.9879

 


Phase response shows that the phase of voltage gain is about 0. So the voltage gain of the circuit is 8.9879, which is close to the square of one-stage voltage gain.

1c)

Change the second stage bias resistor:

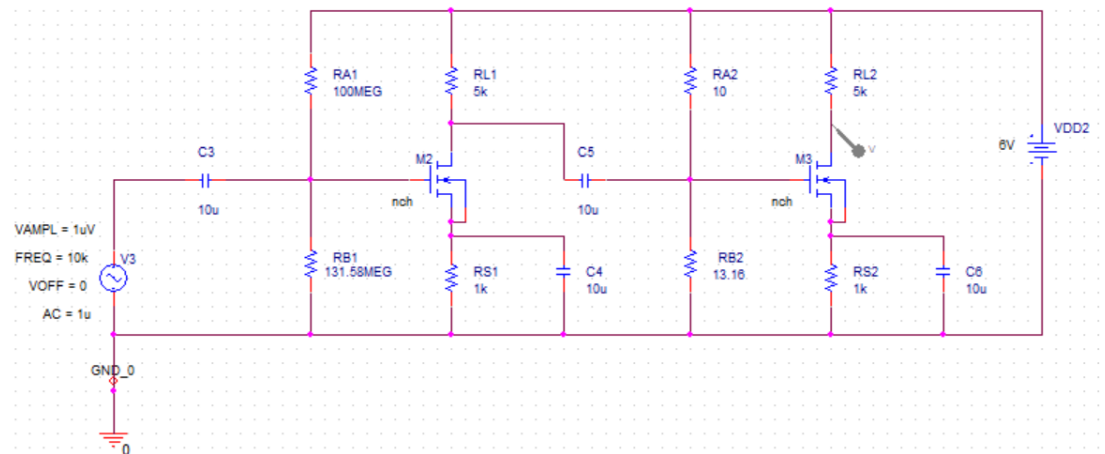

Frequency sweep:

 

Mid frequency band voltage gain is around $5.70e-3$, which is much lower than the result of 1b.

2b)

