 



Homework 6 Solution

ENEE 303
Spring 2019
TA: Yidi Shen


Parameter of Vpulse and Ipulse in Pspice




1. Ring Oscillator

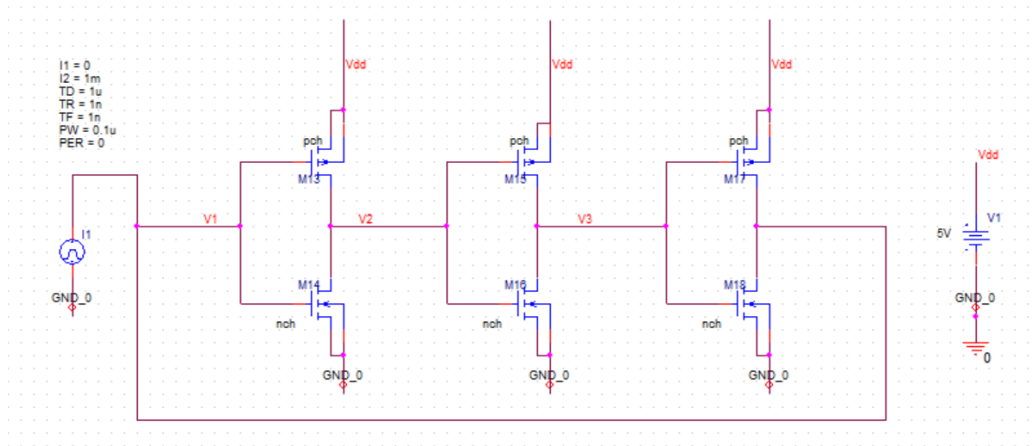

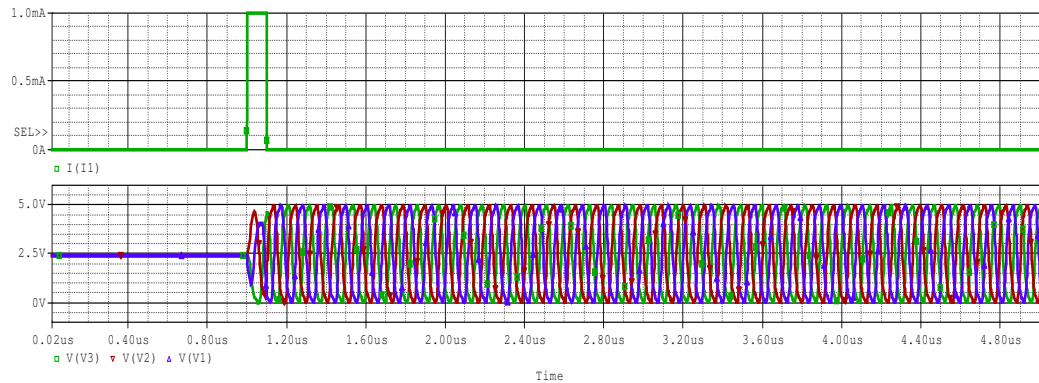Inject a short current pulse to node V1 at t=1us.



 The oscillation starts when the Ipulse come. Here is the waveform after Ipulse has vanished.



First measure the delay of an inverter

Y1	Y2	Y1 - Y2
3.0384u	3.0198u	18.531n
4.5772	2.1801	2.3971
24.867m	438.158m	-413.291m
2.8045	4.9539	-2.1493

Read the time difference between 1 of V1 and next 0 of V2, so the response time:

$$T_S = 18.5ns$$

Then measure the period of the oscillator

Y1	Y2	Y1 - Y2
2.9113u	3.0198u	-108.540n
2.2204	2.1801	40.287m
427.579m	438.158m	-10.580m
4.9540	4.9539	130.075u

Read the time difference between two 1 in V1, so the period:


$$T = 108.5ns$$

So


$$T \cong 5T_S$$

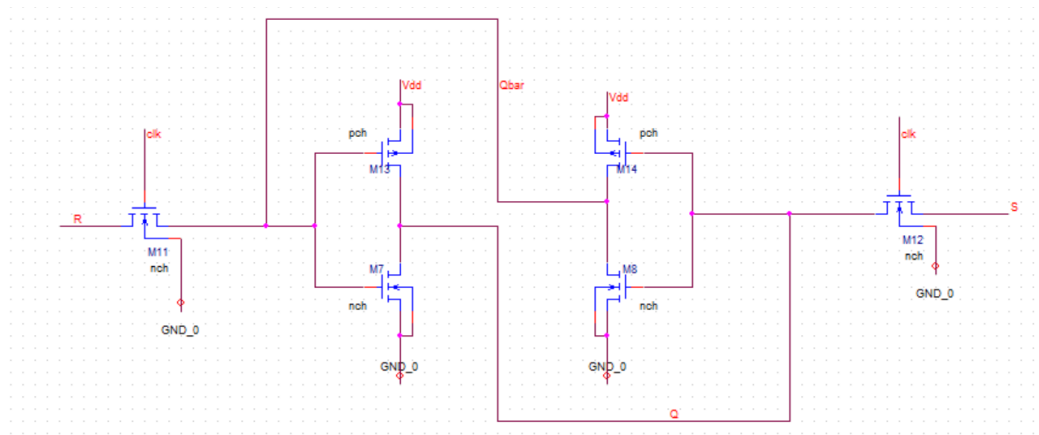2. SR Flip-Flop

I changed the definition of Q and Qbar to stay the same as textbook:



Input data, Clock and power supply:

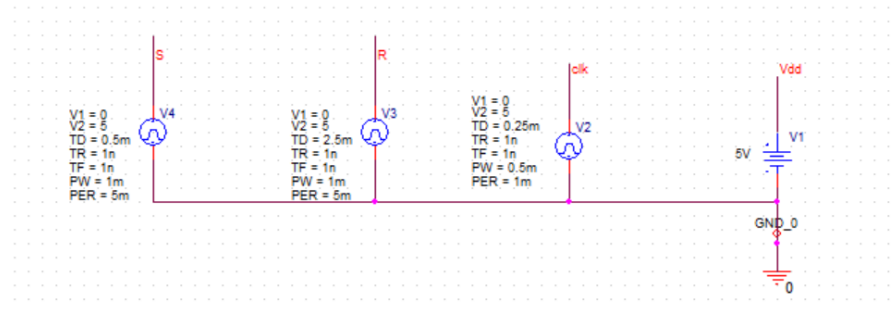


Run the simulation and plot all the input and output:


Figure 1 Clock

Figure 2 Set (Green) and Reset (Red)

Figure 3 Q

Figure 4 Qbar

 

 

Read the cases on the rising edge of the clock signal

time	S	R	Q	Qbar	State
t0	0	0	N/A*	N/A	Latch
t1	1	0	1	0	Set
t2	0	0	1	0	Latch (=t1)
t3	0	1	0	1	Reset
t4	0	0	0	1	Latch(=t3)


*Initial state is not given so the flip-flop has no value to latch at t0.

The voltage decrease in the latching stage, this comes from the non-ideal characteristic of the NMOS switch.


Reference: Pass Transistor Logic

https://en.wikipedia.org/wiki/Pass_transistor_logic

3. D Flip-flop

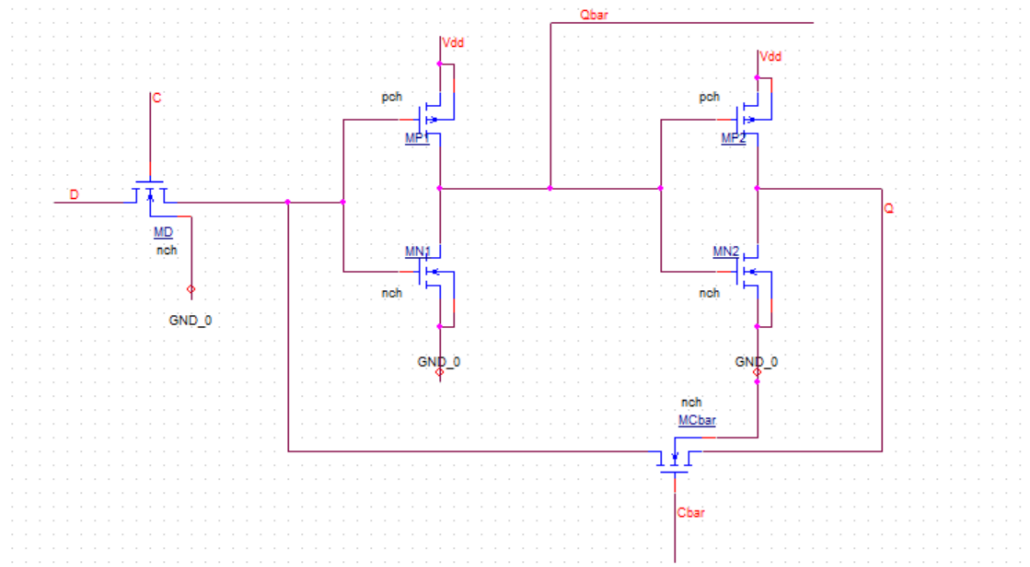

Input data, Clock and power supply:

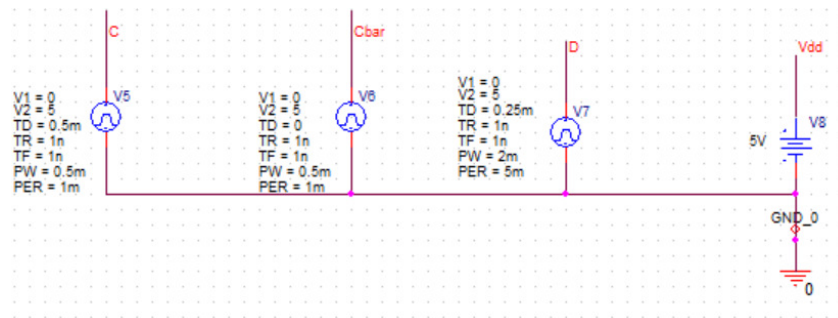

Run the simulation and plot all the input and output:


Figure 1 Clock

Figure 2 Clockbar

Figure 3 D

Figure 4 Q

Figure 5 Qbar

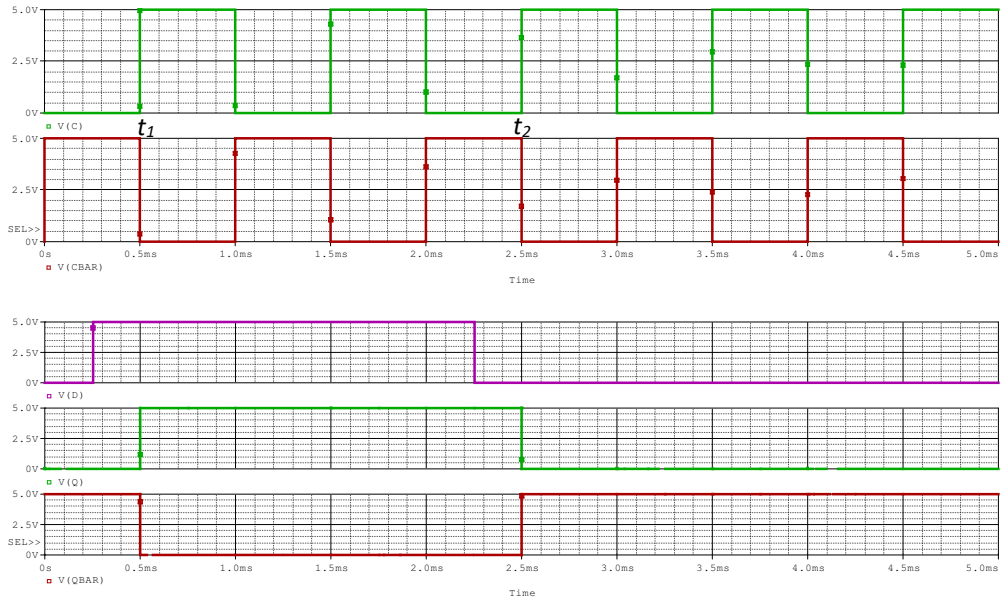

Read the cases on the rising edge of the clock signal

time	D	Q	Qbar
t1	1	1	0
t2	0	0	1

Q follows D at every rising edge of clock.

D flip-flop is edge triggered.

D becomes 1 before t1, but it's not triggered until t1;

D becomes 0 before t2, but it's not triggered until t2;